# Mobile Radio Technology

Voting receiver systems, p. 10

Quality management Build a shielded room 5kHz linear modulation Return-loss bridge applications

An INTERTEC Publication

# Servicing pagers: Build a shielded room

Part 1—A do-it-yourself shielded room helps to isolate a signal generator from nearby paging transmitter signals while troubleshooting pagers. Here are some suggestions for building your own.

# By David Ludvigson

When servicing any type of pagers, certain requirements must be met to guarantee good-quality results.

In large metropolitan areas, such as Houston, many paging transmitters *always* are operating; therefore, pager alignment usually is difficult because the signal generator's output may be "swamped" by an on-frequency paging transmitter.

To date, the only effective means of isolating these signal sources has been to enclose the test equipment and the operator within a copper shield.

Manufactured shielded rooms that are big enough *are* expensive; nevertheless, after setting up the signal generator and trying to align a pager without any shielding, I soon realized that patience and sainthood await the technician working under those conditions!

In the corner of an electronics outlet


Ludvigson is a technician in Houston.




Four pleces of double-sided printed circuit board material make up the back wall of the test bench.



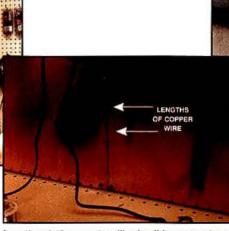Raymond, my co-worker, cuts the aperture for the ac power lines.



 



Raymond checks the wall-ceiling seam. Earlier construction of the shielded room has been sheetrocked and finished. The black door strip is made of conductive foam.



Centrally located, the ac outlet strip is connected to an electromagnetic interference (EMI) filter behind the panel.

store I found some double-sided printed circuit board material at a reasonable price. Enough of these could tile a small room, so my employer, JJ Sounds, purchased several dozen 1.5-foot  $\times$  2-foot sheets.

With boards of these dimensions, about 78 sheets are required to cover the walls. floor and ceiling in a room measuring 4 feet  $\times$  8 feet  $\times$  6 feet. Additional pieces of circuit board are needed to finish the door, and special attention is required around air

conditioning vents, lighting fixtures and ac power outlets.

The framework is a curious mixture of  $2^{"} \times 4^{"}$  and  $2^{"} \times 2^{"}$  materials. Sheetrock screws secure the circuit board material to the frame, with lengths of 12-gauge, tensilized, solid copper wire soldered every four inches to adjoining tiles on the top, sides and bottom.

Small holes were drilled to pass ac power lines, and electromagnetic interference (EMI) filters were placed between the power source and the outlet strips located inside the room.

The door presented an interesting problem because it had to present a sealed plane in common with the walls and floor. A length of conductive foam was used as a pressure seal against the closed door.

Accompanying photographs show the crew of JJ Sounds building the test bench for the homemade shielded room.

Although the idea of using circuit board material may be innovative, the construction is a large undertaking. No matter what, the room is never perfectly square. Gloves and masks should be worn when cutting tiles to size for protection from copper chips and fiberglass dust.

The walls may be finished in anything from sheetrock to carpeting, but the floor requires plywood over the copper-clad fiberglass to distribute the technician's weight without cracking the circuit board material. It might be fair to equate the care and construction of the shielded room to that taken in building the pyramids of Egypt—if labor may be provided in place of currency, the shielded room is relatively inexpensive.

The do-it-yourself shielded room's over-




network of mobile and handheld radio transmissions in the most remote of terrain. Wherever life is in danger, the

Tait Portable Repeater Station brings the promise of help.

Tait Electronics U.S.A. Inc

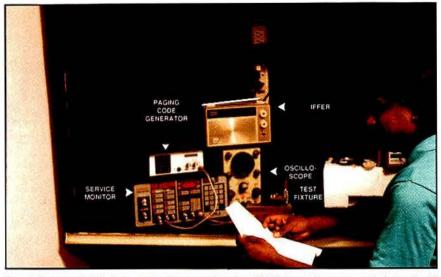9434 Old Katy Road, Suite 1 Houston Texas 77055, USA Phone (1) (713) 984-866 Outside Texas 800 222-1255. Fax (1) (713) 468-694



Once it is covered with dark speaker-box carpeting, the shielded room becomes as dark as a tomb! The Ramsey Com 3 service monitor serves as a test monitor. Above the monitor is a Cushman POCSAG and Golay paging code generator. The Motorola RTL-1005 radiation test fixture is in front of an old RCA oscilloscope. Above the scope rests the IFFER, a piece of test equipment built by the author. Pete, another co-worker, consults a frequency and format chart.

all performance has been good.

Reception on transistor radios and TV sets dies when they are placed in the room. Pagers at 931MHz are almost deaf to paging transmitters located three miles away, reducing their interference by more than 50dB.

To hear any of the paging transmitters on the Ramsey Com 3 service monitor requires an external antenna fed through coax; otherwise, the paging transmitters are just background noise.

Justification for building a shielded room is a matter of individual test locations relative to nearby paging transmitters. If a repair location is within several miles of many transmitters, the quality of pager alignments will improve drastically when using a shielded room.

#### Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds, South Houston, TX, and my co-workers Raymond, Tim and Pete, for their help with this project.

### Postscript

"Copper coffin" is my nickname for the do-ityourself shielded room because receivers "die" when they are brought inside of it. The editor thinks it is too morbid a name to use in the article title, but I like it. I'm experimenting with using aluminum foil to build a shielded room called the "tin foil tomb."





# Auto-Trac's Fleetservice System is your map to success.

Auto-Trac's Fleetservice System gives you a cost effective leading-edge solution for all vehicle tracking applications. The Fleetservice System incorporates the latest in GPS technology, two-way data communications and computerized graphic mapping to improve your fleet planning, dispatching, tracking and

safety. The computerized maps display each vehicle's location and status so you can act quickly and accurately to various situations. The Fleetservice System gives you precise information in an instant. Progress from the 20th to the 21st Century with Auto-Trac!


For more information or a free evaluation of the Fleetservice System call (214) 480-8145 or fax (214) 907-2292.

TA

9330 LBJ Freeway Suite 380 Dallas, TX 75243



 The journal of mobile communications technology



Service monitor tips Pager repair equipment Satellite receiver systems Service quality management Combiner and divider networks

# Servicing pagers: Build an 'IFFER'

Part 2—The IF section from a transistor radio makes an ideal accessory for the test fixture designed for Bravo pagers. Whether you use a shielded room or not, the accessory improves alignment results.

### **By David Ludvigson**

One day, a heavy brass object arrived at JJ Sounds, where I work.

The company owner, J.H. Kim, looked completely baffled. "How do you use?" he asked.

I took a look and chuckled. It was the Motorola RTL-1005 test fixture: nearly \$500 worth of enclosed antenna planes and shielding with a cantilevered set of springs for test probes. To the uninitiated, it must closely resemble the Wouff Hong!\* (See Photo 1 and Figure 1 below.)

Following the directions for modifying the test fixture for use with Bravo series

\*The Wouff Hong, from an amateur radio legend, is a ficticious device said to be used for punishing radio operators who misbehave.

Ludvigson is a technician in Houston.

# Pager servicing series

"Servicing Pagers: Build a Shielded Room," January 1994.

"Servicing Pagers: Build An 'IFFER'," February 1994.

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

pagers requires a few minutes of work, and then a bit more time is required to get the assembly to drop the test probes across test point M1 and ground on a Bravo. (See Photo 2 on page 38.) Unfortunately, after finally adjusting everything, problems just seemed to follow.

First, the pager has to be put into the monitor mode. It seems that these units

spend a good deal of their time turned *off* until they receive the appropriate preamble paging code. Turning the Bravo into a fulltime receiver involves turning the pager off and depressing both the black and gray buttons simultaneously while turning the pager back on to the *beep* mode.

A steady 3.2kHz tone follows. You now have two seconds to release both pushbuttons; quickly depress the gray button and release it. The word PAGING with an optional suffix will appear. Now you can troubleshoot the pager reliably.

While the window displays the word PAGING, insert the Bravo (with the back cover removed) into the test fixture. Close the clamp to connect the decoupling network to M1 and ground.

According to Motorola, alignment of the Bravo can be achieved with an ac millivoltmeter when subjected to an "onfrequency" signal. As I adjusted the output level of the Ramsey Com 3, there were times when the millivoltmeter responded

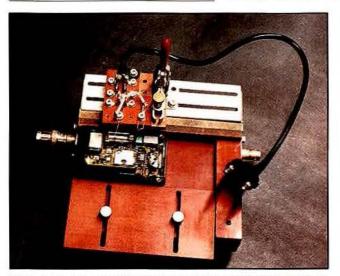


Photo 1. The Motorola RTL-1005 is nearly \$500 worth of enclosed antenna planes and shielding with a cantilevered set of springs for test probes.

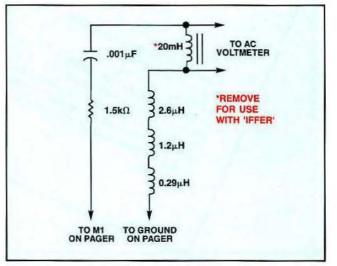


Figure 1. To use the IFFER with the RTL-1005 test fixture, remove the 20mH choke across the output. Otherwise, the inductor swamps the IFFER's input.



# Return Loss Bridges Low Cost Swept SWR

RLB150 bridges can be used with spectrum analyzer/tracking generator or service monitor for swept SWR measurements. This technique simplifies tuning of antennas, cavities, duplexers, isolators and many other RF devices. They also can be used for cable insertion loss and impedance measurements.

Eagle<sup>®</sup> bridges have high directivity, five watt power rating and built-in termination.

| Model     | Freq MHz | Price    |
|-----------|----------|----------|
| RLB150N3B | 5-1000   | \$389.00 |
| RLB150N3C | 5-1300   | \$425.00 |
| RLB150N5A | 5-3000   | \$579.00 |

FREE application note: "High Performance VSWR Measurements". Call and ask for it! Catalogue covers bridges, cable sets and other useful equipment.



Circle (31) on Fast Fact Card

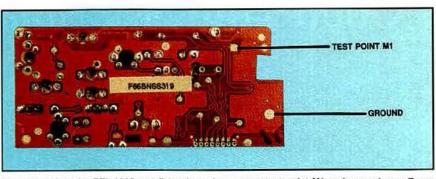


Photo 2. Adjust the RTL-1005 test fixture's probes across test point M1 and ground on a Bravo pager.

smoothly, and other times when it jumped all over the place.

We had not built the shielded room yet, and I was certain that signals from nearby paging transmitters were interfering with the pager test measurements. (See Part 1 in the January issue for information about building the do-it-yourself shielded room.)

Test point M1 is at the input of a 455kHz intermediate frequency (IF) amplifier, and it is isolated by a ceramic filter. To be able to differentiate between the signal from the signal generator and signals from the onfrequency paging transmitters, I use an external 455kHz IF strip followed by an audio detector and audio frequency (AF) power amplifier. By connecting an oscilloscope across the loudspeaker, I can see and hear when the pager is properly tuned.

To find a suitable IF strip, 1 experimented with a transistor AM radio. These radios are plentiful, and the part with a 455kHz IF amplifier, an audio detector and an AF amplifier forms about <sup>4</sup>/<sub>5</sub> of the radio.

Standard transistor radios have a converter that feeds two IF stages at 455kHz. Coupling from M1 on the pager through the radiation test fixture to a point in the IF of an external radio provides several



Circle (32) on Fast Fact Card

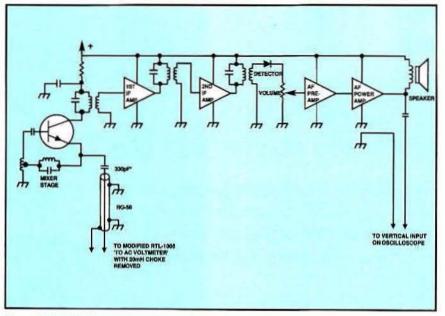


Figure 2. The IFFER is an AM transistor radio's intermediate frequency (IF) strip. A 330pF capacitor (marked with an asterisk) is tiled to the primary side of the AM radio's converter, and the radio is tuned to any unused frequency.

#### advantages.


First, the AM radio continues to operate as an AM radio. Second, the signal at M1 is sufficiently strong to be transported easily over three feet of RG-58 coaxial cable and translated at the external IF strip. (See Figure 2 to the left.)

With the IFFER in place, the 20mH choke across the output of the RTL-1005 is removed. This inductor swamps the input to the IFFER and just gets in the way. A 330pF capacitor is tied to the primary side of the converter in the AM radio, and the radio is tuned to any unused frequency in the broadcast band.

With the IFFER, pager alignment is vastly improved. Standard Sinadder techniques of using a 3.5kHz-deviated 1kHz tone on the selected frequency are sufficient. Unless you have a shielded room such as the one described in Part 1 of this series, on-frequency "rattling" by nearby paging transmitters will upset any alignment attempt. There is no uncertainty as to the cause of erratic meter readings when using the IFFER; you can both see and hear the interference.
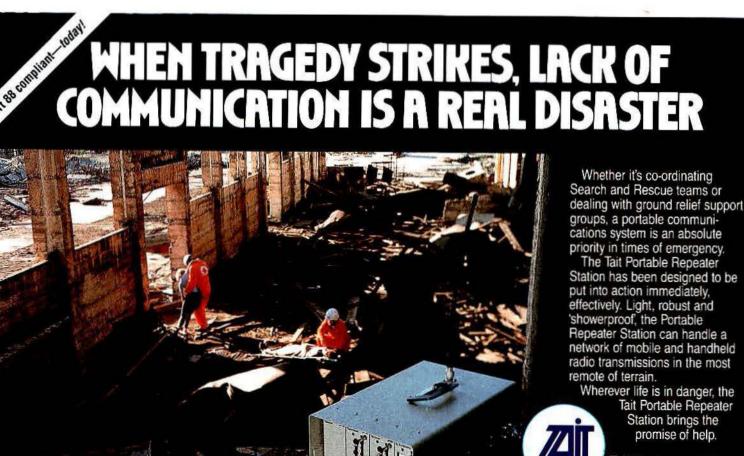
### Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds, South Houston, TX, and co-workers Raymond, Tim and Pete, for their help with this project.



Tait Electronics U.S.A. Inc

9434 Old Katy Road, Suite 11 Houston Texas 77055, USA. Phone (1) (713) 984-868 Outside Texas 800 222-1255. Fax (1) (713) 468-694

Citcle (24) on East East Courd

March 1994/\$3.00

# Mobile Radio Technology

The journal of mobile communications technology

1.03 AM

6

la on

# Personal communicator, p. 10

Servicing pagers Quality management Field intensity vs. signal level IWCE/Spring preview and guide

An INTERTEC Publication

# Servicing pagers: Frequencies, coding formats

Part 3—'Hooking up' customers so their pagers work on one of the various paging services in a given area is simple with the right equipment and information about crystal frequencies, receiver boards and decoder boards.

### By David Ludvigson

Bravo pagers are built to receive paging messages sent in two types of digital code, POCSAG and Golay.

With the POCSAG code, some of the pager's silicon chips decode the slow drawl of 512 bits per second (bps). Other chips can decode at 1,200bps, and yet another version races along at 2,400bps.

Golay, on the other hand, operates at a single rate of speed, forcing all the needed data into a well-defined timeframe.

From the retailer's point of view, this description summarizes all he needs to know about Bravo pager decoder boards. With this information and a 10-power magnifying lens, he has just about mastered the Bravo decoder. At the end of this article, we will hand him his degree.

Previous articles in this series have shown how a modest investment provides a signal generator, a POCSAG-Golay code generator, the radiation test fixture, the IFFER IF strip testing device and a do-ityourself shielded room—everything neces-

Ludvigson is a technician in Houston.


sary to handle service and repairs. An airtime supplier such as Pagenet or Pagemart can provide pagers, capcodes, beeper numbers and, often, the necessary crystals to put Bravo pagers on their frequencies. Programmers for Bravo, Bravo Plus, and Bravo Express are available from Motorola.

Capcodes and pager telephone numbers usually come in pairs. The pager telephone number is the usual seven-digit number that the caller dials from a Touch-Tone telephone. Capcodes usually contain either six digits or seven digits: six digits for Golay codes (sometimes followed by the letter "F"), or seven digits for POCSAG.

Golay codes often are used on paging systems using radio frequencies below 450MHz, and POCSAG generally is used (at varying speeds) above 150MHz.

The frequencies and formats chosen by a retailer must reflect both what pagers he sells and what pagers come in for a "hookup." If a customer wants a hookup for a pager crystalled to 152.24 MHz (with a POCSAG 512 decoder), the retailer probably will want to re-crystal the pager to "his" frequency of, say, 152.84MHz, for example, where the POCSAG 512 format is used, too.

In Houston, three paging carriers served

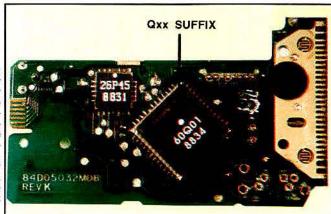

by JJ Sounds operate POCSAG systems between 929MHz and 932MHz. All of them provide 1,200bps service. In addition, one provides 512bps service and another provides 2,400bps service, and they *all* want me to "hookup" customers!

The Bravo pager is well-designed. It is modular—it has two circuit boards: One is a receiver, and the other is the decoder. The modular construction allows the retailer to remove the receiver from the decoder to customize the entire unit to the retailer's frequency and format.

Several tables are provided on page 18 for those using the 930MHz Bravo. These tables are used to determine the operating frequency of Bravo pagers merely by looking at the first conversion oscillator and second conversion oscillator crystal frequencies.

The first intermediate frequencies are either 17.9MHz or 45.00MHz. Determining the first conversion oscillator frequency is a matter of simple math:

[(receiver frequency) – (first IF frequency)] / 12 = first conversion crystal frequency.

Up to this point, you are dealing with a fairly common radio receiver. The big difference is in the triple-conversion superheterodyne circuit that provides a narrowbandwidth receiver capable of "ignoring" other transmitters operating close to the same frequency.

The detector used in the Bravo provides several useful outputs, each of which is metered easily by the "flap" of the RTL-1005 test fixture. Astute technicians will note an audio output pin (TP6) and question the use of the IFFER for alignment rather than this test point.

The IFFER simply provides greater gain at 455kHz, thus allowing a pager to be drastically mis-tuned and still have enough signal to perform "brute-force" alignments.

Data out and data in lines go to and from

Photo 1. The suffix of the identification number printed on the decoder microprocessor is known as the Qxx suffix because it includes the letter Q and two digits. The suffix indicates the micro-processor's paging 'language' (POCSAG or Golay) and speed. A table in the text gives the language and speed that go with each suffix.

# A Motorola Thoroughbred. **R-2600**

The result of years of breeding by design and technical evolution. The Motorola R-2600 has the sleek quality of a thoroughbred and quick manners of a well trained quarterhorse. It knows what's needed with only a soft touch. The R-2600. Computerized, digital accuracy, analog feel. Dependable on the job. Well bred.



- AM / FM Signal Generator
- Duplex Offset Generator
- See & Hear Spectrum Analyzer SINAD Distortion Meter
- Off-the-Air Sensitivity Receiver
- Relative Signal Strength Meter
- Auto-Tune
- Terminated RF Wattmeter
- Tracking Generator (optional)

- Soft Keys and Windowing
- PL/DPL Encode / Decode
- Oscilloscope
- Digital Voltmeter
  - Frequency Counter
  - Serial Printer Interface
  - ... and More

For Communicatons System Analyzer information: Call 1-800-235-9590.



| Carrier Freq.        | 1st Osc. Freq.         | 930.5125             | 76.051042              |
|----------------------|------------------------|----------------------|------------------------|
| (MHz)                | (MHz)                  | 930.5375             | 76.053125              |
|                      |                        | 930.5625             | 76.055208              |
| 929.0125             | 75.926042              | 930.5875             | 76.057292              |
| 929.0375             | 75.928125              | 930.6125             | 76.059375              |
| 929.0625             | 75,930208              | 930.6375             | 76.061458              |
| 929.0875             | 75.932292              | 930.6625             | 76.063542              |
| 929.1125             | 75.934375              | 930.6875             | 76.065625              |
| 929.1375             | 75.936458              | 930.7125             | 76.067708              |
| 929.1625             | 75.938542<br>75.940625 | 930.7375             | 76.069792<br>76.071875 |
| 929.1875<br>929.2125 | 75.942708              | 930.7625<br>930.7875 | 76.073958              |
| 929.2375             | 75.944792              | 930.8125             | 76.076042              |
| 929.2625             | 75.946875              | 930.8375             | 76.078125              |
| 929.2875             | 75.948958              | 930.8625             | 76.080208              |
| 929.3125             | 75,951042              | 930.8875             | 76.082292              |
| 929.3375             | 75.953125              | 930.9125             | 76.084375              |
| 929.3625             | 75.955208              | 930.9375             | 76.086458              |
| 929.3875             | 75.957292              | 930.9625             | 76.088542              |
| 929.4125             | 75.959375              | 930.9875             | 76.090625              |
| 929,4375             | 75.961458              | 931.0125             | 76.092708              |
| 929.4625             | 75.963542              | 931.0375             | 76.094792              |
| 929.4875             | 75.965625              | 931.0625             | 76.096875              |
| 929.5125             | 75.967708              | 931.0875             | 76.098958              |
| 929.5375             | 75.969792              | 931.1125             | 76.101042              |
| 929.5625             | 75.971875              | 931.1375             | 76.103125              |
| 929.5875             | 75.973958              | 931.1625             | 76.105208              |
| 929.6125             | 75.976042<br>75.978125 | 931.1875<br>931.2125 | 76.107292 76.109375    |
| 929.6375<br>929.6625 | 75.980208              | 931.2125             | 76.111458              |
| 929.6875             | 75.982292              | 931.2625             | 76.113542              |
| 929.7125             | 75.984375              | 931.2875             | 76.115625              |
| 929.7375             | 75.986458              | 931.3125             | 76.117708              |
| 929.7625             | 75.988542              | 931.3375             | 76.119792              |
| 929,7875             | 75.990625              | 931.3625             | 76.121875              |
| 929.8125             | 75.992708              | 931.3875             | 76.123958              |
| 929.8375             | 75.994792              | 931,4125             | 76.126042              |
| 929.8625             | 75.996875              | 931.4375             | 76.128125              |
| 929.8875             | 75.998958              | 931.4625             | 76.130208              |
| 929.9125             | 76.001042              | 931.4875             | 76.132292              |
| 929.9375             | 76.003125              | 931.5125             | 76.134375              |
| 929.9625             | 76.005208              | 931.5375             | 76.136458              |
| 929.9875             | 76.007292              | 931.5625             | 76.136542              |
| 930.0125             | 76.009375              | 931.5875             | 76.140625              |
| 930.0375             | 76.011458              | 931.6125             | 76.142708              |
| 930.0625             | 76.013542              | 931.6375             | 76.144792              |
| 930.0875<br>930.1125 | 76.015625<br>76.017708 | 931.6625             | 76.145875<br>76.148958 |
| 930.1375             | 76.019792              | 931.6875<br>931.7125 | 76.151042              |
| 930.1625             | 76.021875              | 931.7375             | 76.153125              |
| 930.1875             | 76.023958              | 931.7625             | 76.155208              |
| 930.2125             | 76.026042              | 931.7875             | 76.157292              |
| 930.2375             | 76.028125              | 931.8125             | 76.159375              |
| 930.2625             | 76.030208              | 931.8375             | 76,161458              |
| 930.2875             | 76.032292              | 931.8625             | 76.163542              |
| 930.3125             | 76.034375              | 931.8875             | 76.165625              |
| 930.3375             | 76.036458              | 931.9125             | 76.167708              |
| 930.3625             | 76.038542              | 931.9375             | 76.169792              |
| 930.3875             | 76.040625              | 931.9625             | 76.171875              |
| 930.4125             | 76.042708              | 931.9875             | 76.173958              |
| 930.4375             | 76.044792              |                      |                        |
| 930.4625             | 76.046875              | $F_c = 12F_o$        | 17.9MHz                |
| 930,4875             | 76.048958              | 2nd Usc. Fi          | reg. = 17.445MH        |

#### NOTE

This table applies to KXN6370A crystals (Y501) which are used in Bravo pagers with receiver board kit number NRF4071A-D ONLY. Bravo pagers with receiver board kit number NRF4071E use NKN3000A crystals.

|      |         | Marking |                 |   | C517 M     | arkings |            |
|------|---------|---------|-----------------|---|------------|---------|------------|
| Grp. | Color   | Code    | ode EIA Marking |   | Color Code |         | C517 Part  |
|      | 1st Dot | 2nd Dot | Code            |   | 1st Dot    | 2nd Dot | Number     |
| 1    | Black   | None    | COG             | 0 | Black      | None    | 2182358G41 |
| 2    | Violet  | None    | U2J F           | R | Violet     | None    | 2182358G46 |
| 3    | Orange  | Orange  | P3K             |   | Orange     | Orange  | 2182358G48 |
| 4    | Yellow  | Orange  | R3A             |   | Yellow     | Orange  | 2182358G49 |
| 5    | No Ma   | rkings  | P3K             |   | Orange     | Orange  | 2182358G48 |

NOTE: Failure to replace Y501 and C517 as a pair could result in radio sensitivity at the temperature extremes of operation.

| Comiss Ess-    | 000A (Y551) Os | 930.5125                            | 73,79270 |
|----------------|----------------|-------------------------------------|----------|
| Carrier Freq.  |                |                                     |          |
| (MHz)          | (MHz)          | 930.5375                            | 73.79479 |
| 10000000000000 | Concernance -  | 930.5625                            | 73.79687 |
| 929.0125       | 73.66770       | 930.5875                            | 73.79895 |
| 929.0375       | 73.66979       | 930.6125                            | 73.80104 |
| 929.0625       | 73.67187       | 930.6375                            | 73.80312 |
| 929.0875       | 73.67395       | 930.6625                            | 73.80520 |
| 929.1125       | 73.67604       | 930.6875                            | 73.80729 |
| 929.1375       | 73.67812       | 930.7125                            | 73.80937 |
| 929,1625       | 73.68020       | 930.7375                            | 73.81145 |
| 929.1875       | 73.68229       | 930.7625                            | 73.81354 |
| 929.2125       | 73.68437       | 930.7875                            | 73.81562 |
| 929.2375       | 73.68645       | 930,8125                            | 73.81770 |
| 929,2625       | 73.68854       | 930.8375                            | 73.81979 |
| 929.2875       | 73.69062       | 930.8625                            | 73.82187 |
| 929,3125       | 73.69270       | 930.8875                            | 73.82395 |
| 929.3375       | 73.69479       | 930.9125                            | 73.82604 |
| 929,3625       | 73.69687       | 930.9375                            | 73.82812 |
| 929.3875       | 73.69895       | 930.9625                            | 73.83020 |
| 929.4125       | 73.70104       | 930.9825                            | 73.83229 |
| 929.4125       | 73.70312       | 931.0125                            | 73.83437 |
|                |                |                                     |          |
| 929.4625       | 73.70520       | 931.0375                            | 73.83645 |
| 929.4875       | 73.70729       | 931.0625                            | 73.83854 |
| 929.5125       | 73.70937       | 931.0875                            | 73.84062 |
| 929.5375       | 73.71145       | 931.1125                            | 73.84270 |
| 929.5625       | 73.71354       | 931.1375                            | 73.84479 |
| 929.5875       | 73.71562       | 931.1625                            | 73.84687 |
| 929.6125       | 73.71770       | 931.1875                            | 73.84895 |
| 929.6375       | 73.71979       | 931.2125                            | 73.85104 |
| 929.6625       | 73.72187       | 931.2375                            | 73.85312 |
| 929.6875       | 73.72395       | 931.2625                            | 73.85520 |
| 929.7125       | 73.72604       | 931.2875                            | 73.85729 |
| 929.7375       | 73.72812       | 931.3125                            | 73.85937 |
| 929.7625       | 73.73020       | 931.3375                            | 73.86145 |
| 929.7875       | 73.73229       | 931.3625                            | 73.86354 |
| 929.8125       | 73.73437       | 931.3875                            | 73.86562 |
| 929.8375       | 73.73645       | 931.4125                            | 73.86770 |
| 929.8625       | 73.73854       | 931.4375                            | 73.86979 |
| 929.8875       | 73.74062       | 931.4625                            | 73.87187 |
| 929,9125       | 73.74270       | 931,4875                            | 73.87395 |
| 929,9375       | 73,74479       | 931.5125                            | 73,87604 |
| 929.9625       | 73.74687       | 931.5375                            | 73.87812 |
| 929,9875       | 73.74895       | 931.5625                            | 73,88020 |
| 930.0125       | 73.75104       | 931.5875                            | 73.88229 |
| 930.0375       | 73.75312       | 931.6125                            | 73.88437 |
| 930.0625       | 73.75520       | 931.6375                            | 73.88645 |
| 930.0875       | 73.75729       | 931.6625                            | 73.88854 |
| 930.1125       |                |                                     |          |
|                | 73.75937       | 931.6875                            | 73.89062 |
| 930.1375       | 73.76145       | 931.7125                            | 73.89270 |
| 930.1625       | 73.76354       | 931.7375                            | 73.89479 |
| 930.1875       | 73.76562       | 931.7625                            | 73.89687 |
| 930.2125       | 73.76770       | 931.7875                            | 73.89895 |
| 930.2375       | 73.76979       | 931.8125                            | 73.90104 |
| 930.2625       | 73.77187       | 931.8375                            | 73.90312 |
| 930.2875       | 73.77395       | 931.8625                            | 73.90520 |
| 930.3125       | 73.77604       | 931.8875                            | 73.90729 |
| 930.3375       | 73.77812       | 931.9125                            | 73.90937 |
| 930.3625       | 73.78020       | 931.9375                            | 73.91145 |
| 930.3875       | 73.78229       | 931.9625                            | 73.91354 |
| 930.4125       | 73.78437       | 931.9875                            | 73.91562 |
| 930.4375       | 73.78645       |                                     |          |
| 930.4625       | 73.78854       | F <sub>c</sub> = 12F <sub>o</sub> + | 45MHz    |
|                | 73.79062       |                                     |          |

#### NOTE

This table applies to NXN3000A crystals (Y551) which are used in Bravo pagers with receiver board kit number NRF4071E *ONLY*. Bravo pagers with receiver board kit number NRF4071A-D use KXN6370A crystals.

|      | Crystal Marking |         | C567 Markings |   |         |         |            |
|------|-----------------|---------|---------------|---|---------|---------|------------|
| Grp. | Color           | Code    | EIA Marking   |   | Color   | Code    | C567 Part  |
|      | 1st Dot         | 2nd Dot | Code          |   | 1st Dot | 2nd Dot | Number     |
| 1    | Black           | None    | COG           | 0 | Black   | None    | 2182358G41 |
| 2    | Violet          | None    | U2J           | R | Violet  | None    | 2182358G46 |
| 3    | Orange          | Orange  | РЗК           |   | Orange  | Orange  | 2182358G48 |
| 4    | Yellow          | Orange  | R3A           |   | Yellow  | Orange  | 2182358G49 |
| 5    | No Ma           | rkings  | P3K           |   | Orange  | Orange  | 2182358G48 |

NOTE: Failure to replace Y551 and C567 as a pair could result in radio sensitivity at the temperature extremes of operation.

# 0-9001

# Our guarantee of total customer satisfaction. In any language.



By itself, quality control no longer assures consistent quality at lowest cost. In today's highly competitive, highly reactive marketplace, it is imperative that we satisfy our customer's needs consistently, and that we do it in a cost effective way. The customer partnerships that we form are long term commitments built on uncompromising integrity. That commitment to always seek improvement in every aspect of our business - is the quality standard to which we have aspired.

As a result, Celwave takes considerable pride in announcing ISO 9001 certification for our manufacturing facilities in Marlboro, New Jersey and Phoenix, Arizona. This international quality standard encompasses all aspects of our business from design through manufacture. We have made a commitment to our customers to listen, to respond, and to excel at what we do. And what we do is to continue to provide the industry's leading telecommunications products...worldwide.

# Celwave

Visit Us at CTIA, Booth #2936.

ellai (

ella -

2 Ryan Road, Marlboro, NJ 07746-1899 Phone: (908) 462-1880 • Fax: (908) 462-6919 Circle (15) on Fast Fact Card

1993 Radio Frequency Systems, Inc.


an 8-pin connector. At this point, the receiver circuitry ends, and the next step is to look at filters and decoders, which are on the second board.

### Decoders

Motorola Bravo pagers use dedicated silicon chips to decode either POCSAG or Golay formats.

These same chips provide output signals to the liquid crystal display (LCD) and control signals to make the pager beep or vibrate. They also have been programmed to respond to various portions of an encoded signal train.

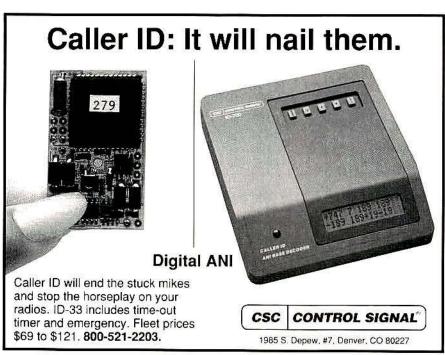A review of these decoders' schematic diagrams will convince a technician quickly that everything here is only a matter of time—or *timing*. Again, Motorola has simplified this technical wonderland by marking each microprocessor with an easily converted code number. It starts with



Circle (16) on Fast Fact Card



Circle (17) on Fast Fact Card

5105860 and has a suffix of Qxx, where xx is a number between 01 and 16. (See Photo 1 on page 16.)

The following table indicates the "language" and speed of the various processors.

| PROCESSOR | LANGUAGE | SPEED                 |
|-----------|----------|-----------------------|
| Q01       | Golay    |                       |
| Q04       | POCSAG   | 512bps                |
| Q06       | POCSAG   | 512bps                |
| Q07       | POCSAG   | 1,200bps              |
| Q08       | Golay    | 0.9497559950099980899 |
| Q10       | POCSAG   | 512bps                |
| Q11       | POCSAG   | 1,200bps              |
| Q12       | Golay    | 8 S                   |
| Q14       | POCSAG   | 512bps                |
| Q15       | POCSAG   | 1,200bps              |
| Q16       | Golay    |                       |

This table, along with a list of frequencies and formats supplied by the airtime vendor, is indispensable for determining rapidly the feasibility of hooking up Bravo pagers.

In Houston, JJ Sounds has signed on with three big airtime suppliers. They operate on the following frequencies and formats:

| 152.24MHz   | Golay  |                 |
|-------------|--------|-----------------|
| 152.84MHz   | POCSAG | 512bps          |
| 454.10MHz   | Golay  |                 |
| 929.6625MHz | POCSAG | 1,200, 512bps   |
| 929.7125MHz | POCSAG | 1,200bps        |
| 931.2875MHz | POCSAG | 2,400, 1,200bps |
| 931.4875MHz | POCSAG | 1,200, 512bps   |
| 931.6875MHz | POCSAG | 1,200bps        |

With a *frequency and format chart*, programming Bravo pagers becomes a process of matching crystals to the operating frequency needed, matching a receiver board to a decoder board and then heading to the Bravo Programmer.

# Pager servicing series

"Servicing Pagers: Build a Shielded Room," January 1994.

"Servicing Pagers: Build An 'IFFER'," February 1994.

"Servicing Pagers: Frequencies, Coding Formats," March 1994.

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

#### Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds. South Houston, TX, and co-workers Raymond, Tim and Pete, for their help with this project. April 1994/\$3.00



The journal of mobile communications technology

# Tower monitoring, p. 10

Lightning protection Servicing pagers Two-way simulcasting Fiber-optics

# Servicing pagers: From bench to programmer

Part 4—Follow these steps to choose an appropriate pager frequency, install the right crystal, verify proper receiver and decoder operation, and program the pager to work with a customer's pager telephone number.

# By David Ludvigson

With a customer's Bravo pager in hand, turn the slide switch all the way up to the *beep mode*.

A rapid series of continuous beeps indicates a weak battery; replace it if necessary.

With a good battery, the pager should emit four sets of "beep-beep" noises, and the display lamps should flash before the pager settles down to "lights out" and a broken horizontal bar across the display.

Up to this point, the microprocessor has gone through its "wake-up" sequence. Failure at any point of this wake-up sequence usually indicates a failure of the decoder board.

Turn the pager off, and then turn the pager's slide switch all the way up (to beep mode) while depressing both the gray and black push-buttons beneath the liquid crystal display (LCD). Quickly release both push-buttons and rapidly depress the gray button. Upon release, the word *paging* (with an optional suffix) will appear in the LCD.

Another depression of the gray button will reveal a set of 1s and 0s. These are the options (in binary format) that have been programmed into the unit. Another depression will reveal the capcode (in decimal format). This condition, in which all the internal data may be read, is called the *service mode*.

While the Bravo is in service mode and *paging* is displayed on the LCD, use a jeweler's hexdriver to remove the two screws holding the case together. Remove the back cover.

At this point, insert the pager into the radiation test fixture with the IFFER attached to test point M1. Using the presets

Ludvigson is a technician in Houston.

of the Ramsey Com 3 service monitor, generate an RF signal modulated with a 1kHz tone at 4.5kHz deviation and scan through the available frequencies to locate the pager's operating frequency.

The IFFER will show (on an external oscilloscope) how well the first local oscillator has been adjusted. Failure to locate the signal will require disassembly of the pager.

Turn the pager off. Remove the battery clip at the bottom of the case, and remove the battery. Remove the diffuser lens behind the LCD.

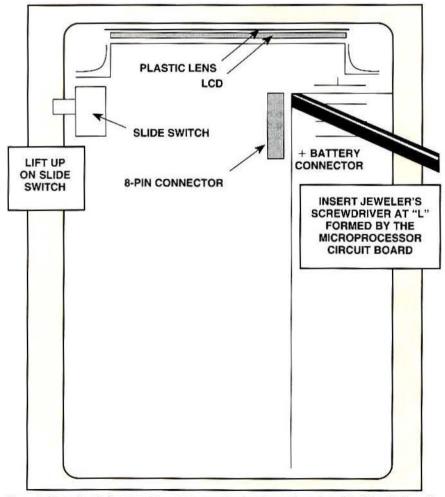


Figure 1. Use a jeweler's screwdriver to remove the decoder and receiver circuit boards from the Bravo pager housing.

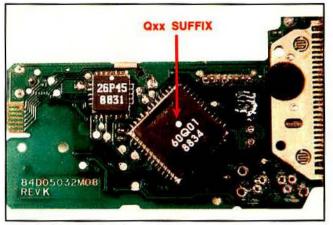


Photo 1. The suffix of the identification number printed on the decoder microprocessor is known as the Qxx suffix because it includes the letter Q and two digits. The suffix indicates the microprocessor's paging 'language' (POCSAG or Golay) and speed.

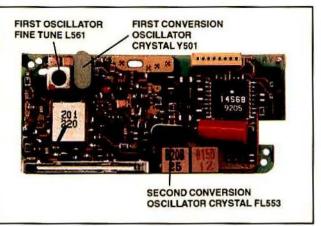


Photo 2. A view of the NRF4071E 928MHz–932MHz receiver board with a 17.9MHz IF shows the locations of the first conversion oscillator crystal, second conversion oscillator crystal and fine-tuning inductor L561.

With a small screwdriver placed at the "L" formed by the circuit board (to the left of the positive battery spring) and while lifting the lever of the side-mounted *on-vibrate-beep* switch, gently wedge the entire unit from the case. (See Figure 1 on page 22.)

Turn the circuit boards over to read the Qxx number on the microprocessor. (See

Photo 1 above.) Let's call it *Q07* for our discussion, so (from our *frequency and format chart* in Part 3) the pager should operate with POCSAG at a rate of 1,200bps.

Gently rock the 8-pin junction, separating the two boards. With a small screwdriver, move the boot around the first conversion oscillator crystal. (See Photo 2 above.) Unless your eyes are good, I suggest the use of a 10-power (10X) loupe (magnifying lens) as an aid in reading the frequency information from the crystal.

Often, the crystal is installed backward, with the frequency information facing the fine-tuning inductor housing. In this case, note the characteristics of the antenna and the preselector tuning networks.



Visit us at IWCE, Booth #452

Circle (21) on Fast Fact Card

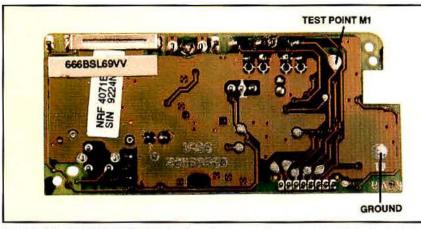


Photo 3. Adjust the RTL-1005 test fixture's probes across the receiver board's test point M1 and ground.

Having determined the range of receiver frequencies, change the crystal to match the desired frequency provided by the airtime carrier. The *frequency and format chart* for your own area will tell whether the capcode can be programmed to operate on POCSAG at 1,200bps for any given radio frequency.

From the F&F chart given as an example in Part 3 and assuming a 930MHz

pager, paging systems on 929.6625 MHz, 929.7125MHz, 931.2875MHz, 931.4875MHz, and 931.6875MHz all use POCSAG at 1,200bps. Experience in Houston has shown transmitter problems with 929.7125MHz and transmitter loading on 931.6875MHz. I might choose 931.2875MHz because the frequency is not heavily loaded—yet.

Determining the first conversion oscil-

lator frequency requires a knowledge of the first intermediate frequency. Subtract either 17.9MHz or 45.0MHz from the operating frequency.

Let's say the first IF frequency is 17.9MHz; therefore

931.2875 - 17.9 = 913.3875

This value (913.3875) is divided by 12 to obtain the first conversion oscillator frequency:

 $913.3875 \div 12 = 76.115625$ 

Remove the original first conversion crystal and install a 76.115625MHz crystal in its place. Trim the crystal leads and reassemble the pager, leaving the back cover off.

Place the pager in the *service mode* with the word *paging* displayed on the LCD. Place the unit in the RTL-1005 test fixture (with the IFFER attached), and bring down the probes to M1 and ground. (See Photo 3 above.)

Radiate a fairly strong (> $500\mu$ V) signal at 931.2875MHz with a 4.5kHz-deviated 1kHz tone. Adjust the fine tuning inductor slug with a ceramic tuning tool until the



Circle (23) on Fast Fact Card


signal from IFFER approximates a sine wave.

If you are in shielded room, such as the one described in Part 1 of this series, you can adjust the pager for maximum sensitivity. As a final check, use the oscilloscope attached to the IFFER and the IFFER's loudspeaker to watch and listen to the activity on 931.2875MHz. While the paging transmitter is active, the difference between the strength of its signal and the signal generator's signal may be on the order of only 10dB.

To this point, you have a working receiver at 931.2875MHz, but the decoder is still untested.

Remove the pager from the radiation test fixture. Depress the gray button to reveal the current capcode in the pager. Set the POCSAG-Golay generator to match the original capcode.

Depress the gray button on the Bravo to

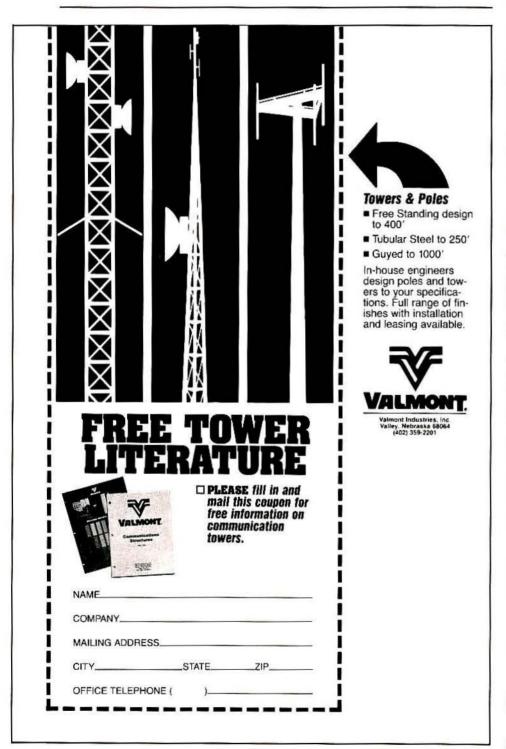

# Placing the Bravo pager in *Test Mode 1*

1. With the pager off, depress both push-buttons beneath the display and bring slide-switch fully up (to *beep position*).

2. A steady tone at 3kHz or higher will be heard.

3. Release both buttons and momentarily depress the gray (*read*) button. The word *paging* (with an optional suffix in some cases) will appear.

4. At this point, the Bravo pager is configured as a full-time receiver. If it should receive its capcode, one lamp will flash and a single beep will be heard from the internal speaker.

# **Reading the capcode**

1. Perform steps 1 through 3 above. 2. Depress the gray (*read*) button several times until the capcode is displayed on the LCD.

show *paging* on the LCD and set the pager back into the radiation test fixture. First defeat the 1kHz tone on the RF signal generator. Then modulate a strong RF signal with the code generator. A single *beep* and a flash of the back-light lamp indicate a working decoder.

Continue to decrease the RF signal while activating the code generator. At a certain point, the pager no longer will respond. In an unshielded room (with pager transmitters active) the pager will have a lot of junk data with which to contend.

Only with a shielded room will an accurate measure of overall sensitivity be obtained.

Okay, the pager understands the old capcode, and the receiver is working. It's time to go to the programmer.

### Bravo programmer

Place the pager into the programmer.

When the programmer is turned on, it plays about 10 seconds worth of commercial messages. Then, it asks the operator to select:

1 GSC (Golay sequential code) or


2 POCSAG

Because you want POCSAG for this pager, select 2. The screen now displays: 1 JRB/JRC

2 BAB

BAB, JRB and JRC were parts of the original model numbers, and probably have been lost as labels were replaced.

Circle (25) on Fast Fact Card

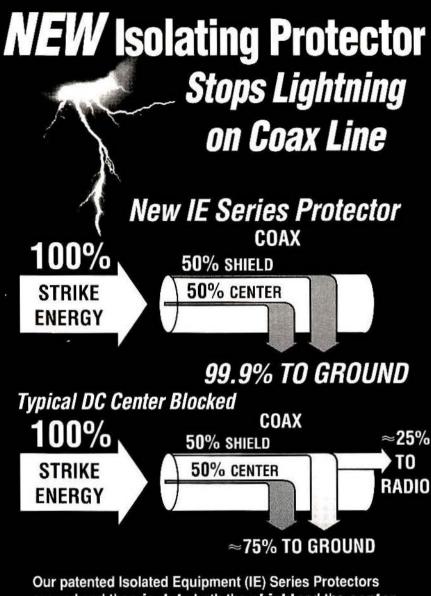

Gur patented isolated Equipment (IE) Series Protectors ground and then *isolate* both the *shield* and the *center* conductor of your coax line. Lightning is diverted to the outside ground system. It can not travel to the equipment chassis and follow the electrical wires to ground which can happen with all other type protectors including 1/4 wave shorted stubs. The IE Series Protectors are available from 1.5MHz to 2.6GHz (to 20GHz Special). This innovative and unique series is **99.9% effective**, setting a whole new meaning to the term "Coax Protector". Of course it's from the World Leader in RF coax protection.

# 1500 models of coax, power and twisted pair protectors . . . plus lightning/EMP and grounding solutions.



(800) 325-7170 (702) 782-2511 FAX: (702) 782-4476

2225 Park Place 🔳 P.O. Box 9000 🔳 Minden, NV 89423-9000

Circle (27) on Fast Fact Card

Pager servicing series

Part 1: "Build a Shielded Room," January 1994.

- Part 2: "Build An 'IFFER'," February 1994.
- Part 3: "Frequencies, Coding Formats," March 1994.

Part 4: "From Bench To Programmer," April 1994.

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

Simply put, JRB/JRC is normal POCSAG code, whereas BAB responds to inverted POCSAG code. Select *1.* 

The screen now presents several options. Because we want to program the Bravo, we select option 2.

The screen now displays ENTER 7 DIGIT CAPCODE.

Select one of the capcodes for 931.2875MHz POCSAG at 1,200bps and enter the capcode. Hit the ENTER key.

The following screens allow a Bravo pager to perform numerous functions and are found in the programming manual which comes with the Bravo Programmer.

After the customizing, the programmer prompts, READY TO PROGRAM? Punch YES.

Any erratic connection between the pager and programmer halts the programming and prompts INSERT PAGER. Some wiggling and wedging might be needed to make proper connection.

The programmer will report PRO-GRAMMING PAGER and PROGRAM-MING FINISHED. Remove the pager, grab your notes, and head for a telephone.

On a Touch-Tone telephone, dial the phone number associated with the capcode you have programmed. Depending on the activity on 931.2875MHz, the pager should sound off in a few minutes. Assuming success, strike out the capcode from your list. This step prevents duplicated pagers and upset customers.

# Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds, South Houston, TX, and co-workers Raymond, Tim and Pete, for their help with this project.

御



# Servicing pagers: The receivers

Part 5—Here are some tips for identifying which frequency bands correspond with which receiver boards in Bravo pagers to help you install the right boards for hooking up new customers.

### By David Ludvigson

Motorola Bravo receivers have been designed for several frequency ranges.

Although these ranges include the range from 33MHz to 50MHz, this discussion covers pagers used at frequencies above 150MHz.

# Quick identification

From the backside, there are few visible differences between most of the Bravo receiver boards—they are all the same size, they all fit the 8-pin connector, and they all do basically the same job.

Our task is to identify which receiver will work in any given portion of the spectrum allowed by our *frequency and function chart*. (See Part 3, March issue.) Again, Motorola has simplified the task.

Located on a sticker on the back side of

Ludvigson is a technician in Houston.

the receiver module is a number. Refer to the following chart for frequency range.

| FREQUENCY<br>RANGE (MHz) | RECEIVER<br>MODULE No. |
|--------------------------|------------------------|
| 929 – 932                | NRF4071A-F             |
| 406 - 420                | NRE6421A,B             |
| 450 - 465                | NRE6423A,B             |
| 465 - 480                | NRE6424A,B             |
| 480 - 495                | NRE6425A,B             |
| 495 - 512                | NRE6426A,B             |
| 450 - 465                | AARE4001A-0            |
| 450 - 465                | AARE4001A-1            |
| 465 - 480                | AARE4002A-0            |
| 465 - 480                | AARE4002A-1            |
| 138 – 143                | NRD7211A,B             |
| 143 - 148.6              | NRD7212A,B             |
| 148.6 - 152              | NRD7213A,B             |
| 152 - 159                | NRD7214A,B             |
| 159 - 164                | NRD7215A,B             |
| 164 - 169                | NRD7216A,B             |
| 169 – 174                | NRD7217A,B             |

These receiver boards are interchangeable; thus, by merely replacing a 932MHz board with a 454MHz board, the pager is capable of operating in a different frequency band. Certain caveats must be noted when trying to interchange Bravo Plus or Bravo Express boards in the simple Bravo. Specifically, they will not work. Pinouts on the 8-pin connector are incompatible.

In passing, the second conversion oscillator in these receivers determines the *polarity* of the received POCSAG or Golay code. Depending on *high-side* or *low-side* signal injection (at the second mixer), the detector *flips* the output polarity of either code format in the same manner as detecting *one side* of a single-sideband signal.

This factor might require attention during the Bravo programming stage (SE-LECT JRB/C or BAB), but it is confirmed easily by the NORMAL/INVERTED position of a POCSAG-Golay generator.

Quick identification of the band of operating frequencies requires a look at the component side of the receiver board.

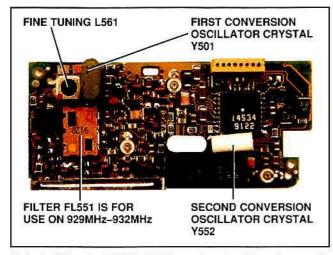


Photo 1. NRF series 929MHz–932MHz receiver circuit boards are easily identified by the small rectangular filter (FL551) used at the output of the RF pre-amplifier. Fine tuning is available by adjusting L561.


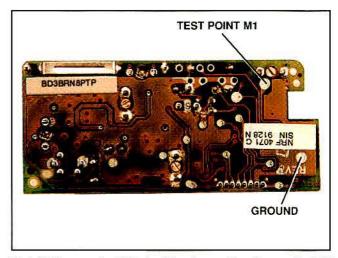


Photo 2. These are the M1 test point and ground locations on the NRF series 929MHz–932MHz receiver circuit boards.

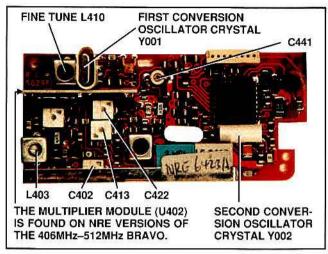

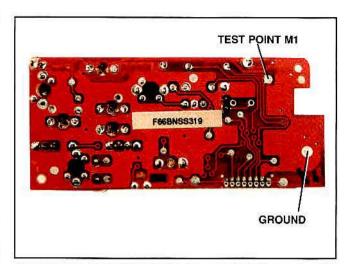


Photo 3. NRE series 406MHz–512MHz receiver circuit boards are identified simply by the ceramic module for the first conversion oscillator stage. Changing crystals requires adjusting both L410 and C441, and 'touch-ups' on C422, C413, L403, and C402. For small frequency changes, try adjusting only L403 and C402.

Photo 4. These are the M1 test point and ground locations on the NRE series 929MHz–932MHz receiver circuit boards.

Antenna and RF pre-amplifier filters tell the whole story.

The 928MHz–933MHz receiver usually has a single band of strapping for an antenna and a small square subassembly for a pre-amplifier filter. For 406MHz–512MHz, the antenna may be either a single strap or a dual-strap (inductively coupled) assembly. When the dual-strap antenna is present, look for a ceramic sub-strated first conversion oscillator. This is a modular multiplier for the first conversion frequency.

Another version of the 406MHz– 512MHz band receivers uses three tuning inductors as a helical filter between the RF pre-amplifier and the mixer. Wide frequency changes require both




a re-alignment and a shielded room, such as the one described in Part 1, January issue, to optimize these inductors effectively,

Receivers equipped to run on 138MHz-174MHz are denoted by the use of a ferrite core surrounded by a single band of metal for an antenna loop. Beneath an identifying sticker are several capacitors placed in a notch across the metal band. The resonant circuit for this band is formed by the distributed capacitance, the values of these


capacitors and the amount of inductance provided by the core.

Another significant clue to the frequency band is the placement of the first conversion oscillator crystal. It is placed parallel to, and at the edge of, the circuit board.

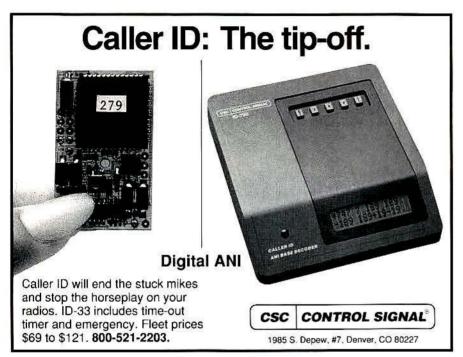Receivers with a ferrite core with several windings of ribbon metal operate below 50MHz and will not be treated in these discussions.



Circle (16) on Fast Fact Card

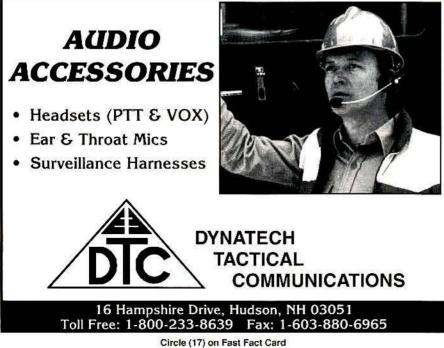

Please note that tuning of these receivers will require a ceramic tuning tool, Severe de-tuning results from the use of metal tools, such as jeweler's tools.

# NRF (929MHz-932MHz) receivers

The 929MHz-932MHz NRF series receiver circuit boards are identified easily by the small rectangular filter (FL551) used at the output of the RF pre-amplifier. (See Photo 1 on page 16.)

Located at one corner of the filter is the first oscillator crystal (Y501). Depending on the frequency of the first intermediate frequency, this crystal's frequency ranges between 73.666MHz and 76.175MHz. Fine tuning is available by adjusting L561.

The alignment of these receivers is straightforward. Radiate a signal into the RTL-1005 (You are in your shielded room, aren't you?) and test receiver sensitivity using M1 and ground. (See Photo 2 on page 16.) If necessary, adjust L561 to center the signal, and adjust the multiplier stage, the RF pre-amp and the second conversion oscillator frequency for optimum performance.

### NRE (406MHz-512MHz) receivers

The 406MHz-512MHz NRE series receiver circuit boards are identified simply by the ceramic module for the first conversion oscillator stage. (See Photo 3 on page 18.)

Alignment can be really difficult without a shielded room because there are several LC networks in the RF pre-amp that interact. Changing crystals requires adjusting both L410 and C441, and "touch-ups" on C422, C413, L403 and C402. For small frequency changes, I suggest adjusting only L403 and C402.

Photo 4 on page 18 shows the M1 test point and ground locations.

### AARE (406MHz-512MHz) receivers


AARE4001A receiver circuit boards cover the range of 450MHz-465MHz and

|            | Pager servicing series                     |
|------------|--|
| Pa         | art 1-"Build a Shielded Room," Janu-       |
| ary I      | 1994.                                      |
| Pa         | art 2-"Build An 'IFFER'," February         |
| 1994       |  |
| Pa         | art 3-"Frequencies, Coding Formats,'       |
|            | ch 1994.                                   |
| Pa         | art 4 "From Bench To Programmer,"          |
| Apri       | 1 1994.                                    |
| Pa         | art 5-"The Receivers," May 1994.           |
| В          | ack issues printed within the past two     |
|            | s can be ordered for \$5 each, postpaid    |
|            | customer service at 800-441-0294. Is-      |
|            | printed more than two years ago and        |
|            | vidual article photocopies are unavailable |
|            | the publisher.                             |
| and a real | NAMES - PARTICIPATION                      |


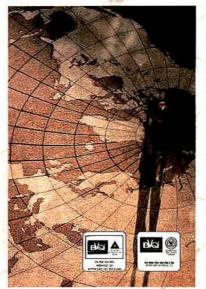
# We are at home in your world.


As a division of Radio Frequency Systems, Inc., Celwave offers the most complete selection of antenna system components; the strong engineering support; the integrity and the quality you can only expect from a leader. For paging, cellular, personal communications networks, dispatch and trunking, we are your global source for precisely manufactured products that assure total system performance.



Base station antennas. Duplexers. Filters. Cavity devices. Transmitter combiners. Receiver multicouplers. Bi-directional amplifiers. Advantage mobile antennas. Distributed antenna systems. Transmission line. Connectors and accessories. Celwave,

2 Ryan Road, Marlboro, NJ 07746-1899 In the U.S.: (800) 321-4700 • fax: (615) 641-1910 Outside U.S.: (908) 462-1880 • fax: (908) 431-8388



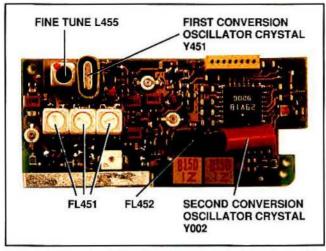

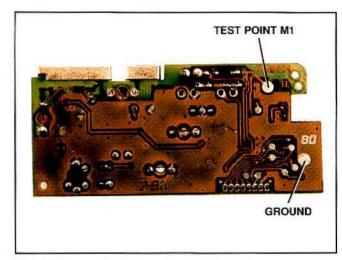


Photo 5. AARE series 406MHz–512MHz receiver circuit boards are virtually identical, with the exception of the tuning range. The AARE4001A board (pictured) covers 450MHz–465MHz and contains a 3-bay helical filter (FL451). Note that Y002 is the second conversion oscillator crystal. FL452 serves as a band-pass filter.

Photo 6. These are the M1 test point and ground locations on the AARE series 406MHz–512MHz receiver circuit boards.

contain a three-bay helical filter (FL451). (See Photo 5 above left.)

The AARE series pagers virtually are identical, with the exception of the tuning range. Further, note that Y002 is the second conversion oscillator crystal.

FL452 serves as a band-pass filter. Photo 6 above right shows the M1 test point and ground locations.

NRD (138MHz–174MHz) receivers As shown in Photo 7 on page 26, NRD series receiver circuit boards use a ferrite bar in the antenna circuit.

The first conversion oscillator crystal, Y001, is in the range of 40.00MHz to 65.3MHz, followed by a frequency multiplier. The second conversion oscillator



# **Remote Comparator Display**

The Smartswitch II<sup>™</sup> Remote Comparator Display monitors and controls voting receiver systems on a personal computer or console. It can be used locally or remotely with leased-line or dial-up modems.

Now you can get control of your voting system.



(513) 595-5900




Circle (20) on Fast Fact Card

22 Mobile Radio Technology May 1994

Visit us at UTC, Booth # 576.

Circle (19) on Fast Fact Card

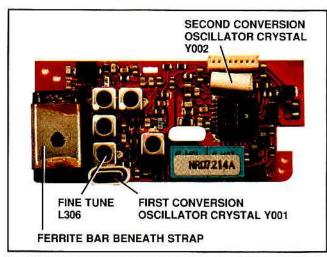

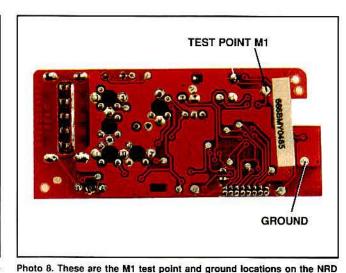


Photo 7. NRD series 138MHz-174MHz receiver circuit boards use a ferrite bar in the antenna circuit.

(Y002) is set either +455kHz or -455kHz from 17.9MHz. As mentioned earlier, this frequency choice affects the polarity of the decoded signal.

L305 varies the signal input from the multiplier into the first mixer. L306 tunes the crystal (Y001) to frequency. L302 and L303 adjust the RF pre-amplifier to resonance while L304 is broadly resonant at

17.9MHz. A future article describes these circuits in detail.

Photo 8 above right shows the M1 test point and ground locations.


Motorola, from the start, has designed the Bravo receivers around triple-conversion superhets. Although the costs and complications of this conversion scheme have their drawbacks, the unrivaled sensitivity and selectivity this circuit affords cannot be denied.

#### Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds, South Houston, TX, and co-workers Raymond, Tim and Pete, for their help with this project.

ー

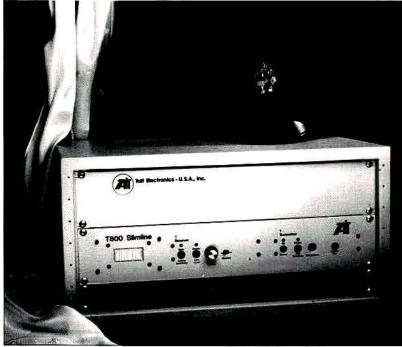Tait SMR repeaters: "Air Power" performance for less than \$2000!



Logic ready

series 138MHz-174MHz receiver circuit boards.

- 800 to 960 MHz; also UHF and VHF
- One to five watts, continuous duty
- Up to 128 frequencies
- Part 88 ready
- Two-year warranty

# Call now!

**Tait Electronics-U.S.A., Inc.** 1-800-222-1255 Fax: 713/468-6944

Tait repeater shown with optional cabinet, and Trident TNT-60 logic.



@1994 Tait Electronics-U.S.A., Inc. All rights reserved.

Circle (23) on Fast Fact Card

The journal of mobile communications technology

500

Mobile Radio

# Mobile cellular antennas, p. 10

booth

- Servicing pagers
- Rechargeable batteries
- Utility telemetry, SCADA
- 220MHz SMR systems
- Smith charts

June 1994/\$3

Radio coverage analysis

# Servicing pagers: Elegant simplicity

Part 6—Here are some details about the Bravo receiver circuitry. Surprisingly, the Bravo does not include one particular circuit that is common to most FM receivers. Alignment information is included.

# By David Ludvigson

In engineering terms, the Bravo receivers share *elegant simplicity*.

To manufacture a receiver with the fre-

quency stability, sensitivity, selectivity and features found on just the 930MHz Bravo—and to do it with only five transistors and a silicon chip—well, that (for me) defines *elegant simplicity*.

Let's take a look at the Bravo receivers,

starting with the NRF series (929MHz-932MHz).

Figure 1 below is a block diagram of one of the NRF series receivers.

Ludvigson is a technician in Houston.

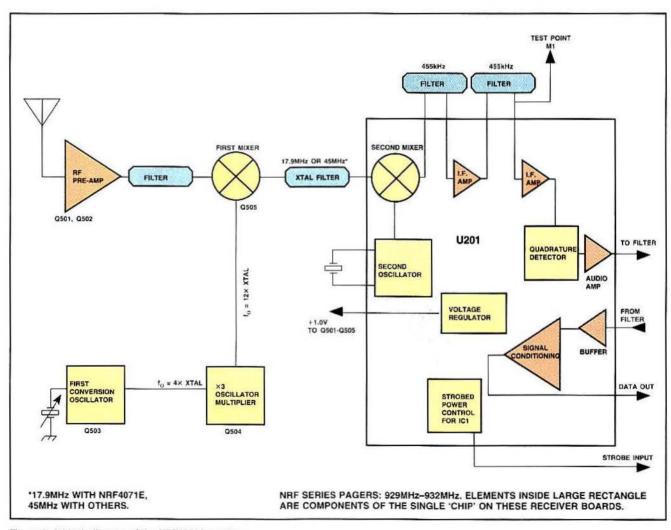


Figure 1. A block diagram of the NRF4071A receiver.

# Alignment procedure: Bravo NRF series (45MHz IF)

The following procedure deviates somewhat from the suggested Motorola technique and assumes the use of a shielded room (See Part 1) and the IFFER (See Part 2).

1. Set signal generator to exact frequency of receiver:  $F_{oper} = (12 \times 1 \text{ st conv.} \text{ xtal}) + 45 \text{MHz}.$ 

2. Frequency-modulate the signal with a 4.5kHz-deviated 1kHz tone.

3. Meter M1 using the IFFER and an oscilloscope.

4. Adjust L511 for a close approximation of a sine wave (as viewed on scope). This should be the first peak as L511 is adjusted clockwise as viewed from the foil side of the circuit board.

5. Trim C521 to slightly distort the sig-

(Additional detail is available from the schematic printed in the pager manual.) The antenna loop circuit (L501 and L502) is coupled via L503 and L504 into the emitter of Q501. C502 provides antenna

nal viewed in step 4. This adjustment affects the multiplier stage and causes "pulling" of the crystal oscillator.

6. Reduce the signal generator's output level. Adjust C521 (multiplier), C532 (45MHz filter response), C513 (930MHz bandpass filter input) and C502 (antenna trimmer)—in that order—to achieve maximum sensitivity.

7. Repeat step 6 as needed for maximum sensitivity. Output from the signal generator should read -90.2dBm ( $<7\mu$ V) for 1,200 baud POCSAG or -92.5dBm ( $<5.5\mu$ V) for 512 baud POCSAG. Measurements are signal generator output level readings applied through a 6dB attenuator to the RTL-1005 fixture.

tuning for the frequency of interest. Between the loop antenna and the emitter of Q501 is a matching network that effectively transforms the high-impedance antenna to about  $50\Omega$ . Q501 and Q502 provide roughly 12dB-15dB of signal gain.


Configured in *common base*, these transistors' input and output signals remain *in phase* with each other, making neutralization virtually unnecessary. Output from Q502 (L508, C512 and C513) is tuned to the input frequency, reducing adjacent channel signals and images by about 15dB.

Lightly coupled by C514, this stage easily matches the 50 $\Omega$  stripline filter (FL501).

FL501 is the "postage-stamp" near the first-conversion oscillator crystal on these boards. This dual-pole stripline filter has been pre-assembled and pre-tuned to provide image signal rejection at around 840MHz, while passing the 929MHz–932MHz antenna signal.

In the meantime, a signal is being generated at the first conversion oscillator. Q503 is a basic Colpitts oscillator operating from a nominal 73.8MHz crystal. The collector circuit of Q503 is roughly resonant at a frequency four times that of the original 73.8MHz, thus providing a frequency of 295.2MHz—along with the strong presence of 73MHz—to the base of Q504.

Between the collector of Q503 and the

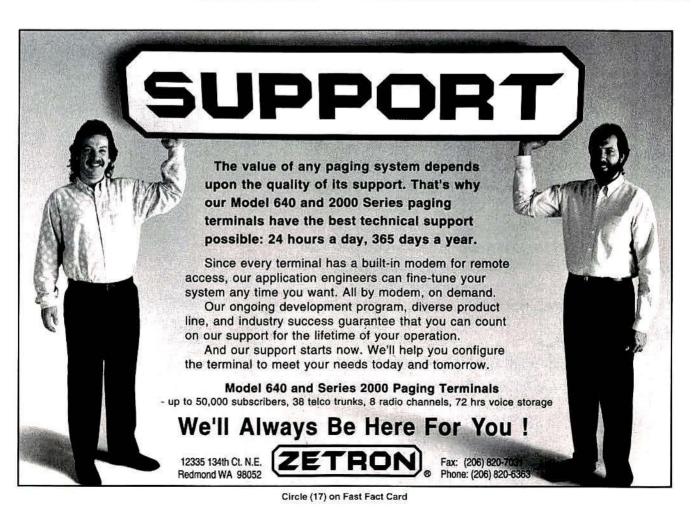

20

base of Q504 is a network (L514, C521 and C520) that is tuned to the 4th harmonic of 73.8MHz (295.2MHz). Having cleaned up the input, Q504 is used as a frequency tripler to provide an output of  $12 \times 73.8 = 885.6$ MHz.

Q504's collector is broadly tuned to 880MHz by the combination of C524 and L515. Note the use of resistor R508, though. This resistor lessens the effective "Q" of the tuned circuit, allowing a fair amount of multiplier bandwidth.

L516 and C526 may seem redundant, but actually they provide another filter that keeps the output signal sinusoidal. (Multiplier stages get messy around the edges of their transition from  $F_{ie}$  to  $F_{out}$ ).

So, at one end of the bandpass filter (FL501) there is an amplified off-the-air signal, and at the other end of the filter the first conversion oscillator signal is injected. Mixer Q505 helps to sort them out.

At the base of Q505 is a parallel resonant circuit (C529 and L517) that closely matches the frequency response of the bandpass filter FL501. It also provides image rejection by selectively reducing the first conversion oscillator signal and passing the antenna signal.

Q505 mixes the incoming antenna sig-

# Pager servicing series

Part 1: "Build a Shielded Room," January 1994.

Part 2: "Build An 'IFFER," February 1994.

Part 3: "Frequencies, Coding Formats," March 1994.

Part 4: "From Bench To Programmer," April 1994.

Part 5: "The Receivers," May 1994. Part 6: "Elegant Simplicity," June 1994.

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

nal at 930.6MHz with the signal frequency of the first conversion oscillator (at 885.6MHz) to provide an output of 45MHz.

The incoming FM signal should be deviated from 4kHz to 5kHz by the data



# ...Remote control, of upto 16 channels -Radius M200, GM300 & Maxtrac 300 series radios

The CPI model MCR210 remote and MCR series interface panel will allow you to remote control Radius or Maxtrac radios, upto sixteen channels, over any two wire voice grade circuit.

The MCR210 remote control system provides LED displays for remote channel indication, channel up and down buttons, PTT indicator, on-hook PTT capability, monitor button and indicator, intercom capability between parallel remotes and the radio, scan control button and indicator for those radios so equipped and speaker volume control.

#### Features

- Simple installation No soldering, cutting or crimping.
- Provides remote channel indication.
- Does not require B308 option.
- · Remote transmissions heard over radio speaker.
- Radio transmissions monitored on remote speaker
- Uses any two wire voice grade circuit.



1186 Commerce Drive • Richardson, TX 75081 (214) 437-5320 • FAX (214) 437-5360 • (800) 869-9128 stream. (Years ago, 5kHz deviation was the norm, but today the maximum deviation seems to vary.) As such, the second conversion mixer output should be able to pass at least  $\pm$ 5kHz from the center frequency. Bravo pagers' second conversion mixers pass signals with deviation from  $\pm$ 3.5kHz to  $\pm$ 5kHz, depending on the crystal filter's frequency.

The 45MHz intermediate signal then is mixed at the "crossed circle" located in IC U201. Onboard U201 is the "second oscillator," with C026 coupling either the 44.545MHz or 45.455MHz signal back to the second mixer.

Mixer output goes directly to a narrowbandwidth external 455kHz filter, back into the chip for amplification, and into another filter. The second filter's output is test point M1 and the input to a second IF amplifier.

Up to this point, old-timers will have noted something *strange* about the entire receiver. *There is no limiter circuitry in it*, nothing to prevent it from responding to an AM signal, a dead carrier or a single-sideband signal. In short, it "pays attention" to anything it hears.

It is only after the second 455kHz amplifier that the "whatever it hears" is demodulated by an active quadrature demodulator, and we have an actual FM receiver. Demodulator output is sent to lowpass filter and audio buffer stages, and subsequent RC filtering networks on the decoder board.

Once filtered, the audio signal is processed further by the peak and valley detectors, limited, and then returned to the decoder board as *data*.

Further refinements in U201 include a battery-check comparator with a I or 0 output at TP9, and a voltage regulator with IV output for all five transistors on the receiver board. The main current reference is toggled later by the battery saver signal, but it may be defeated by forward-biasing TP10 with a 10K resistor fed from TP4.

Elegantly simple, or simply elegant. A 930MHz receiver that fits in the palm of the hand, and is run by a 1.5V battery.

#### Acknowledgement

I would like to thank J.H. Kim, owner of JJ Sounds, South Houston, TX, and coworkers Raymond, Tim and Pete, for their help with this project.

锄

July 1994/\$3

# Jobile Rac Technolo

The journal of mobile communications technology

# Duplexers, p. 10

- Servicing pagers
- Rechargeable batteries
- Product/services showcase
- EMI/RFI solutions
- Working with the decibel

# Servicing pagers: Problems in paradise

Part 7—The hot sun is no friend of electronic equipment, and the Bravo pager is no exception. The 17.9kHz IF receiver board is the most susceptible to drift, especially in aftermarket cases. Here are some alignment tips.

### By David Ludvigson

As was mentioned in last month's installment, making a five-transistor, onechip radio receiver work reliably at 930MHz is quite a feat. When it comes to *paging* receivers, there is more to it than first meets the eye.

A side-by-side comparison of the NRF 4017A and NRF 4017E boards reveals many differences. (See photos 1 and 2 below.) The 45MHz IF "A" board has a gold-colored RF filter. The RF filter on the "E" board is slightly taller and silver-colored. The "E" board uses a 17.9MHz IF and has fewer components than the "A." There is also a glaring lack of "tech-tweakable" adjustments on the "E" boards; all that can be tuned is the antenna matching circuit (C552) and the oscillator frequency (L561).

Electronically, the two versions of this receiver are quite similar. The oscillator frequency first is quadrupled, then tripled, to provide an overall multiple of 12 times the crystal frequency. Although the 4017A and 4017B provide multiplier tuning, the 4017E does not have this feature. L564 and C570 are fixed-value components, generally resonant at around 304MHz.

Next, the 45MHz IF filter of the NRF 4017A is changed to 17.9MHz in the 4017E. This narrows the bandpass "window" for the incoming signal, making the oscillator tuning more critical.

After several months of working with the 4017E, I started noticing several customers having problems receiving their pages. In each case, they complained about a string of "Es" in their messages. (Displaying an E is the Bravo's way of reporting an error in data.) Every customer was using a pager with the NRE 4071 for a receiver. A few minutes spent aligning the oscillator was all that was required to bring back solid message reports.

### Pager servicing series

Part 1: "Build A Shielded Room," January 1994. (All pagers.) Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.) Part 3: "Frequencies, Coding Formats," March 1994. (Bravo.) Part 4: "From Bench To Programmer," April 1994. (Bravo.) Part 5: "The Receivers," May 1994. (Bravo.) Part 6: "Elegant Simplicity," June 1994. (Bravo.) Part 7: "Problems In Paradise," July 1994. (Bravo.) Back issues printed within the past two years can be ordered for \$5 each, postpaid.

years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

Of utmost importance in any receiver design is the stability of the local



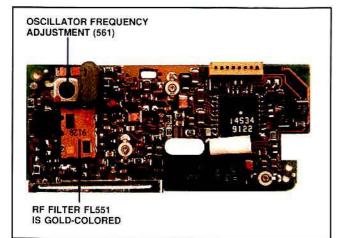


Photo 1. The NRF 4071C board closely resembles the NRF 4071A board referred to in the text. NRF 4071A, NRF 4071B and NRF 4071C boards have gold-colored RF filters (FL551) and a 45MHz IF.

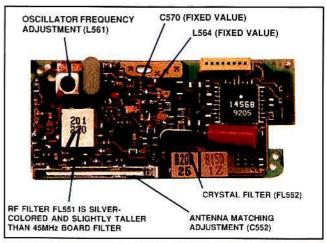


Photo 2. The NRF 4071E board has a 17.9MHz IF and a silver-colored RF filter (FL551) that is slightly taller than the filter on the A, B and C series boards.


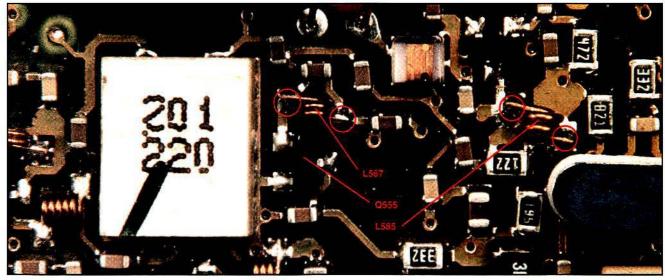


Photo 3. Poor performance of the NRF 4071E Q555 mixer stage often may be traced to poor soldering joints at either the base inductor (L567) or the collector inductor (L585).

oscillators and the bandpass characteristics of the IF. Should the oscillator drift beyond the bandpass window provided by the IF filter, the detected signal is going to be either above or below the range the decoder can handle. In short, the letter E will become common in displayed messages. Summer came, and outdoor temperatures rose higher and higher. Beach activity followed. Again the NRF 4071E began plaguing my bench. In some cases, the first conversion oscillator was off by as much as 22kHz to 49kHz, and always on the high side. In each case, the customer had replaced the original black pager case with a semi-transparent after-market unit.

Any first-year electronics student can

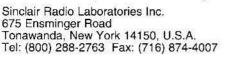





# Alignment procedure: Bravo NRF series (17.9MHz IF)

The following procedure deviates somewhat from the suggested Motorola technique and assumes the use of the shielded room (Part 1, January 1994 issue) and the IFFER (Part 2, February 1994 issue).

1. Set the signal generator to the exact frequency of receiver  $[(F_{oper} = (12 \times 1st \text{ conv. xtal}) + 17.9\text{MHz}]$ .

- 2. Frequency-modulate the signal with a 134Hz tope at 3kHz deviation
- a 134Hz tone at 3kHz deviation.

3. Meter M1 using the IFFER and an oscilloscope. (See photo A below.)

4. Adjust L561 for the maximum peakto-peak scope display with the 134.0Hz tone. (See photo B below.) This should be the first peak as L561 is adjusted clockwise as viewed from the foil side of the circuit board.

5. Reduce the signal generator's output level, and adjust C552 for maximum sensitivity.

1.561

6. Repeat steps 4 and 5 as necessary for maximum sensitivity and 134.0Hz reception. Output from the signal generator should read  $-90.2dBm (<7\mu V)$ for 1,200bps POCSAG and  $-92.5dBm (<5.5\mu V)$  for 512bps POCSAG. Measurements are signal generator output level readings applied through a 6dB attenuator to the RTL-1005 fixture.

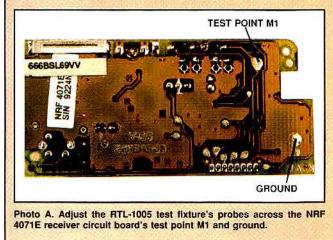



Photo B. These are the circuit adjustment locations for aligning the NRF 4071E receiver circuit board.

C552 (UNDERNEATH ANTENNA BAR)

tell you that temperature changes cause frequency drift. At 76MHz, a  $\times 12$  frequency multiplier converts a 4kHz oscillator drift to a 48kHz drift at the output. This drift is exacerbated further by users who clip their pastel pagers to the sun visors of their cars in 100°F+ temperatures.

What effect does high temperature have on that fixed-tuned  $\times 4$  multiplier stage? L564 and C570 are getting the heat treatment as well as the oscillator. These surface-mounted components have been chosen to resonate around 304MHz—under ordinary circumstances. As the temperature increases, the components expand slightly, decreasing the actual amount of capacitance of C570, while also decreasing the inductance of L564. In short, the



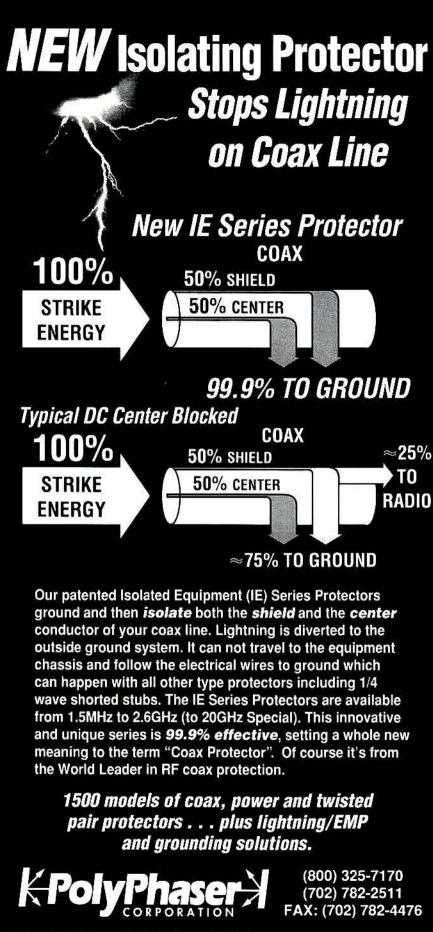

2225 Park Place 
P.O. Box 9000 
Minden, NV 89423-9000

LC combination is changing its resonant frequency upward as well. This decreases the drive signal level to Q554, the  $\times$ 3 frequency multiplier. Output from the overall  $\times$ 12 oscillator-multiplier chain suffers, and the receiver sensitivity falls off. As the frequency drifts, the RF signal at the collector of Q555 moves closer and closer to the edges of the passband of the crystal filter (FL552) until the window is essentially shut, and the pager no longer receives pages.

Receiver boards NRF 4017A and NRF 4017B also tend to drift as temperatures rise. To its credit, Motorola selected com-

Poor performance of the Q555 mixer stage often may be traced to poor soldering joints at either the base or collector inductors.

ponents with decent temperature coefficients to minimize this tendency. Furthermore, the  $\times 4$  multiplier tuned circuit is capable of being optimized—literally, tuned to resonance—by the use of a variable capacitor in the 4017A and 4017B series. As another feature of these boards, the 45MHz IF is generally broad enough to tolerate a wandering oscillator.


Other caveats on the NRF 4017E must include the problems encountered with some components. Poor performance of the Q555 mixer stage often may be traced to poor soldering joints at either the base or collector inductors. (See photo 3 on page 16.) It seems as though little time may have been spent tinning these inductors before assembly, because they are notoriously difficult to solder.

Tuning the first conversion oscillator is fast. A single turn of the L561 inductor brings the oscillator to frequency—and several kilohertz beyond—with only a fraction of a turn. There simply is too much inductance here, and adjustment of this coil is critical. The permeability of the core or the number of turns of the inductor needs to be changed. Whatever, it is too touchy for the east Texas climate.


锄

Circle (17) on Fast Fact Card

August 1994/\$3

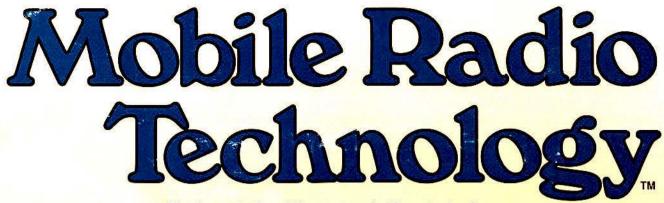

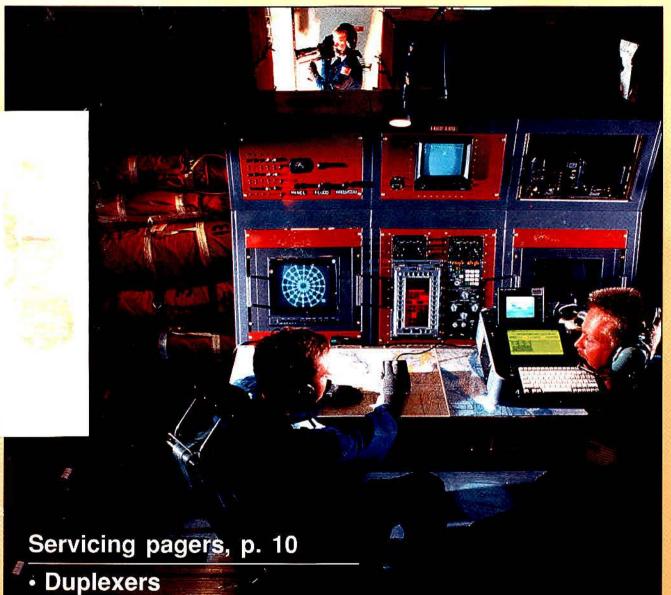The journal of mobile communications technology



- APCO preview/guide
- Automatic vehicle location
- Radio path profiles

## Servicing pagers: 406MHz–512MHz receivers

Part 8—Here are some details about the inner workings of UHF Bravo receiver circuitry. Alignment information that makes use of some special equipment and techniques is included.

#### By David Ludvigson

As outlined in Part 5, the Bravo pager has been well-equipped to handle the 450MHz spectrum. Let's take a closer look at the NRE and AARE 406MHz-512MHz receivers.

| FREQUENCY | MODEL NO.  |
|-----------|------------|
| 406 - 420 | NRE6421A,B |
| 450 - 465 | NRE6423A,B |
| 465 - 480 | NRE6424A,B |
| 480 - 495 | NRE6425A,B |
| 495 - 512 | NRE6426A,B |

The NRE series covers:

Figure I below is a block diagram of the NRE series receivers. (For additional detail, refer to the schematic diagram in the pager manual.)

An *outer loop antenna* is tuned by C402 and C403 to resonance at the operating

Ludvigson is a technician in Houston.

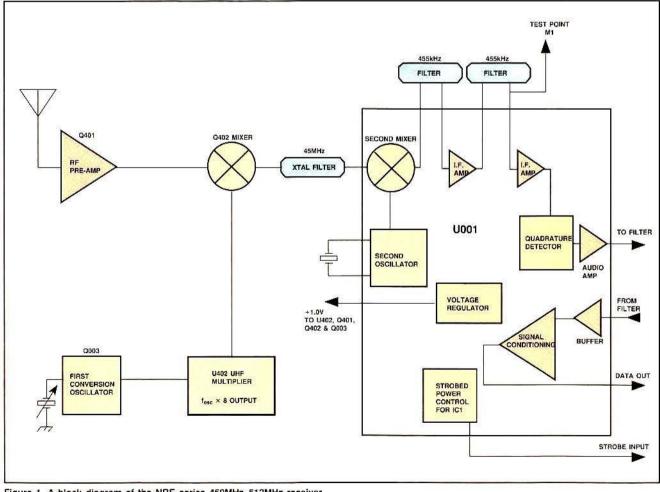


Figure 1. A block diagram of the NRE series 450MHz-512MHz receiver.

#### Alignment procedure: Bravo NRE series (45MHz IF)

The following procedure deviates somewhat from the suggested Motorola technique, and assumes the use of a shielded room (See Part 1) and the IFFER (See Part 2).

1. Set the signal generator to the exact frequency of receiver:  $F_{oper} = (8 \times 1st \text{ conv. crystal}) + 45MHz$ .

- 2. Frequency-modulate the signal with a 4.5kHz-deviated 1kHz tone.
- 3 Meter ML using the IEEED and
- 3. Meter M1 using the IFFER and an


oscilloscope.

4. Adjust L410 for close approximation of a sine wave (as viewed on scope). This should be the first peak as L410 is adjusted clockwise as viewed from the foil side of the circuit board.

5, Trim C441 to slightly distort the signal viewed in step 4. This adjustment affects the multiplier stage and causes "pulling" of the crystal oscillator.

6. Reduce the signal generator's output level. Adjust C441 (multiplier); L408 (45MHz filter response); C413 and C407 (antenna filter response); and C402 (antenna resonance)—in that order—to achieve maximum sensitivity.

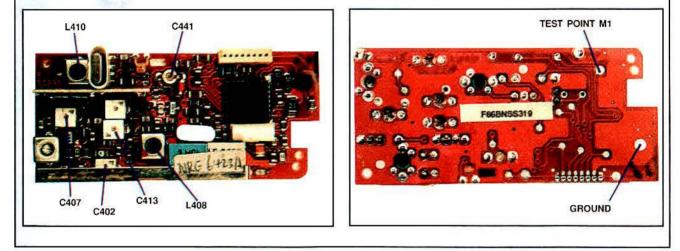7. Repeat step 6 as needed for maximum sensitivity. Output from signal generator should read  $-93dBm (5\mu V)$  for Golay or  $-90dBm (7\mu V)$  for POCSAG 1,200. Measurements are signal generator output level readings applied through a 6dB attenuator to the RTL-1005 fixture.



frequency. The *inner loop* transforms the incoming signal to a low impedance, matching the antenna to the RF pre-amplifier.

L403, R402, C404 and C405 provide negative feedback to Q401, stabilizing the common-emitter amplifier. Should the receiver be subjected to static discharges,



CR001 will forward-bias with a negative voltage and clamp the discharge to ground.

Output from Q401 is coupled via C406 to C408, C407 and L405, which combine to form one portion of the bandpass filter. The rest of the filter consists of C412, C410, C413 and L406. This two-port filter provides attenuation of unwanted signals amplified by Q401.

Meanwhile, Q003 operates as a Colpitts oscillator at about 51MHz. U402 contains a parallel resonant circuit tuned to the 4th harmonic, across pins 2 and 3. The U402 module amplifies the resulting 204MHz signal, and then doubles it to produce an output at 408MHz (*Note:* Some versions use a tripler, followed by a doubler, for an overall  $\times$ 6 multiplier stage.)

The resulting 408MHz signal from the first conversion oscillator is injected (along with the amplified antenna signal) at the base of Q402. The L409-and-C414 combination serves to bypass much of the 408MHz signal, while the antenna signal is virtually unaffected. Output from Q402, at 45MHz, may be adjusted by L408 to center the IF filter.

Once through the filter (FL401), the 45MHz signal mixes (at pin 12, U001) with the second oscillator signal at either

45.455MHz or 44.545MHz to produce a 455kHz output at U01, pin 13. External filters at 455kHz are matched with on-chip amplifier stages before being detected by the active quadrature demodulator.

As mentioned in Part 6, the signal at test point MI is not FM! Until the received signal is demodulated, the input may be anything from AM to a dead carrier. There are *no limiters* in the Bravo receivers.

#### **AARE** series receivers

Figure 2 below is a block diagram of the AARE series receivers. (For additional detail, refer to the schematic diagram in the pager manual.)

These receivers are identified easily as having a triple set of tuning adjustments for the RF pre-amplifier stage, and as lacking the frequency multiplying module found in the other 406MHz–512MHz receivers (NRE series).

To begin with, a loop antenna network (E401, C451) is matched via C452 and C453 to the base of Q451. Diode CR451 performs as a static discharge device to prevent damage to Q451.

Q451 and Q452 are configured as *common emitter/common base* or *cascode*. The need for neutralization has been minimized by use of R453 across the resonant circuit L452, C455 and C456.

The helical filter (FL451) is adjusted to pass the RF signal at the antenna. AARE4001 receivers tune from 450MHz to 465MHz, and AARE4002 series receivers tune from 465MHz to 480MHz. As such, these helical filters tune the receiver accordingly.

As an example, in an AARE4001, the first conversion oscillator Q454 is in a Colpitts circuit operating at 51.12MHz. Output from Q454 is tuned to the 4th harmonic (204.48MHz) with tuned circuit L458 and C471. This signal drives multiplier Q455 (a frequency doubler) across L460 and C477 at 408.96MHz. L460 and C477 provide post-multiplier filtering at 408.96MHz.

Mixer Q453 combines the signals coming through the filter (FL451) and the signal from the oscillator-multiplier chain.

#### Pager servicing series

Part 1: "Build a Shielded Room," January 1994. (All pagers.)

Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.) Part 3: "Frequencies, Coding Formats,"

March 1994. (Bravo.) Part 4: "From Bench To Programmer,"

April 1994. (Bravo.)


Part 5: "The Receivers," May 1994. (Bravo.)

Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems In Paradise," July 1994. (Bravo.)

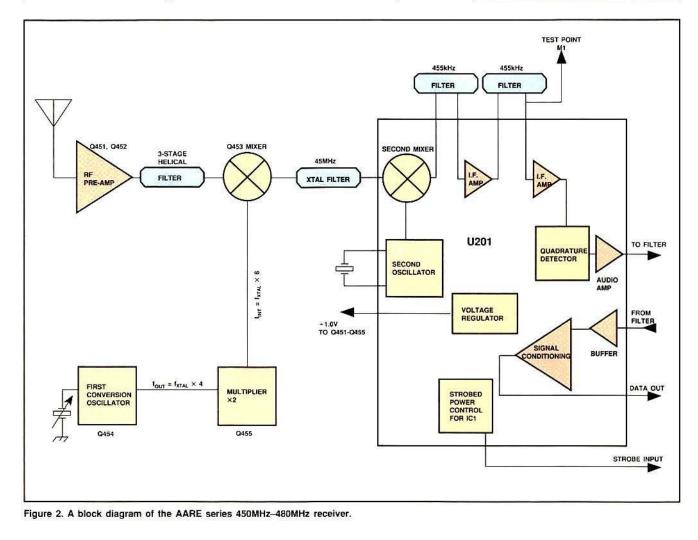Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.



#### Alignment procedure: Bravo AARE series (45MHz IF)

*Note:* FL451 has three sections. These will be noted as L1 (antenna side), L2 (intermediate section) and L3 (mixer side) in this procedure.

The following procedure deviates somewhat from the suggested Motorola technique and assumes the use of a shielded room (See Part 1) and the IFFER (See Part 2).

1. Set the signal generator to the exact frequency of the receiver ( $F_{oper} = (8 \times 1st \text{ conv. crystal}) + 45\text{MHz}$ .

2. Frequency-modulate the signal with

a 4.5kHz-deviated 1kHz tone.

3. Meter M1 using the IFFER and an oscilloscope.

4. Adjust L455 for a close approximation of a sine wave (as viewed on scope). This should be the first peak as L455 is adjusted clockwise as viewed from the foil side of the circuit board.

5. Trim C471 to slightly distort the signal viewed in step 4. This adjustment affects the multiplier stage and causes "pulling" of the crystal oscillator.

6. Reduce the signal generator's output level. Adjust C471 (multiplier), C463

(45MHz filter response), L3 (mixer side), L2 (intermediate), L1 (antenna side), C455 (RF preamp output) and C451 (antenna)—in that order—to achieve maximum sensitivity.

7. Repeat step 6 as needed for maximum sensitivity. Output from the signal generator should read -93dBm (5 $\mu$ V) for Golay or -90dBm (7 $\mu$ V) for POCSAG 1,200. Measurements are signal generator output level readings applied through a 6dB attenuator to the RTL-1005 fixture.

mixer operation because antenna-side sig-

nal level and local oscillator injection levels determine both sensitivity and selectiv-

The 45MHz output from Q453 is filtered by FL452, and then sent to the U001 "second mixer," along with the signal from the internal crystal oscillator (at either 45.435MHz or 44.545MHz). The resulting 455kHz signal then is filtered, amplified, filtered and amplified before it reaches the

quadrature detector. Further processing of the signal delivers audio to TP8. External

filters (on the decoder board) route back to the Data Fil I/P (TP10) where the retrieved

audio is converted into a data stream and

I would like to thank J.H. Kim, owner of JJ

Sounds, South Houston, TX, and co-workers


Raymond, Tim and Pete, for their help with this

ity of the receiver.

subsequently decoded.

Acknowledgement

project.

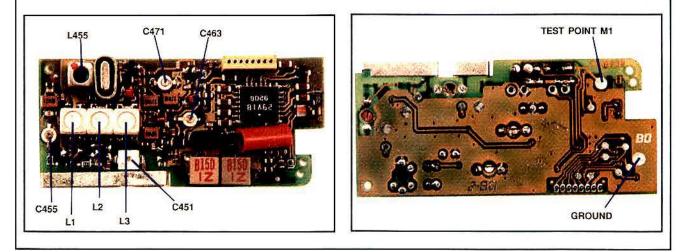

The filter composed of C459, C460 and L453 effectively reduces the oscillator-

side signal while allowing the antenna signal to pass. These values may be critical to



Circle (13) on Fast Fact Card

御

September 1994/\$3

# Mobile Radio Technology

The journal of mobile communications technology

Frequency hopping, p. 10

- Servicing pagers
- Duplexers
- Digital signal processing
- Radio range

## Servicing pagers: 150MHz receivers

Part 9—Here are some details about the inner workings of VHF Bravo receiver circuitry. Tips are included for changing pager frequencies for alignment purposes and other applications.

#### By David Ludvigson

NRD receiver boards cover:

| То     | this  | poin    | t we   | have    | disc   | ussee  |
|--------|-------|---------|--------|---------|--------|--------|
| Motor  | ola   | Bravo   | receiv | ver boa | rds 1  | or the |
| 929M   | Hz-9  | 32MH    | z and  | 406MH   | 1z-51  | 2MHz   |
| freque | ncy   | ranges  |        |         |        |        |
| The    | folle | owing i | nform  | ation a | oplies | to the |


NRD7211–NRD7217 150MHz receivers that cover 138MHz–174MHz.

| FREQUENCY<br>RANGE (MHz) | MODEL NO.  |  |
|--------------------------|------------|--|
| 138 - 143                | NRD7211A,B |  |
| 143 - 148.6              | NRD7212A,B |  |
| 148.6 - 152              | NRD7213A,B |  |
| 152 - 159                | NRD7214A,B |  |
| 159 - 164                | NRD7215A,B |  |
| 164 - 169                | NRD7216A,B |  |
| 169 - 174                | NRD7217A,B |  |


This particular series of boards is a mixed bag of tricks.

Figure 1 below is a block diagram of the NRD series receivers. (For additional detail, refer to the schematic diagram in the pager manual.) The first IF is 17.9MHz, and the second conversion oscillator may be either 17.445MHz or 18.355MHz, To

Ludvigson is a technician in Houston.

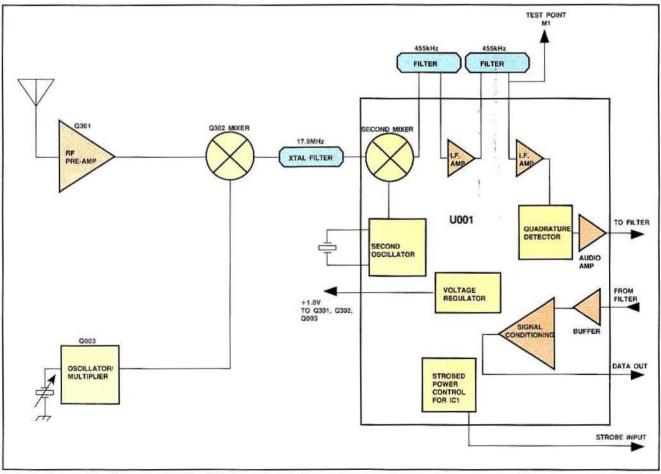

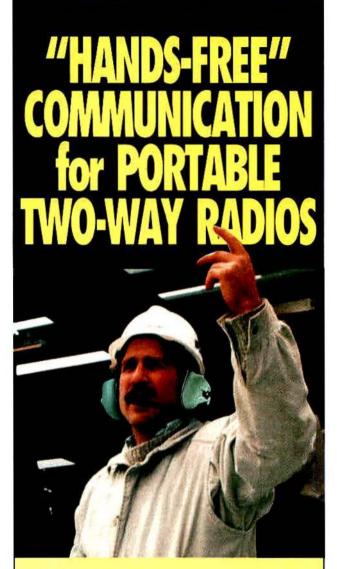A block diagram of the NRD series 138MHz-174MHz receiver. See text for oscillator/multiplier details.



Hands-free operation of portable two-way radios is now possible with David Clark Company's Voice-Activated (VOX) Headsets. New miniaturized circuitry fits inside the headset ear cup, eliminating the need for a separate bulky VOX module.

With a Noise Reduction Rating of 24, these Voice-Activated Headsets with noise-canceling microphones, assure clear, crisp transmissions regardless of the background noise.

Choice of boom microphone headset or throat microphone headset.

No radio modification required.

For more information and a FREE DEMONSTRATION, call or write:

David Clark company INCORPORATED

360 Franklin Street, Box 15054, Worcester, MA 01615-0054 TEL: (508)751-5800; FAX: (508)753-5827; TELEX: 920482 ©1991 David Clark Company Inc.

a David Clark Company Inc.

Circle (16) on Fast Fact Card

#### Alignment procedure: Bravo NRD series (17.9MHz IF)

The following procedure deviates somewhat from the suggested Motorola technique, and assumes the use of a shielded room (See Part 1) and the IFFER (See Part 2).

1. Set the signal generator to the exact frequency of the receiver. See text for a discussion of how to determine the receiver frequency.

2. Frequency-modulate the signal with a 4.5kHz-deviated lkHz tone.


3. Meter M1 using the IFFER and an oscilloscope.


4. Adjust L306 for a close approximation of a sine wave (as viewed on scope). This should be the first peak as L306 is advanced clockwise into the core as viewed from the foil side of the circuit board.

5. Trim L305 to slightly distort the signal viewed in step 4. This adjustment affects the multiplier stage and causes "pulling" of the crystal oscillator.

6. Reduce the signal generator's output level. Adjust L305 (multiplier), C301F (antenna), L302 (RF preamp output), L303 (RF preamp filter) and L304 (17.9MHz filter response)—in that order—to achieve maximum sensitivity.

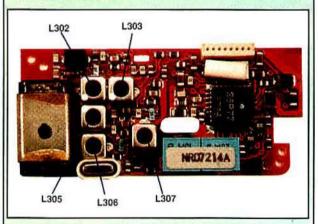7. Repeat step 6 as needed for maximum sensitivity. Output from signal generator should read -88.8dBm (7µV) or less for Golay and POCSAG 512. For POCSAG 1,200, the output should read -86.5dBm (10.9µV) or better. Output level is measured at the input to the 6dB attenuator at the RTL-1005 fixture.



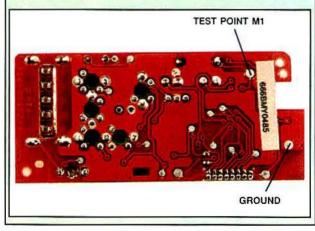

keep the second conversion oscillator's multiple harmonics out of the bandpass of other tuned circuits, 18.355MHz is used as the second conversion oscillator frequency for some receiver frequencies.

Conversely, to keep the second conversion oscillator's multiple harmonics out of the bandpass of the same tuned circuits, 17.445MHz is used as the second conversion oscillator frequency for other receiver frequencies. A chart is included to sort them out.

Next, the first conversion oscillator multiplier stage is either a doubler or tripler, again depending on the receiver operating frequency. The 138MHz-148.599MHz receiver boards (NRD7211A,B and NRD7212A,B) use a frequency *doubler* after the first conversion oscillator. NRD7213 through NRD7217 use a frequency *tripler* after the first conversion oscillator.

A receiver board missing the identifying sticker is no big problem. After having determined that it operates in the 138MHz-174MHz range, look at the first conversion oscillator crystal. If its frequency is between 60.8MHz and 65.32MHz, the oscillator is followed by a doubler stage. If the crystal frequency is between 43.6MHz and 52.03MHz, the oscillator is followed by a tripler stage.

The second conversion oscillator crystal (the smallest crystal on the board) is supposed to be color-coded, either yellow or green. Yellow indicates a frequency of

#### Pager servicing series

Part 1: "Build a Shielded Room." January 1994. (All pagers.)

- Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 3: "Frequencies, Coding Formats," March 1994, (Bravo.)
- Part 4: "From Bench To Programmer," April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.)
- Part 6: "Elegant Simplicity," June 1994. (Bravo.)
- Part 7: "Problems In Paradise," July 1994. (Bravo.)
- Part 8: "406MHz-512MHz Receivers," August 1994, (Bravo.)
- Part 9: "150MHz Receivers," September 1994. (Bravo.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

#### 'Leftovers'

The NRF series (929MHz–932MHz) pagers includes the 4017E, which has a 17.9MHz IF and a first conversion oscillator operating around 76MHz.

Use the following equation to calculate the frequency for these pagers:

$$F_{oper} = (12 \times 1st \text{ conv. crystal}) + 17.9 \text{MHz}$$

Although I have not tried it, modifying these units to operate on other frequencies probably would be easy. Converting the first conversion oscillator into a variable crystal oscillator would require replacing the fine-tuning inductor with an external permeability-tuned inductance. Although the range of frequencies that could be tuned in this manner might be relatively small, a bank of crystals might be switched in and out of the circuit. M1 provides a starting point for an AM detector stage, and any old LM386 will provide adequate output to feed a small speaker (when powered by a 3V– 6V supply). Tap into TP6 for demodulated FM.

Here is another idea. If your facility is set up to make changing pager frequencies easy, it might be helpful to offset the first conversion oscillator to a quiet frequency before starting the alignment procedure. If the purchase of a screen room or the construction of a doit-yourself shielded room as described in Part 1 is out of the question, shifting the frequencies of both the receiver module and the signal generator to a relatively quiet frequency would help with the alignment procedures.

In short, the Bravo receivers might just find other applications than simply beeping!

17.445MHz and means that data inversion is *not* required. Green indicates a frequency of 18.355MHz and means that data inversion *is* required. Selecting inversion is part of the programming function (DI = Y/N under Functions).

Now that we have waded the muddled waters, let's look at the block diagram.

The antenna assembly consists of a single band of metal surrounding a ferrite bar, a variable capacitor and several fixed capacitors forming a parallel resonant circuit at the operating frequency. C303 couples the antenna signal to the *diode clamped* RF preamplifier, Q301.

A neutralizing circuit, consisting of C304 and C305, helps to stabilize the common emitter circuit. The tuned circuit formed by L302 and C306 is tuned to the operating frequency. L303 and C309 provide impedance matching to the mixer, Q302, while providing image rejection.

C310 serves as a dc isolation capacitor and has negligible bearing on the tuned circuits.

A Colpitts crystal oscillator (Q003) feeds either a tripler or doubler (depending on the board; see above) tank circuit, L305 and C317. Fine-tuning of the crystal frequency is accomplished by L306.

Mixer output at 17.9MHz is applied to the crystal filter (FL301) and routed to the second mixer in U001. The internal second oscillator operates at either 17.445MHz or 18.355MHz (see above) and mixes with the 17.9MHz first IF to develop the 455kHz second IF. Further filtering and amplification of the 455kHz signal is then FM-demodulated by the U001's *quadrature detector*.

Passed through an external RC filter (on the decoder board), the audio is converted into a data stream by peak-and-valley detectors, limited, and sent back to the decoder board for translation.


As with all the receiver boards discussed so far, this one may be turned into a fulltime receiver by connecting a 10K resistor between TP10 and TP12, defeating the strobed *battery saver signal* generated by the decoder board.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds & Communications, South Houston, TX, for their help with this project. Tel: 713-944-1813.

锄



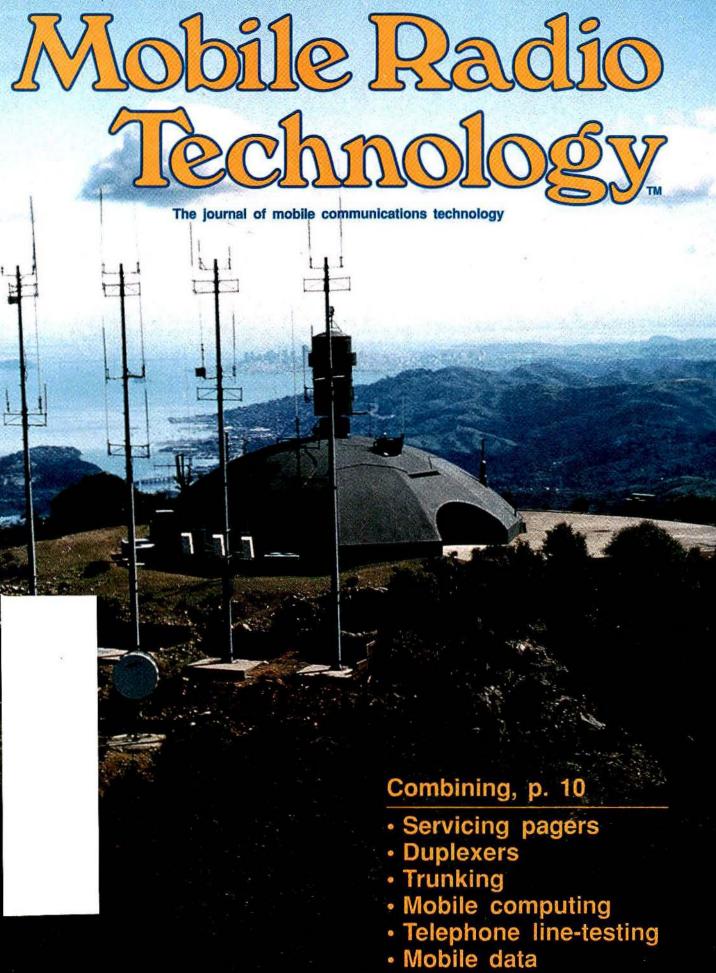

## Servicing pagers: Tales crystal filters tell . . .

Part 10—Tuning Bravo pager crystal filters to the high side of the first injection oscillator frequency results in proper operation. Here's why, plus some tips for making and verifying the adjustment.

#### By David Ludvigson

Crystal filters long have been used to reduce a received signal's bandwidth. As a rule, filters usually are adjusted to approximate a rectangular passband characteristic at the receiver's intermediate frequency to restrict detection to only that portion of the signal containing the desired intelligence.

Perhaps the best demonstration is the tuning of an AM broadcast radio with an analog dial. With the receiver tuned to the low side of the carrier frequency, a decent audio signal is heard. As the radio is tuned upward in frequency, a point is reached at which the fidelity of the recovered audio drops off. This point is the carrier frequency. The carrier does not contain any

Ludvigson is a technician in Houston.


audio information. Continuing to tune upward, once again a point of maximum fidelity is reached. This effect is especially noticeable if a narrow IF filter is used in the circuit ahead of the detector and amplifier.

An FM receiver's bandwidth (and the recovered information) may be restricted by use of an IF filter, with similar effects.

When placed in the path of a low-level signal, a properly terminated crystal filter passes only the fundamental frequency and a small portion of frequencies on either side of the fundamental. Depending on the construction and type of crystal geometry used to cut it, a crystal's bandwidth usually falls between 0.02% and 0.05% of the crystal frequency.

Several crystals of the same frequency may be configured to provide a narrower bandpass, but for the sake of discussion, we will limit the options to the 0.02% fig-

 17.9MHz IF 45MHz IF 3.58kHz BANDPASS 9kHz BANDPASS 9kHz BANDPASS -5kHz CARRIER FREQUENCY



ures with respect to the Bravo receivers.

#### The mathematics

 $F_{xtal} \times 0.02\%$  = bandwidth 17.9MHz × 0.02% = 3,580Hz 45.0MHz × 0.02% = 9,000Hz

These figures determine the "window" or bandwidth available through the associated 17.9MHz IF and 45.0MHz IF filters and agree quite closely with measured performance of the Bravo IF filters.

The signal radiated from paging transmitters is symmetrical. (See Figure 1 to the left.) On either side of the carrier frequency, the same intelligence is transmitted. "Normal" POCSAG is normal on both sides of the center frequency; "inverted" POCSAG remains inverted on both sides.

The crystal filter imposes a bandwidth factor that allows the quadrature detector to "see" that portion of the signal to which it has been tuned. This bandwidth factor may be adjusted by means of the first injection oscillator.

With a 9kHz window, the 45MHz IF boards are the easiest to tune, and they maintain their tuning for quite a long time. The narrower 3.58kHz window of the 17.9MHz IF filter is more critical of adjustment, and oscillator frequency drift causes reception of erroneous messages. Recalling that the maximum rate of data is 2,400bps and that the POCSAG signal preamble calls for a large portion of the overall "batch" to contain the "alternate 1 and 0" sequence, we are left with an IF window that must pass 2,400Hz to be of any value.

Next, consider the FM detector. Regardless of its design, an FM demodulator responds with an output voltage polarity determined by whether an input signal is higher or lower than the center frequency.

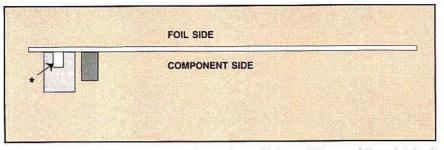


Figure 2. A side view of the Bravo receiver board. Start with the oscillator core fully up (at circuit board level) when adjusting it to frequency.

In short, careful adjustment of the first injection oscillator frequency might result in failure to decode a received message! Placing the Bravo pagers (all of them) on the high side of the first injection oscillator frequency results in proper operation. This fact means that the core of the oscillator coil should be set to the first peak as you adjust the core from the circuit board plane to the top of the coil form. (See Figure 2 above.)

Further advancing the core (downward, as viewed by the operator) causes the IF window to move lower in frequency, toward the carrier frequency, and if advanced further, toward the "unwanted side" of the FM signal.

When testing my tuning, I usually use a 134Hz tone that modulates the signal generator to 3.5kHz deviation. Using the IFFER, I can quickly determine proper tuning by noting symmetrical response above and below the oscilloscope's horizontal line. (See Part 2: "Build An 'IFFER,'" February 1994 issue.) At 134Hz, I am testing the low-frequency response of my filter, and by setting it symmetrically, I am moving the bandpass completely off the "unwanted" side. Audible output from the IFFER also reveals a more resonant response to the 134Hz signal when tuned in this fashion. 和

| Pager serv | icing seri | les |
|------------|------------|-----|
|------------|------------|-----|

- Part 1: "Build a Shielded Room," January 1994. (All pagers.)
- Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.) Part 3: "Frequencies, Coding Formats,
- March 1994. (Bravo.) Part 4: "From Bench To Programmer,"
- April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.)
- Part 6: "Elegant Simplicity," June 1994. (Bravo.)
- Part 7: "Problems In Paradise," July 1994. (Bravo.)
- Part 8: "406MHz-512MHz Receivers," August 1994, (Bravo.)
- Part 9: "150MHz Receivers," September 1994. (Bravo.)
- Part 10: "Tales Crystal Filters Tell . . .," October 1994. (Bravo.)
- Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

 Save the save you time and money with our fast shipping and competitive pricing. Tune into a dependable distributor who provides quality products and services designed to meet your own tough standards. Call a Hutton representative today for help with your next order. You'll be glad you did!

 Image: Comparison of the standards of the standards of the standards of the standards.

 Image: Comparison of the standards of the standards of the standards of the standards.

 Image: Comparison of the standards of the standards of the standards.


 Image: Comparison of the standards of

Comm.works Denver, Colorado 303-820-2929 FAX 820-2809 800-726-6245


Comm.Works NW Seattle,Washington 206-453-2132 FAX 453-1558 800-426-2964



November 1994/\$3

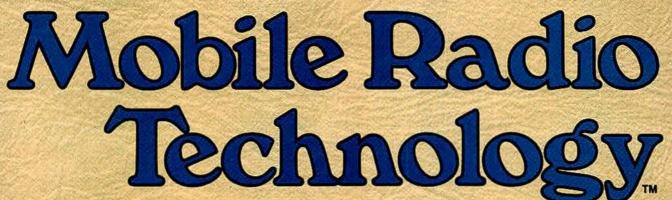

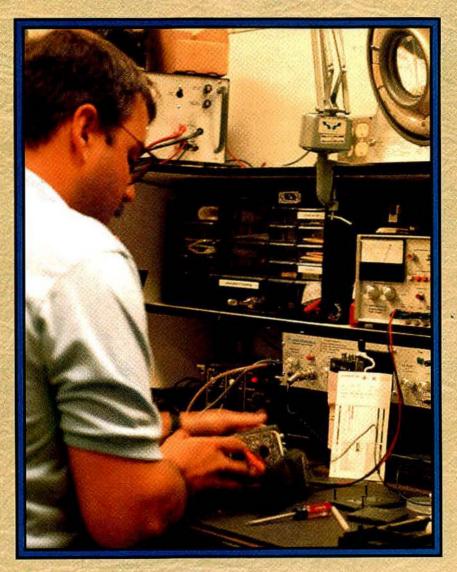The journal of mobile communications technology



### Duplexers, p. 10

- Antenna testing
- Servicing pagers
- RF power amplifiers
- Installation guidelines
- New Part 22 rules

An INTERTEC® Publication

## Servicing pagers: Microprocessor board

Part 11—Here's how the versatile Bravo pager microprocessor board performs its tasks in shifting the pager from standby to receive, verifying address reception and displaying messages from electronic memory.

#### By David Ludvigson

To this point, we have discussed the various receiver boards for the Motorola Bravo pager. Now we will take a closer look at just how the decoder board operates.

Motorola has made use of "dedicated" microprocessors to handle the decoding functions found in the Bravo. A list printed in Part 3 (March 1994 issue) identifies which chips handle Golay, POCSAG 512 and POCSAG 1,200. Although the formats may differ, programming each subset of chips uses the same microprocessor.

The most obvious difference to the technician is found in the values of RC filters (R101/R201, R102/R202/R302, C101/ C201/C301, and C104/C204/C304) and the *clock* speed (Y101, Y201, and Y301). The RC filter values have been chosen to optimize the frequency response at *rec*, *audio* (pin 4, J001). The *peak* and *valley* detectors (on the receiver board) detect the level transitions of the audio signal and apply it to the *limiter*. The resulting output is a stream of rectangular pulses.

□ NRN5155A-2 and NRN5156A-2 decoder boards:

Numerous revisions have occurred with the decoder boards.

The NRN5155A-2 and NRN5156A-2 are capable of Golay and POCSAG 512 operation only, and use the 5105860Q01 or 510586Q04 microprocessors ('Q01 or 'Q04 in these discussions). Should you ever find a 'Q02 or a 'Q20 for a microprocessor (1 never have), these processors serve as a POCSAG 512 chip when installed in these boards.

□ NRN5155A-4, NRN5156A-4, NRN7459A, NRN7463A, and NRN7549A decoder boards:

Ludvigson is a technician in Houston.

We will be discussing this series of decoder boards at length.

They are capable of operating Golay. POCSAG 512 and POCSAG 1,200 formats, with the previously noted modifications to the board (i.e., RC filter, clock speed and microprocessor). Our discussion will cover the three basic modes in which this board operates: the "Wake-up!" mode, the "I'm looking for it!" mode and the "Look what I found!" mode.

#### The 'Wake up!' mode

Placing a battery in the Bravo and switching it to "on" is just the beginning of its day. (See Figure 1 on page 24, or see Motorola manual 68P81006B85-C, page 15, for more detail.)

Switch S001 is shown in its *full up* (beep) position. B+ (from the nominal 1.5 volt battery) is applied to pin 2 of the switch, one side of L001 and the emitters of Q001-Q004. Power for the *support-interface* chip (U001) is provided through pin 21.

At the far side of L001 is a voltage multiplier that produces 3.2Vdc. This boosted dc is applied to pin 48 of U102 and pin 13 of the codeplug (U004) for operating voltage.

Pin 10 of U001 is fed a *high* voltage by means of the slide switch. This *flag* informs the chip that we expect it to *beep*. If this *high* is missing, the pager will go into the *vibrate* mode.

With the signal output devices having been determined and with the chips having been provided with the required operating voltages, the crystal oscillator (Y001 and associated circuitry) is enabled. The *reset* line (pin 2, U102) is held low until C006 charges. This momentary *low* forces the CPU (U102) and the codeplug (U004) to restart to its lowest address and begin execution of the program stored in the *6K* BYTE ROM. From ROM, the program begins.

The oscillator/timer counter advances by increments, starting the process of reading information stored in the codeplug. Line A0 (pin 11, U102) is tested. If it is *high*, peripheral interface adapter (PIA) *Port C* controls the flow of information *out* of the codeplug (U004) into PIA *Port A*. PIA Port A strobes the codeplug via A0 (pin 11, U102), reading the stored data via the I/O (pin 10, U102) into A1. These data contain the capcode and the options programmed into the codeplug. This information is stored in internal RAM.

If, for any reason, the program fails to execute properly, the *deadman timer* performs a *reset*. This failure is detected when a *low* is sensed on pin 11 of U102 and

#### Pager servicing series

Part 1: "Build a shielded room," January 1994.(All pagers.)

- Part 2: "Build an 'IFFER'", February 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 3: "Frequencies, coding formats, March 1994. (Bravo.)
- Part 4: "From bench to programmer," April 1994. (Bravo.)
- Part 5: "The receivers," May 1994. (Bravo.) Part 6: "Elegant simplicity," June 1994. (Bravo.)
- Part 7: "Problems in paradise," July 1994. (Bravo.)
- Part 8: "406MHz-512MHz receivers," August 1994. (Bravo.)
- Part 9: "150MHz receivers," September 1994. (Bravo.)

Part 10: "Tales crystal filters tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor board," November 1994. (Bravo.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

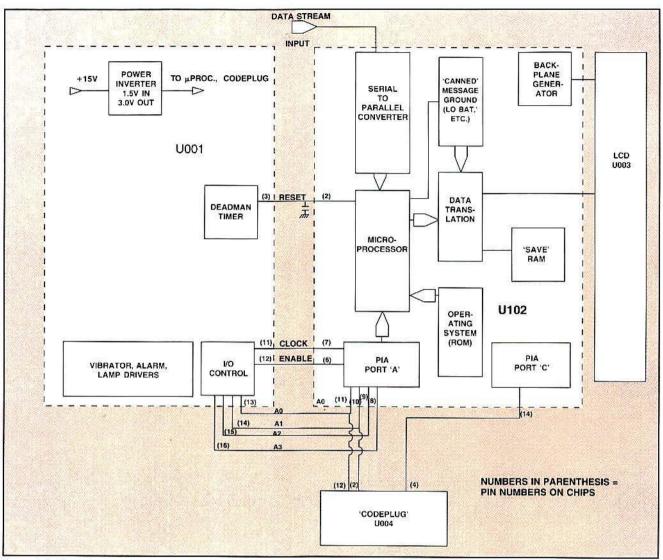


Figure 1. A block diagram of the Bravo decoder boards.

## For Worry-Free Communication, It Pays To Be Well Connected.

#### New LMR<sup>™</sup> 500 Low-Loss, Low-Cost, Flexible Communications Cable Gives You:

- Loss of 3.13 dB/100 feet at 900 MHz.
- Greater than 90 dB RF shielding.
- Weather resistant polyethylene jacket.
- Minimum bending radius of 1".
- \$0.90 per foot.

Times Microwave Systems LMR Cables and Connectors... A Better Connection.

Circle (21) on Fast Fact Card

IMES

MICROWAVE SYSTEMS

PO. Box 5039, Wallingford, CT 06492 (203) 949-8400 • (800) TMS-COAX FAX: (203) 949-8423

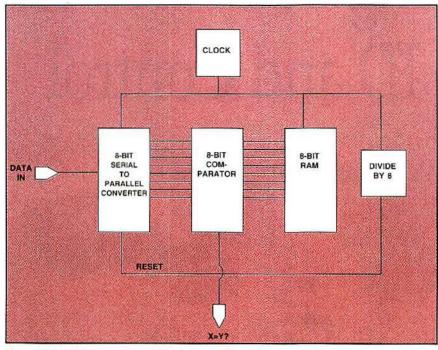


Figure 2. A block diagram of one method of comparing serial data. The Bravo uses a similar method of comparing 18 bits while looking for the capcode. It takes 32 bits to identify the proper pager, to determine the source and to perform parity checks at a rate of 512bps or 1,200bps for POCSAG. Assuming everything matches (X = Y), the alarm sounds and the following 32 bits are decoded as a message to be seen on the liquid crystal display.

generates a *warm reset* of the operation outlined to this point.

A warm reset is performed without any external signaling and will be unnoticed by the user unless the pager fails to either beep or buzz when turned on.

Once data from the codeplug have been transferred to RAM, the Bravo begins to beep, flash, enable the display generator (BP1–BP4) and provide a broken horizontal bar to the display.

#### 'I'm looking for it!': format, results

Motorola has prominently displayed copyright notices throughout its literature to deter the unauthorized use of its techniques by competitors. We can, nevertheless, make an educated guess as to the coding structure, and here we concentrate on the POCSAG format.

The POCSAG format (regardless of speed) consists of a *preamble* and one or two *batches* of codewords. A 32-bit *frame* sync code precedes the *frame/codeword*. Each *batch* transmits signals to a maximum of eight pagers (16 for double-batch). Each *frame* contains a pager number and a message, with a total of eight *frames* (one for double-batch) being sent in a single *batch*. If the *batch* is occupied in only




frames 1, 3 and 5, an *idle codeword* occupies frames 2, 4, 6, 7 and 8 (plus frames 9-16 for double-batch).

First, the *preamble* is 576 bits of alternating "10101...". The decoder in the Bravo uses this preamble to determine whether it is "hearing" POCSAG signals, and it determines synchronization with the transmitted signal. Note that if the *preamble* is transmitted at 1,200 baud, a 512baud Bravo on the same frequency would "hear" a continuous string of either 1s or Os.

Similarly, a 512-baud signal would produce an alternating "11001100" in a 1,200baud Bravo on the same frequency. Such invalid code response is what allows several formats to share a single frequency.

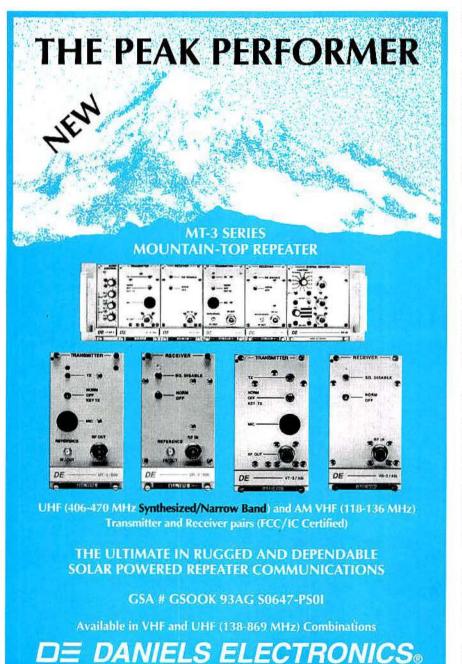Next, the *batch*. Within each batch are eight (or 16) *frames*. Each *frame* is 64 bits long. The first 32 bits are the capcode programmed into the Bravo. The follow-



43 Erie Street, Victoria, B.C., Canada V8V 1P8 Phone: 1-604-382-8268 Fax: 1-604-382-6139 (Canada) Phone: 1-206-671-8046 Fax: 1-206-738-2230 (U.S.A.)

Circle (25) on Fast Fact Card

ing 32 bits contain the calling party's phone number or message.

*Frame synchronization* is a unique 32-bit code (011111001101001000010 10111011000) that signals the beginning of each *batch*. The Bravo receiver board is activated each time this *frame sync* code is transmitted.

Within the Bravo codeplug, three bits have been programmed (by the capcode) to identify which *frame* in each *batch* is its own. (A double-batch pager would have four bits to identify which of 16 *frames* is its own). As the *batch* is sent, the Bravo turns on the receiver board only at the time its *frame* is being sent.

Up to this point, the information stored in RAM has been sitting there. Now, a comparison is made between the capcode information and the incoming data stream. (See Figure 2 on page 26.) If a match is found, the Bravo either beeps or vibrates. Further incoming data are then stored in RAM for display. This is the calling party's phone number or other information. Failing to match the capcode results in going back to looking for the *preamble*.

All this takes some split-second timing and a lot of coordination.

#### Meanwhile, back at the programmer...

From the preceding information, we can learn much about the programming of Bravo pagers.

When turned on, the Bravo Programmer asks, GSC or POCSAG? Your response to this question sets a bit in the Bravo that determines the *preamble* format. With POCSAG, the *preamble* consists of 576 alternating 1s and 0s. Golay has 14 alternating 1s and 0s sent at a rate of 600bps.

Next, the Bravo Programmer requests JRB/C or BAB. The JRB/C is used for twoboard Bravos, one receiver and one decoder board. The BAB is used for singleboard Bravo receivers not discussed in this series, JRB/C will place the POCSAG or Golay format in normal. BAB will place the format in inverted. These formats require the proper signal injection frequency in the receiver boards, "Normal" POCSAG or Golay usually is transmitted by paging systems. Most often, it is the receiver that is "inverted."

Selection of an *inverted* format also sets a bit to signal the need to *logically AND* the incoming data stream with a *1*. This step produces a reversed image of the incoming signal (e.g., 10010 transmitted becomes 01101 received).

The capcode comes next. Hidden within the POCSAG capcode is the *frame* number it is assigned. Let's see where a capcode of 1034067 would be *framed*.

Divide 1034067 by 8. The quotient

### THE WEST'S COMMUNICATIONS CONNECTION FOR

CELWAVE

Base Station Antennas, Cavities, Duplexers, Filters, Multicouplers, Combiners and System Components

- Celwave's Largest Supplier in the West
- Tune Filter Products, New & Used
- Site Expansions, Both Tx & Rx
- Technical Engineering with Hotline
- Local Inventory
- Lower Shipping Costs
- Talley Will Stage Your System for On Time Delivery

Call Today:

800-949-7099



Los Angeles • Phoenix San Diego • San Francisco Fax: 310-948-3126 equals 129258.375. Multiply the decimal portion of the answer by 8. The product of  $0.375 \times 8 = 3$ . Recall that this is actually the *4th frame* because the *frames* start at *true* 0 and count to either 7 or 15. We just don't start counting at zero!

#### The heart-beat: synchronization

Acquiring and synchronizing with an incoming data stream takes some sophistication, but it is nicely done in the Bravo pagers by generating impulses at a regular rate of speed.

At 512bps, there are 576 bits (preamble) + 32 bits (frame sync) +  $(8 \times 64 = 512)$  bits) (eight frames), for a total of 1,120

bits per message. Because these 1,120 bits take 2,187472 seconds for transmission, divide 2,187472 by 1,120 to determine the duration of each bit; 2,187472  $\div$  1,120 = 0.0019531 seconds or 1,9531 milliseconds.

By reciprocation, we find that the clock is operating at 1/0.0019531 =512Hz. This value is easily achieved by dividing the 1.048576MHz timebase crystal frequency by 2.048 (a 10-bit shift).

Similarly, dividing the 2.457600MHz crystal frequency (used at 1,200bps) by 2,048 results in a clock frequency of 1,200Hz. By reciprocation, 1/1,200 = 833.3 microseconds, the duration of each bit in 0.933296 seconds (the message time at 1,200bps).

Somewhere in this chip is a stage with the single function of counting these impulses and signaling when the count reaches 32. For want of a better term, call 32 impulses a *click*.

Everything in the POCSAG signal format is divisible by a number of clicks. There are 18 clicks in the *preamble* (576/32 = 18); there is one click in the *frame* sync and two clicks per *frame*.

For the duration of each click, a comparison is made. Does the information in the data stream during one click match the *preamble* (101010...)? If so, the receiver is turned on to receive the *frame sync*. If the click window matches the first half of a *frame* (the capcode), then the alert is signaled while the receiver stays on to get the next click of information (the calling party's number). These go into RAM.

Failing to match the capcode in its assigned *frame*, the Bravo starts looking for the 576-bit *preamble* and the 32-bit *frame sync code*.

Lacking a *preamble*, the Bravo drops into *POCSAG battery-saver mode*. The receiver is turned on for 217 milliseconds out of every 1.047 seconds (for POCSAG 512) and 93 milliseconds out of every 1.047 seconds (for POCSAG 1.200).

#### 'Look what I found!': memory display

Once the Bravo "sounds off," it is free to display the converted data on the liquid crystal display (LCD).

Acquiring and synchronizing with an incoming data stream takes some sophistication, but it is nicely done in the Bravo pagers by generating impulses at a regular rate of speed.

Recalling the data stream "snapshot" from RAM (by depressing the gray read button at pin 9 of U001) involves two operations. The first depression of the read button silences the tone (if it is on). The second depression causes the microprocessor to transfer RAM contents into a decoder, and then to the display.

U102 contains 12 8-bit registers. These may hold as

many as three 32-bit *words* — incoming phone numbers — and are enabled by use of the *protect* switch at pin 45 of U102. As long as power is available from pin 4 U001, these numbers remain in *memory*.

Electronically, the display section consists of the LCD driver, the LCD and a light switch. Another portion of the microprocessor is used to drive the multiplexed display and to provide backplane ac signals.

There is still more: Several *canned* messages are available when needed, as is a 3.2kHz audio generator to feed the *beep* speaker.


In all, there is a lot of technology to be found in the Bravo pager.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds & Communications, South Houston, TX, for their help with this project. Tel: 713-944-1813.

啣

January 1995/\$3

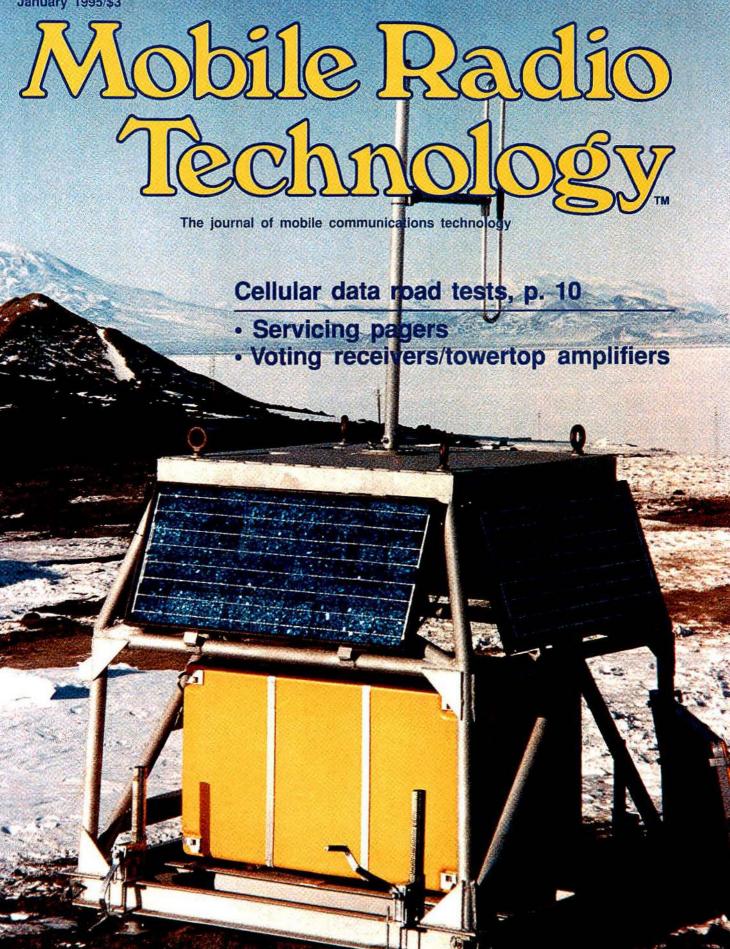

## Servicing pagers: Headaches (and some aspirin)

Part 12—Here are some tips for solving little quirks and problems that come up from time to time with Motorola Bravo pagers. A computer program you can use to track your customers is included.

#### By David Ludvigson

You have just finished replacing a crystal and aligning a Motorola Bravo pager. The frequency and format problems have been solved. You go to the programmer and confidently enter the new capcode and answer the appropriate prompts with "yes." Then you page it.

"123A456B789C" shows in the display. Whaaat?

This problem is one of several poorly documented problems that occur with different versions and programming methods of and for the Bravo pagers.

Certain "hidden" programming options can remove those interfering letters, as well as the annoying chirp that sounds when the Bravo is "reminding" you to read an unread message.

When trying to program a series of pagers simultaneously, the letters "PRC" may appear on the programmer display. To fix that error, from the selection page just preceding the *READY TO PROGRAM*? prompt, depress  $\theta$  and 9 on the programmer simultaneously. This step places you in another page of programming options. (See the operator's section of the manual for a full description of what the initials mean.) It is important that the *BSVR* (battery-saver) option be enabled, so enter Y in response to that prompt.

The page of options that follows contains the single entry *PRC*. Entering N (no) here removes those interfering letters from the display. The next page again prompts for *READY TO PROGRAM*?

Customers often complain of the momentary *chirp* that precedes vibration when the pager is in its vibration-alert mode. Use the Bravo Programmer to read the pager's programming. Under OP-

Ludvigson is a technician in Houston.

TIONS, the SMC prompt is followed by Y, which means that the *silent mode chirp* (SMC) has been enabled. Change the Y to N, and the problem is solved.

Recall what has been written about *normal* and *inverted* code formats. It is a good idea to test the pager with your code-box just to make sure the code format is correct. If you have to switch signal polarity to cause the pager to respond, then reverse your DI selection.

Sometimes, the output signal at M1 will look dead, even when you are belting it with 10V of RF signal. Recheck the first conversion crystal frequency. It is possible that you are using a 45MHz offset crystal

#### Pager servicing series

- Part 1: "Build a Shielded Room," January 1994. (All pagers.)
- Part 2: "Build An 'IFFER,'" February 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 3: "Frequencies, Coding Formats, March 1994. (Bravo.)
- Part 4: "From Bench To Programmer," April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.) Part 6: "Elegant Simplicity," June 1994. (Bravo.)
- Part 7: "Problems In Paradise," July 1994, (Brayo.)
- Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)
- Part 9: "150MHz Receivers," September 1994. (Bravo.)
- Part 10: "Tales Crystal Filters Tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 11: "Microprocessor Board," November 1994. (Bravo.)
- Part 12: "Headaches (and Some Aspirin)," January 1995.

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. in a 17.9MHz receiver board (or viceversa). The oscillator cannot work so far from its intended frequency.

Several crystal manufacturers support the Bravo. I was doing fairly well in finding crystals, and then my supply improved when I found Crystronics' "rocks." Figure I on page 32 lists the company's codes for VHF through 900MHz crystals. Call the company at 305-566-6949 for further information.

#### **Tracking customers**

When a merchant begins to deal in pagers, he may discover rapidly that he needs a means of keeping track of his customer base. Generally, as long as he does not exceed 200 customers, he can handle customer records with a Rolodex file. With more than 200 customers, though, it is time to look for a decent bookkeeping program.

After looking around for several months, I finally decided there was no software available that was designed for pager information filing. Several programs merely laid information down on the disk, and the user had to define whether his input was in the "Pager Number" or "Capcode" field. Then you could twiddle your thumbs while the disk found a match. The occasional "double number" problem (where two customers have the same capcode and pager number) was frustrating with some software because it would find the first match and just stay there! It was not possible to get beyond the first collision of matching data to find out what was on the other side.

Then, there was the issue of how ornate the software had to be. Were alternating color bars really necessary, or just a screen with information? How much of a hard disk drive would be occupied with actual data, and how much would be used to crunch color and location information as it printed the data to a particular spot on the screen? I decided to write my own software in a (Beginner's All-purpose Symbolic Instruction Code) programming language called BASICA to see which would do the best. The results were surprising.

Heavy-duty databases use a separate data file where the information lies in wait to be displayed on the screen. Whenever you search for some data, this file is interrogated until a match is found, starting at your first file and marching through each file, one at a time. As your database increases, this search can become a huge task. One version of this sort of program uses nearly 3 million bytes of storage for the nearly 2,000 customers at JJ Sounds and Communications, South Houston, TX.

My own method is more conservative. No flashing colors, no neon, just basic business. The same 2,000 customer files and the program occupy only 650K of disk space.



The grinding of the hard drive is broken into 12 nearly identical programs that have been "chained" together, each calling the next in sequence. Information is presented in an easy-to-edit fashion, and a 12-yearold could easily update the program.

When entering data, eight fields are used in each file: AZ is the pager phone number; N is the line number in which the data have been entered for this pager; CC is the capcode for the pager; NM is the customer name; AD is the rate and month rental charge; CT tracks special features such as voice mail or statewide coverage; ST is the month-to-month payment due date; and NT is used to keep track of various notes, such as our own registration number, price paid and when the last payment was received.

Often, we receive payment by check, with no more information than a name and address. Perhaps the most powerful portion of this program is found in the MID\$ (midstring) function, which allows names (first, last and whole name) to be found by the program.

#### Pagerfiles

The Pagerfile program uses a universal entry format to allow the user merely to type in whatever information he has without specifying the field—and the program finds the match(es).

Pagerfiles contain—within themselves the DATA statements that pertain to your customers. These statements are edited by the screen editor, and doubly resaved so there is a backup copy of the files. Each Pagerfile starts out about 5.5K long, but it can grow rapidly, so it is a good idea to install the program on a hard disk drive.

Hard copy receipts may be generated with Pagerfiles. Automatic "next payment due" mathematics are performed within the program and printed on the receipt. Embedded commands allow the user to print files for customers with past-due payments.

Current versions of Pagerfiles are "chained" through 12 programs, each capable of 200-250 customer fields. This capacity represents 2,400 to 3,000 customers. With slight modifications to the program, Pagerfiles could be extended to several hundred programs, each capable of handling 200-250 customers.

Written in BASICA, the essential program is adapted easily to any IBMcompatible computer offering a version of BASIC, which is usually bundled with the disk operating system (DOS).

It is important to note the presence of the "echo" copy, thus doubling the memory requirements of the floppy disk or hard disk drive. Ten full copies (and "echoes") of Pagerfiles fit nicely on a

Circle (26) on Fast Fact Card

1.44Mb floppy diskette and take care of 2,000 to 2,500 customers.

Depending on the microprocessor speed and hard drive access time. Pagerfiles sorts through 2,000 customers in about 4.5 seconds on a '486. 33MHz computer on the hard disk drive. Using a 5.25-inch diskette, the same machine takes 12 seconds. Speed is a question of machine and storage media.

Data entry consists of structuring your

files around the format given (i.e., pager number, line number from the program, capcode, name, rate per month, features, monthly due date and miscellaneous and search information). Once this information is entered, begin entering data at line 500. (See program on page 36.)

Other special features may be embedded in Pagerfiles. Various portions of the NT\$ may be used to indicate unassigned or inactivated pagers. A bit of imagination with



## You.

Value added. They're the "buzz words" for the 90's. And the test equipment business is no exception.

So when you told us you needed a reliable Communications System Analyzer that was packed with features but lean on price, we listened. Then we built the R-2550. For testing two-way conventional radios,

there's simply no better value on the market.



Call Communications Test Equipment today at:


1-800-235-9590 Ext. 23.

The R-2550 from Motorola, priced from \$8,695.\*





\*From \$286/mo. on a 36-mo. lease.

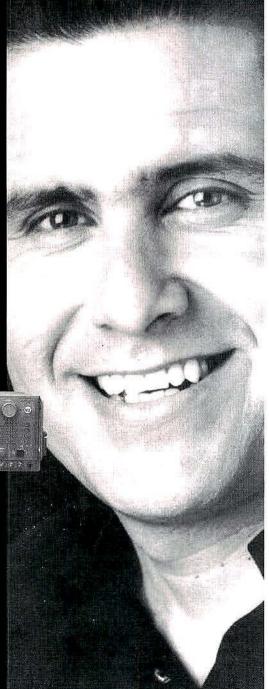

Circle (31) on Fast Fact Card

Pagerfiles goes a long way toward achieving a better Rolodex index file.

Also included in Pagerfiles is a laborsaving routine that determines from the data exactly when payment is due and dials the pager number. The program downloads into any Hayes-compatible modem to leave a "get back to me" phone number that is programmed by the user. (See lines 92-116 in the program listing.)

When using BASICA, it is necessary to reset the date and time calendar-clock to print an accurate receipt. With BASICA running, type PRINT DATE\$ and hit RE-TURN. The value of DATES is printed. To change it, type DATE\$="mm/dd/ yyyy" (with mm, dd and yyyy standing for month, date and year) and hit RE-TURN. To change the time, type PRINT TIMES and hit RETURN. The value of TIMES will appear. To change it, type TIMES="hh/mm/ss (with hh, mm and ss standing for hours, minutes and seconds in a 24-hour clock format) and hit RE-TURN. This step sets the internal calendar and clock, and the information will be printed on each receipt.

A documented copy of PGRFILE I is included with this article, and anyone is free to adapt, modify or use it. Copies of PGRFILES are available for a \$15 check or money order. A program called PGF0 contains documentation of the program, and an INFO file provides an overview.

The following lines *must* be written carefully to allow the programs to chain properly: lines 12, 14, 20, 24, 66, 74, 78 and 100. Line 14 informs the user which Pagerfile is being used. The remaining lines handle the chaining operations.

Pagerfiles are provided on 5.25-inch diskettes (formatted for 360K) and 3.5-inch diskettes (formatted for 1.44mB) for IBM-compatible computers. Indicate which version you need. Send to: David Ludvigson, 318 Avenue B. South Houston, TX 77587.

For readers interested in a Windowsstyle bookkeeping and billing method, I recommend a program called PAGE-KEEP, available from Electronic Information eXchange (EIX). This particular software generates reports and has numerous options such as multi-user capability, auto-page, over-call management and automatic data exchange, which provides an instant comparison between your records and those of the billing company. For further information, call 713-765-7400.

#### Acknowledgement

I would like to the management and staff of JJ Sounds and Communications, South Houston, TX, for their help with this project, Tel.: 713-944-1813.



 Doubles as remote programmer for our TP-154 and TP-154 PLUS tone panels.

Connects only to Detector or De-mod output and 12 VDC.


In Canada: CARTEL - PH: (800) 663-0070 EASTCOM -PH: (800) 263-2323



Circle (29) on Fast Fact Card

| CHISINO                                | NICS PART # AND FRI<br>REFERENCE CHART | EQUENCY                                |
|--|--|--|
| мото                                   | ALL                                    |  |
| LOW                                    | UHF                                    | 900                                    |
| BR110001-35.200/L                      | BR310001-454.025                       | BR410001-929.3625                      |
| BR110002-35.220/L                      | BR310002-454.050                       | BR410002-929.3875                      |
| 3R110003-35.240/L                      | BR310003-454.075                       | BR410003-929.4125                      |
| 3R110010-35.500/L                      | BR310004-454.100                       | BR410004-929.4375                      |
| 3R110011-35.540/L                      | BR310005-454.125                       | BR410005-929.4625                      |
| 3R120011-35.540/H                      | BR310006-454.150                       | BR410006-929.5625                      |
| 3R110012-35.560/L                      | BR310007-454.175                       | BR410007-929.6375                      |
| 3R110013-35.580/L                      | BR310008-454.200                       | BR410008-929.6625                      |
| 3R120013-35.580/H                      | BR310009-454.225                       | BR410009-929.6875                      |
| 3R110014-35.600/L                      | BR310010-454.250                       | BR410010-929.7125                      |
| 3R120017-43.200/H                      | BR310011-454.275                       | BR410011-929.7375                      |
| 3R110019-43.240/L                      | BR310012-454.300                       | BR410012-929.7625                      |
| 3R120019-43.240/H                      | BR310013-454.325                       | BR410013-929.7875                      |
| BR120022-43.340/H                      | BR310014-454.350                       | BR410014-929.8125                      |
| 3R120024-43.420/H                      | BR310015-454.375                       | BR410015-929.8375                      |
| BR110028-43.560/L                      | BR310016-454.400                       | BR410016-929.8625                      |
| 3R120028-43.560/H                      | BR310017-454.425                       | BR410017-929.8875                      |
| BR120029-43.580/H                      | BR310018-454.450                       | BR410018-929.9125                      |
| 3R120031-43.620/H<br>3R120033-43.680/H | BR310019-454.475                       | BR410019-929.9375<br>BR410020-929.9625 |
| SH120033-43.000/H                      | BR310020-454.500<br>BR310021-454.525   | BR410020-929.9825<br>BR410021-929.9875 |
|  | BR310022-454.455                       | BR410021-929.9875<br>BR410022-931.0125 |
| VHF                                    | BR310022-454.455<br>BR310023-454.575   | BR410022-931.0125<br>BR410023-931.0375 |
|  | BR310023-454.600                       | BR410024-931.0625                      |
| BR210001-152.030                       | BR310025-454.625                       | BR410025-931.0875                      |
| BR210002-152.060                       | BR310026-454.650                       | BR410026-931.1125                      |
| BR210003-152.090                       | BR310027-462.750                       | BR410027-931.1375                      |
| BR210004-152.120                       | BR310028-462.775                       | BR410028-931.1625                      |
| BR210005-152.150                       | BR310029-462.800                       | BR410029-931.1875                      |
| BR210006-152.180                       | BR310030-462.825                       | BR410030-931.2125                      |
| BR210007-152.210                       | BR310031-462.850                       | BR410031-931.2375                      |
| BR210008-152.240                       | BR310032-462.875                       | BR410032-931.2625                      |
| BR210009-152.480                       | BR310033-462.900                       | BR410033-931.2875                      |
| BR210010-152.510                       | BR310034-462.925                       | BR410034-931.3125                      |
| BR210011-152.540                       | BR310035-465.000                       | BR410035-931.3375                      |
| BR210012-152.570                       | BR310036-464.975                       | BR410036-931.3625                      |
| BR210013-152.600                       | BR310037-457.575                       | BR410037-931.3875                      |
| BR210014-152.630<br>BR210015-152.660   | BR310038-452.130                       | BR410038-931.4125                      |
| BR210015-152.690                       | BR310039-455.500                       | BR410039-931.4375                      |
| BR210017-152.720                       | BR310040-452.650                       | BR410040-931.4625                      |
| BR210018-152.750                       | BR310041-457.975                       | BR410041-931.4875                      |
| BR210019-152.780                       | BR310042-454.550                       | BR410042-931.5125                      |
| BR210020-152.810                       | BR310043-464.700                       | BR410043-931.5375                      |
| BR210021-152.840                       | BR310044-456.375<br>BR310045-464.375   | BR410044-931.5625<br>BR410045-931.5875 |
| BR210022-154.625                       | BR310045-464.375<br>BR310046-452.750   | BR410045-931.5875<br>BR410046-931.6125 |
| BR210023-157.740                       | BR310047-453.125                       | BR410040-931.6125<br>BR410047-931.6375 |
| BR210024-158.100                       | BR310048-456.680                       | BR410048-931.6625                      |
| BR210025-158.460                       | BR310049-463.200                       | BR410049-931.6875                      |
| BR210026-158.700                       | BR310050-463.250                       | BR410050-931.7125                      |
| BR210027-152.420                       | BR310051-449.675                       | BR410051-931.7375                      |
| BR210028-159.855                       | BR310052-464.350                       | BR410052-931.7625                      |
| R210029-152.0075                       | BR310053-454.6125                      | BR410053-931.7875                      |
| BR210030-153.710                       | BR310054-445.600                       | BR410054-931.8125                      |
| BR210032-155.280                       | BR310055-445.675                       | BR410055-931.8375                      |
| BR210042-152.650                       | BR310056-445.825                       | BR410056-931.8625                      |
| BR210046-153.605                       | BR310057-445.950                       | BR410057-931.8875                      |
| BR210053-152.500                       | BR310058-462.625                       | BR410058-931.9125                      |
| BR210056-150.635                       | BR310059-462.200                       | BR410059-931.9375                      |
| 3R210059-151.190                       | BR310060-462.350                       | BR410060-931.9625                      |

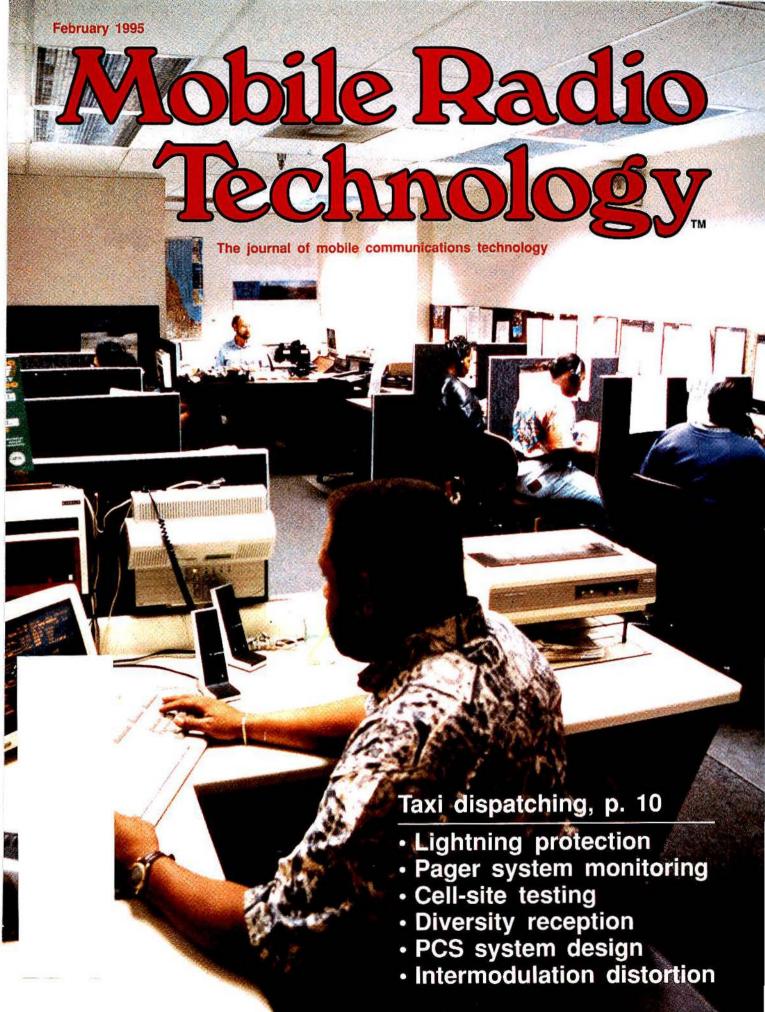The first two characters of the model number BR = Bravo; BE = Bravo 17.9IF (900 band). The last two digits represent a specific frequency and is common for all models.



An INTERTEC<sup>®</sup> Publication



## Servicing pagers: Mixed signals

Part 13—Check pager alignment after a customer has used a new pager for a week and listen to the paging system regularly for signs of trouble to make yourself extra valuable to the airtime supplier.

#### By David Ludvigson

To this point in the pager servicing article series, various pitfalls and problems that occur with Bravo pagers have been discussed. The following information describes some other "disturbances" not previously covered.

After changing a crystal in a Bravo pager, it is wise to have the customer bring the unit back after about a week to check the alignment. There is a natural tendency of a crystal to age, which may cause it to wander from its original frequency. This phenomenon is especially noticeable with Bravo pagers that use 17.9MHz IF receivers operating in the 930MHz range. The operating frequency also is adversely affected by changes in ambient temperatures, so as the seasons change, expect a sudden influx of alignment work orders.

#### **Beyond local control**

Frequent "hookups" (setting up new customers to receive messages) require a paging network to maintain vast quantities of capcodes and associated telephone lines. Having these, the supplier also must deliver a radio signal to geographic areas that suit the customers' needs. Theoretically, all the equipment and data will provide reliable service—but there may be other problems.

As the reseller's customer base grows, confusion may result: capcodes may suffer from "dyslexia;" pager telephone numbers may be confused or duplicated; and transmitters may fail. More unusual problems may arise, too.

As a paging service grows, the need to expand current services may conflict with the existing structure. Thus, in spite of a

Ludvigson is a technician in Houston.

technician's loud insistence that "this capcode *has* to be working" (and the network representative asserting that "it should be"), it usually is discovered that expansion (or some other work) has caused inadvertent shut-downs of several capcodes—at the *network's* end. A capcode generator and an alignment of the pager have produced reliable operation, but the switchboard required at-

#### Pager servicing series

Part 1: "Build a Shielded Room," January 1994. (All pagers.)

- Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 3: "Frequencies, Coding Formats, March 1994. (Bravo.)
- Part 4: "From Bench To Programmer," April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.)
- Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems In Paradise," July 1994. (Bravo.)

Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Part 9: "150MHz Receivers," September 1994. (Bravo.)

Part 10: "Tales Crystal Filters Tell . . .," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and Some Aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)


Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294, Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. tention to make the proper connection.

Technicians who are always listening to their airtime suppliers' frequencies usually are quick to notice impending problems. In September 1993, a noticeable "pinging" was heard in a signal from one of Houston's largest airtime suppliers. I suggested that the transmitter's voltagecontrolled oscillator (VCO) was introducing distortion. Tests conducted with the transmitter circuitry off-line and under ideal conditions revealed proper waveforms. When the transmitter was placed back on the air, though, the waveform distortion returned. A new VCO assembly was required to tame the problem.

Unfortunately, not all problems are consistent. Tracking the source of countless "error" messages in pagers caused one Houston airtime supplier to lose many of its resellers. Intermodulation distortion was entering the data stream at the satellite receiver and cutting data to ribbons. With the intermittent nature of the problem, tracking the source was extremely difficult. The solution was expensive because it involved new sites and accompanying transmitters.

Sometimes, the problem might be localized. A paging transmitter sometimes will fail, leaving a large territory without service. Listening to the monitor revealed that the distant paging transmitters were operating, but the local one seemed to be dead. A thunderstorm had flooded a transmitter location in south Houston.

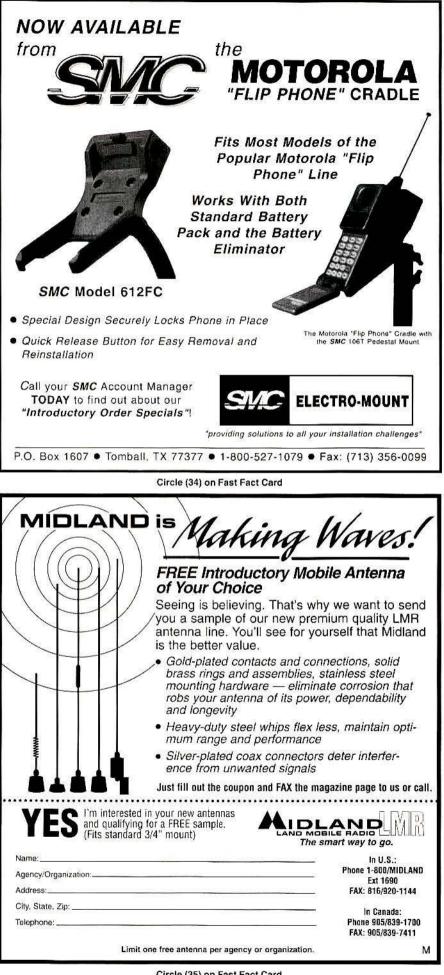Service technicians who take time to listen to their supplier's frequencies can be helpful when they contact service employees at the paging company to report unusual system operation. Remote transmitter monitors may report a system is working fine, but they cannot report the presence of intermodulation distortion. Furthermore, varying weather conditions may also cause signal fading.



With the proliferation of 930MHz assignments has come the considerable problem of transmitter noise. In heavily populated areas, transmitted signals tend to overlap one another, causing desensitization at the receiving pager. (See "Technically Speaking—Transmitter Noise" by Harold Kinley, C.E.T., in the September 1993 issue, p. 8, for an indication of the headaches that may occur at transmitter sites.) In Houston, where many pager users are often directly *beneath* paging transmitters, channel spacing vs. pager sensitivity may become a critical issue. Re-

Another issue often found in synchronous or simulcast paging systems is the problem of synchronizing the very start of the message at the preamble or comma.

ceiver designers will attempt to narrow the pager's bandwidth (at the IF) to allow reception in the presence of a strong adjacent-channel signal, but this places stringent requirements on receiver local oscillators for frequency stability.

Another issue often found in synchronous or simulcast paging systems is the problem of synchronizing the very start of the message at the preamble or comma. The alternating 1-0 pattern of POCSAG coding could easily become confusing to a pager located mid-way between two outof-sync transmitters. At 512bps, this condition could occur in as little as  $1/_{512}$  of a second. It gets worse as the bps rate is increased! Various proposals have been suggested (such as specific codewords) to minimize this problem, although implementation would require a totally new approach, as well as new pagers.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds & Communications, South Houston, TX, for their help with this project. Tel: 713-944-1813.

嚠

Circle (35) on Fast Fact Card

April 1995

## The journal of mobile communications technology

ac


10

## Coaxial connectors, p. 10

- CDMA.cellular
- Servicing pagers
- Lightning protection theory
- Pulling cable
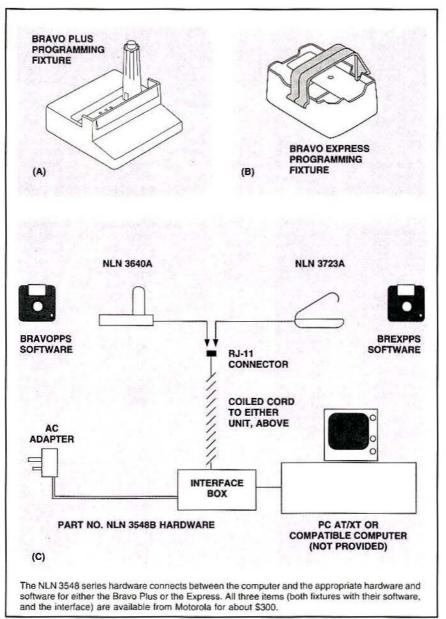
## Servicing pagers: Essential differences

Part 14—Here are some tips for programming Bravo Plus and Bravo Express pagers, including computer and storage media selection, hardware connections and software installation.



#### By David Ludvigson

Unlike the Bravo pager, the Bravo Plus and Bravo Express pagers are capable of more than merely receiving pages and displaying basic information in the window. One big difference is a 12/24-hour clock with a time stamp. The clock and time stamp features (although not essential to pager operation) provide something for the microprocessor to do while waiting for a paging message.

#### View from the programmer

Plus and Express programming requires more sophistication than the Bravo. In this case, the user will need an IBMcompatible computer with at least 360K of resident RAM (user supplied) and the programming interface and software (provided by Motorola). The necessary hardware and software are packaged under Motorola part number NLN 3548B. The NLN 3640A includes diskettes for the Bravo Plus and the necessary interfacing hardware to match the pager to be programmed. Similarly, the NLN 3723A package contains software and a test fixture to mate with the Bravo Express.

The NLN 3548B requires the use of one of the RS-232 serial ports found at the rear of the computer, defined by the user in the SETUP program when saved to hard disk or diskette. It is suggested that the default names be used to access the program, i.e., BRAVOPPS for Bravo Plus, and BREXPPPS for the Bravo Express.

Depending on what is connected to your computer, it may be convenient to use COM PORT 1 for a printer and COM PORT 2 for the programmer. In this manner, PGRFILES (or any other bookkeeping utility program) will not collide on

Figure 1: Programming fixtures are used to hold the Bravo Plus (A) and Bravo Express (B) pagers. The equipment configuration is shown at (C).

Ludvigson is a technician in Houston.

the RS-232 lines. (PGRFILES was covered in Part 12 in the January 1995 issue.)

There is one quirk with the Bravo Plus and Bravo Express software. The Bravo Plus software runs well at 33MHz; both reading FROM and writing TO the Bravo Plus may be done at Turbo speed. Programming the Express, though, requires defeating the Turbo feature of most highspeed computers. The software can READ the pager fine at Turbo speeds, but WRIT-ING to the Express requires a slower speed. Motorola has a software remedy for this problem, available for the asking.

Software protection is an option in these programs. Passwords can be placed in front of the main body of the program, preventing unauthorized use. Similarly, a password may be embedded in either the Plus or Express to prevent others from reading or overwriting the data you have entered. As you will discover, there are 10 spaces in the ENTER PAGER PASSWORD frame. Each space may be filled with any letter, number or some punctuation marks. Because there are 26 letters. 10 digits and numerous punctuation marks, the possibility of exactly matching an unknown string is exceedingly remote—and you only get six or seven attempts to do so! Unofficial (non-Motorola) hardware and software adaptations have been developed that allow the user to defeat the password protection. Password-removal equipment may be purchased from Viamtel, 2909 Fannin, Houston, TX 77002, 713-750-0007.

#### Hardware connections

An ac adapter provides the required operating voltages for the interface unit. Attached by means of RJ-11 connectors, a mechanical interface consisting of a 3-pin electrical connector and a form-fitting pager nest provides the terminals for communicating data to and from the pager. (See Figure 1 on page 66.) The mechanical interface is changed to match either the Bravo Plus or the Express.


#### Software installation: Bravo Plus

Provided with the NLN 3640A are the necessary diskettes (both 5<sup>1</sup>/<sub>4</sub>-inch and 3<sup>1</sup>/<sub>2</sub>-inch) that turn the computer into a programmer.

Bring up the drive-prompt (A>). Insert the proper diskette into the A drive. Verify the drive by typing A: and hit ENTER. Behind the A prompt, type SETUP and hit *ENTER.* Copyright and version number will be displayed along with a "hit any key to continue" message. Doing so will bring up a selection screen where you decide whether you will be using backup floppy copies of the software or installing it on a hard drive.

... a password may be embedded in either the Plus or Express to prevent others from reading or overwriting the data you have entered.

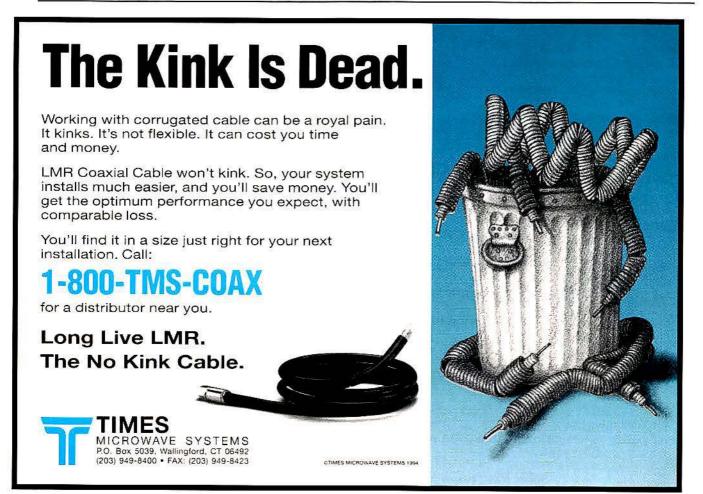Assuming use of the hard drive, merely hit *ENTER* or *RETURN* after reading the first page of the SETUP program. Page two asks for verification of the destination drive for the program. Is it the hard drive?



Circle (65) on Fast Fact Card

If you answer YES, the program will prompt for PATHS and PATHNAMES for your program. Because the program is on the A drive and you wish to place it on the hard drive (usually "C"), your source drive is A and the destination drive is the C drive.

The BRAVOPPS.EXE file will start on the C drive, so the program path will originate on C: . The archive files (BPLUSARK) and help files (BPLUSHLP) are "child" files called by BRAVOPPS.EXE. Unless you know how to use paths and pathnames, I suggest simply hitting *ENTER* when the default names are highlighted—it is easier that way, and the names are odd enough to avoid accidental over-writes.

Next, the COM PORT is selected. As mentioned earlier, I use COM PORT 1 for my printer, so COM PORT 2 is assigned for the interface. It should be noted that resident software for fax or modems might occupy various COM PORTS, so someone who *knows* might be helpful in determining what is available and how to get to it.

Ok, password time . . . (sigh!) If you are paranoid, enter your magic password in the blank. If not, leave it blank. (Mega-sigh!) The password will prevent unauthorized use of your computer as a means of programming Bravo Plus pagers.

#### No hard drive?

If you have no hard drive, get into your DOS version of DISKCOPY and make copies of both disk 1 and disk 2, labeling them appropriately.

Enter the SETUP program by answering N to the "Is this setup correct?" question at the bottom of the screen. Place your *copy* of disk 1 in the B drive and

your copy of disk 2 in the A drive.

At the DISK #1 DRIVE prompt, enter B. At the DISK #2 DRIVE prompt, enter A. Hit the ENTER key as the default paths are highlighted, and select your COM PORT and PASSWORD as outlined above. If you have followed these directions, or if you are content with your choices, answer Y to the query at the bottom of the screen. The drives will grind for a few seconds as the appropriate files

#### Crystal suppliers

David Ludvigson's January 1995 article included a reference to a supplier for crystals that can be used in the Motorola Bravo pager. In response to a request, here is a list of additional suppliers for such pager crystals. Circle the corresponding number on the Fast Fact Card on page 117 to receive information from any supplier. Addresses, telephone numbers and fax numbers for these suppliers are printed in the December 1994 edition's buyers' guide section.

Adams Distributing Circle (225) on Fast Fact card

Bomar

Circle (226) on Fast Fact card

Cal Crystal Lab Circle (227) on Fast Fact card

D&L Wholesale Distribution Circle (228) on Fast Fact card are marked and transferred from one to the other.

Starting the diskette version of BRAVOPPS will require placing the *copy* of disk 2 in drive A and the *copy* of disk 1 in drive B. At the A> prompt, enter *BRAVOPPS*. Unless you have protected your program with a password, the Motorola copyright notice and "hit any key.," message will appear. If the program has been password-protected, you

#### Electro Dynamics Crystal Circle (229) on Fast Fact card Frequency Management Circle (230) on Fast Fact card Hite Electronic Sales Circle (231) on Fast Fact card Hy-Q International Circle (232) on Fast Fact card ICM Communications Circle (233) on Fast Fact card K-W Manufacturing

Circle (234) on Fast Fact card

Marden Electronics Circle (235) on Fast Fact card

Motorola Circle (236) on Fast Fact card

Sentry Manufacturing Circle (237) on Fast Fact card

#### E - X - T - E - N - D YOUR EXISTING RF COVERAGE


#### USE:

Patented signal taps On Frequency Radio Repeaters Booster amplifiers, Line amplifiers . . .

and the
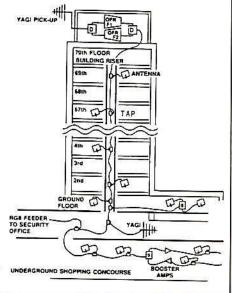
#### EXPERIENCE OF THE COMPANY that specializes in RF extension systems





Circle (67) on Fast Fact Card



#### Pager servicing series

- Part 1: "Build a Shielded Room," January 1994. (All pagers.)
- Part 2: "Build An 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.) Part 3: "Frequencies, Coding Formats, March 1994. (Bravo.)
- Part 4: "From Bench To Programmer," April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.)
- Part 6: "Elegant Simplicity," June 1994. (Bravo.)
- Part 7: "Problems In Paradise," July 1994. (Bravo.)
- Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)
- Part 9: "150MHz Receivers." September 1994. (Bravo.)
- Part 10: "Tales Crystal Filters Tell . . .," October 1994. (Bravo, Bravo Plus, Bravo Express.)
- Part 11: "Microprocessor Board," November 1994. (Bravo.)
- Part 12: "Headaches (and some aspirin)," January 1995. (Bravo.)
- Part 13: "Mixed Signals," February 1995. (Bravo.)
- Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)
- Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher.

will *have* to enter your password before the program will let you in.

Similarly, starting BRAVOPPS from the hard drive will require entering *BRAVOPPS* at the C> prompt. Enter your password, if required, and you will be at the copyright notice.

#### Software installation: Bravo Express

In general, installation of the Bravo Express software is identical to that of the Plus.

With the SETUP diskette in drive A, type *SETUP* behind the A> prompt. The same options as presented above will appear on the screen, allowing you to exit and make copies using DOS DISKCOPY or proceed to install the programs on your hard drive. You will be prompted for your COM PORTS and PASSWORD. If the Bravo Plus software works well, enter the same COM PORT as you used previously. As noted earlier, diskette working copies will end up with diskette copy 1 in drive B and diskette copy 2 in drive A. The use of default paths and pathnames is encouraged.

Having successfully installed the software, type *BREXPPPS* at the drive prompt and hit *ENTER*. Enter your password (if used) and begin programming the Bravo Express.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds & Communications, South Houston, TX, for their help with this project. Tel: 713-944-1813.

御



Circle (70) on Fast Fact Card

## 

THUHUH

LULLUL LEUR

June

### Flex paging setup, p. 10

- Verifying coverage
- Servicing pagers
- Mobile antennas

# Servicing pagers: And you shall receiver knowledge . .

Part 15—Details about the Bravo Plus and Bravo Express 928MHz–932MHz NRF4101 receiver boards include some tips to make testing easier and faster. As with the Bravo, the 17.9MHz IF units have critical adjustments.

#### By David Ludvigson

The NRF 4104 receiver board for 928MHz–932MHz Bravo Plus and Bravo Express pagers comes in two basic fla-

vors—17.9MHz IF and 45MHz IF versions. Past articles on the Bravo have dealt extensively with the frequency stability and other characteristics of these two IF blocks. (See Part 7, "Problems In Paradise," July 1994 issue.) Basically, the 45MHz IF board is less critical of adjustment than the 17.9MHz board. This difference stems from:

Ludvigson is a technician in Houston.


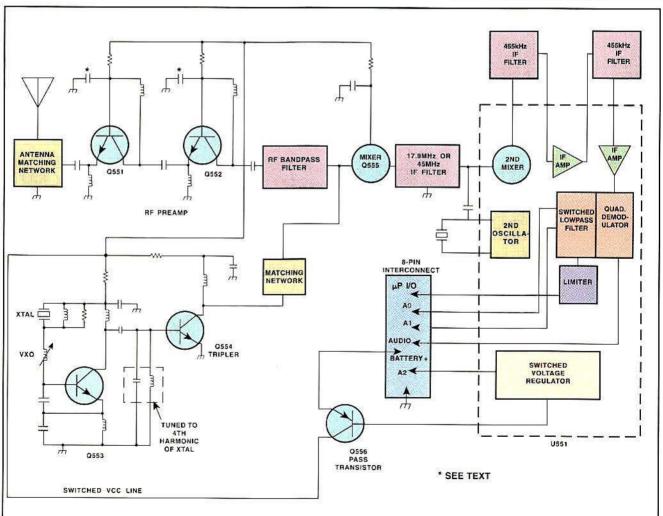


Figure 1. This block diagram represents the circuitry used in the Bravo Plus and Bravo Express receivers.
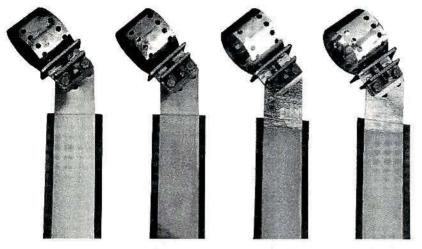
## **New** Unique Cable Grounding Kit Series



## **Uni-Kit 2 Series**

- ► Fits cables up to 2" (down to 1/4")
- Fits elliptical waveguides
- Lower resistance (less than half others)
- Lower inductance (almost half others)
- Vibration and wind tested
- Quick nut driver installation
- Adjustable strap to cable angle
- Four models for no dissimilar connections
- Competitively priced





Uni-Kit 2CT Copper coax to Tower



to Copper

Uni-Kit 2TT Tinned coax\* to Tower



Uni-Kit 2TC Tinned coax\* to Copper

\* Can also be used for grounding a galvanized tower leg.



(1) the stability of the first conversion oscillator.

(2) the bandwidth of the signal getting through the 1F stage.

The service technician can expect problems with the 17.9MHz IF boards from another perspective—the only controls accessible to the technician are the first conversion oscillator tuning and the antenna matching network. The rest of the tuned circuits are either thin-film encapsulated or surface-mounted, pre-tuned networks that only a soul bent on sainthood would care to adjust!

One block diagram is sufficient to fully appreciate these receivers. (See Figure 1 on page 34.)

RF preselection is provided by a pair of transistors in common-base configuration. These two stages have been configured to provide about 12dB of gain without requiring a neutralizing network. Either of these stages, though, can get "wild" if the base bypass capacitors should open—in which case sensitivity drops off severely, or adjustment of the antenna network causes the stages to oscillate—so watch for poor solder joints!

The first conversion crystal oscillator is a Colpitts circuit with oscillation taking place between the base and emitter of Q553. Output from the collector is tuned to roughly four times the crystal frequency by means of a surface-mounted coil and capacitor. This same LC network feeds Q554, which is configured as a frequency tripler. This tripler yields an output of nearly 900MHz to the base of mixer Q555.

At Q555, a combination of the RF signal (at 931MHz, roughly) and the signal from the oscillator-multiplier stages is coupled into the base. The collector circuit contains the crystal filter, either 17.9MHz or 45MHz, and a matching network directly feeding the second mixer.

Within, U551 has a multitude of capabilities. Not only does it include a mixer, it has another crystal oscillator, a pair of 455kHz IF amplifiers, a quadrature FM detector, a switching low-pass filter, a limiter and at least two voltage regulators. It's a jungle in there!

In the Bravo, low-pass filtering is a function of a separate RC network on the logic boards. In the Bravo Plus and Bravo Express, the 4101 series receiver boards have audio filtering functions controlled by signals from the logic board that are fed into the "jungle-chip" on the receiver board. More about this later.

#### Getting into test mode

As with their little brother, the Bravo, the Bravo Plus and Bravo Express spend much of their time turned off. The battery

Circle (32) on Fast Fact Card

#### SIGNALLING For interconnect and remote control applications

D.T.M.F.

MODEL NC401

The Model NC401 is a micro-miniature DTMF decoder, designed for selective control of local or remote applications. Measuring .80"W x 1.37"L x .23"H, the NC401 combines three distinct, multi-addressable decoders offering multiple user-configurable functions. All programmed features are stored in nonvolatile E2Prom memory and are easily programmed by means of a conventional DTMF encoder or the Model NC500 Universal/P.C. programmer. This highly engineered decoder is ideal for portable radio applications having limited space for accessories. The NC401 comes complete with micro-miniature 14 pin header and 12" color coded cable assembly. For FREE detailed information ask for the NC401 user's manual.

> MODEL NC409

The Model NC409 is a DTMF ANI/Alarm

status encoder and companion product to the Model NC401 DTMF Decoder designed to automatically or manually generate any of the 16 DTMF characters. The NC409 features 15 memory locations of up to 30 digits each plus last number redial and multiple user-configurable functions. Programming is easily performed by means of a 12 or 16 button "X-Y" keypad with common ground or the Model NC500 Universal/P.C. programmer. The NC409 measures .85"W x 1.36"L x .165"H and comes complete with micro-miniature 14 pin header and 12" color coded cable assembly. For FREE detailed information ask for the NC409 user's manual.

For detailed information or product catalog call 1-800-874-8663 or Fax 916-477-8403



Circle (34) on Fast Fact Card

saver literally gates the entire 1V line to the RF preamp, first injection oscillatormultiplier and mixer stages simultaneously. At first glance, one would expect this gating to cause frequency instability as the oscillator is being turned from *off* to *on*. The single saving grace for this method lies in the fact that the switched voltage is well-regulated, and the dc decoupling networks to each stage have very short RC time constants.

Placing the Bravo Plus into full-time receive mode requires depressing the two buttons beneath the display simultaneously while bringing the *off-mem-beep* power switch from *off* all the way to the *beep* position. Quickly release the buttons beneath the display, and depress the gray (READ) button momentarily. This procedure sets the pager into sound pressure level (SPL) mode, and the internal speaker will emit a steady tone. Depress the gray button again to advance the pager to MODE 1. In this mode, the pager is serviceable as far as the receiver alignment is concerned.

Another depression of the gray button sets the pager to MODE 2. In this mode, the decoder gives a single chirp when the proper capcode has been transmitted.

Another depression of the gray button reveals hexadecimal information as to how the pager has been programmed. None of this information reveals the capcode, by the way. The capcode must be read with the BRAVOPPS software discussed in Part 13, "Essential Differences," in the February 1995 issue.

When placing the Bravo Express into test mode, a different approach must be taken. Turn the Express off, then, sequentially, from right to left, depress each button beneath the display, and wait. The word POCSAG with a numeral will appear in the window. If you want an SPL test, depress the center switch; otherwise the pager is set only to the test mode. To get out of test mode, turn the Express on by depressing the left button.

There are other ways of turning these pagers into full-time receivers without constantly lifting them out of the RTL 1005 radiation test fixture. For the Bravo, you could solder a 10K resistor across pins 1 and 8 of the interconnection block. For the Bravo Plus and Express, simply ground line A2 (this is easily traced to a test point) coming from the interconnecting block between the circuit boards.

It was mentioned earlier that the Bravo Plus and Express use a switched filter to define the bandpass of the POCSAG signal. The filter connects to lines A0 and A1, again available at the interconnecting block. A bit of experimenting shows that when the pager is in normal operating mode (capable of decoding an on-the-air signal), programming different POCSAG rates into the pager (at the computer) cause lines A0 and A1 to respond differently.

POCSAG 512 A0 goes low, A1 goes high POCSAG 1200 A0 goes high, A1 goes low

These changes occur in response to the strobed battery-saver signal at Line A2 and the received data stream. It will help greatly if you use the IFFER ("Build An 'IFFER,'" February 1994 issue) when trying this for yourself, because you can actually hear the voltage transitions while moving an oscilloscope probe from test point to test point.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds & Communications, South Houston, TX, for their help with this project. Tel: 713-944-1813.

#### Pager servicing series

Part 1: "Build a Shielded Room," January 1994. (All pagers.)

Part 2: "Build An 'IFFER,'" February 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 3: "Frequencies, Coding Formats, March 1994. (Bravo.)

Part 4: "From Bench To Programmer," April 1994. (Bravo.)

Part 5: "The Receivers," May 1994. (Bravo.)

Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems In Paradise," July 1994. (Bravo.)

Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Part 9: "150MHz Receivers," September 1994. (Bravo.)

Part 10: "Tales Crystal Filters Tell . . .," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and some aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)

Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)

Part 15: "And You Shall Receiver Knowledge . . .," June 1995. (Bravo Plus, Bravo Express.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294, Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. May 1995

# Mobile Radio Technology

The journal of mobile communications technology

### ower site reuse, p. 10 🚙 🥌

EMI/RFI survival VHF, JHF trunking Anter a site selection Serv g pagers Prod services showcase Pagi hannel efficiency

An INTERTEC<sup>®</sup> Publication

# Servicing pagers: The information highway

Part 16—Some tips for programming Bravo Plus and Bravo Express pagers help you to bypass possibly unnecessary bells and whistles. It may be better to have the pager 'beep on bad data' than to risk undelivered messages.

#### By David Ludvigson

The interface between the pager and its programming device is relatively simple.

Serial information is read sequentially from the pager into the program or, conversely, from the program into the pager. Although the presentation of this data "looks" different than the Bravo program-

| Motoro<br>BRAVO<br>Page 1<br>Mani, 1 | O Plus<br>of 2 | o Servici<br>Ve |    | ware<br>2.00.01 |        | Enter c           | haracters   | PG Up/Dn for | Menus |                |
|--------------------------------------|----------------|-----------------|----|-----------------|--------|-------------------|-------------|--------------|-------|----------------|
| Inventory Control # BP4BUL2R2C       |                |                 |    |                 | RPC    | Serial            | #BP4BUL2R2C |              |       |                |
| Synthesized Pager<br>Frequency       |                |                 |    | No              |        |                   |             |              |       |                |
|                                      |                |                 |    | 931.2875M       | 4137   |                   |             |              |       |                |
| Phone 1                              | Sumher         | Screen          |    |                 |        |                   |             |              |       |                |
| Coding Format 1                      |                |                 |    | POCSAG          | 2400   |                   |             |              |       |                |
|                                      |                |                 |    | Code A          | Code B |                   |             |              |       |                |
|                                      |                |                 |    | 1802572         | None   |                   |             |              |       |                |
|                                      |                |                 |    | 1234            | 1234   |                   |             |              |       |                |
| Acuve                                |                | Y.N             |    | YYYY            |        |                   |             |              |       |                |
| Functio                              | ns.            | T.N.O           |    | NNNN            |        |                   |             |              |       |                |
| Priority                             |                | Y.N             |    | NNNN            |        |                   |             |              |       |                |
| Code T                               | ype :          |                 |    | Indiv           | Index. |                   |             |              |       |                |
| Code A                               | lerts          |                 |    | Indiv           | Indix  |                   |             |              |       |                |
| FI                                   | 12             |                 | F3 | E-4             | 1.5    | Fo                | F7          | E8 14        | }     | 1.10           |
| HELP                                 | KEY<br>HEL     |                 |    |                 |        | CLEAR TO<br>EMPTY |             |              | 1     | EXIT<br>D MAIN |

Figure 1.The first programming screen for the Bravo Plus includes some superfluous information that has little to do with the operation of the pagers.



Figure 2. The second programming screen offers a 'beep on bad data' option. More on this in the text. Additional clock options are not vital.

mer presentation, actual differences between the IBM-compatible computer hookup and the Bravo programmer are minor, as far as data handling is concerned.

As described in "Servicing Pagers: Microprocessor Board" in the November 1994 issue, there is a definite pattern to the Bravo programmer. First, you define whether to program POCSAG or Golay information; then you look for NORMAL or INVERTED data handling, and so forth.

With the Bravo Plus and Bravo Express, this "fill in the blanks" form of programming gets muddled. Suddenly, there is room for serial numbers, passwords, meaningless frequency information, clock options and cadenced tone alerts—none of which has anything to do with the operation of the pager! Bells and whistles!

As you fill in the various pieces of information, a "string" of information is created for downloading into the pager's codeplug. Pieces of this "string" will be placed into specific program locations where they will be used to perform individual tasks.

I mentioned that much of the information filled in at the computer is just so much junk as far as the paging operation is concerned. With a crystal-controlled pager, there is no point in identifying operating frequency—it is nice to have but not necessary. Clock options are other "nice to have" features, but they are not terribly vital—but I have made my point.

Once programmed, the pager operation resolves itself to performing specific tasks at certain well-defined times. When initially turned on, the whole system performs a reset, clearing the memory, performing self-testing functions and resetting the clock display. Capcode information is downloaded from the codeplug into

Ludvigson is a technician in Houston.

the proper memory location, the receiver "on-time" cadence is determined by the POCSAG data rate information, and the audio filter is activated to pass the data stream information at the selected speed.

The receiver is enabled for a specific period during each BATCH transmission. This is a function of the CAPCODE. If, during the BATCH, the CAPCODE is matched, the information contained in the following 32 bits transfers to the microprocessor. Decoded, these bits form the numerals that are passed to the display.

When the data matches the CAPCODE, several operations occur. First, the cadenced tone generator sounds (while the phone number is being decoded). Clock information is stored to indicate the hour at which the page arrived at the pager. In this manner, two memory locations are occupied and sequentially accessed via the gray (READ) push-button.

If the user wishes to LOCK the information in the pager, a form of "scratch-pad" memory stores the number and time in the next available scratch-pad slot. The LOCK key serves to latch or to unlatch this data, and a padlock symbol appears in the display to indicate saved data. Unlike the

#### Pager servicing series

- Part 1: "Build a Shielded Room," January 1994. (All pagers.)
- Part 2: "Build an 'IFFER,'" February 1994. (Bravo, Bravo Plus, Bravo Express.) Part 3: "Frequencies, Coding Formats,"
- March 1994. (Bravo.)
- Part 4: "From Bench to Programmer," April 1994. (Bravo.)
- Part 5: "The Receivers," May 1994. (Bravo.) Part 6: "Elegant Simplicity," June 1994. (Bravo.)
- Part 7: "Problems in Paradise," July 1994. (Bravo.)
- Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)
- Part 9: "150MHz Receivers," September 1994. (Bravo.)
- Part 10: "Tales Crystal Filters Tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.) Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and Some Aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)


Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)


Part 15: "And You Shall Receiver Knowledge ...," June 1995. (Bravo Plus, Bravo Express.)

Part 16: "The Information Highway," July 1995. (Bravo Plus, Bravo Express.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. Individual photocopies of articles printed since January 1987 can be ordered from UMI Information Store, 800-248-0360.

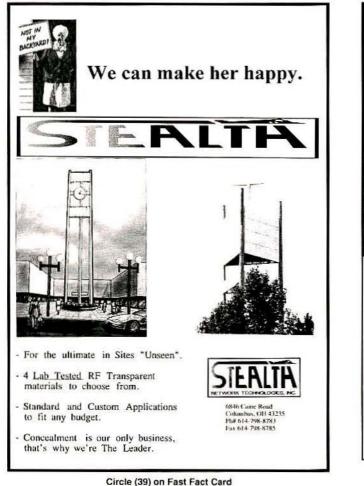Bravo, the Bravo Plus and Bravo Express do not necessarily drop memory contents when the power is turned off. Instead, they offer a CLEAR function to erase those numbers that are UNLOCKED. The majority of functions found in the Plus and Express are virtually identical to those of the Bravo. (See "Servicing Pagers: "The Receivers," May 1994 issue.) The receiver boards differ in that the



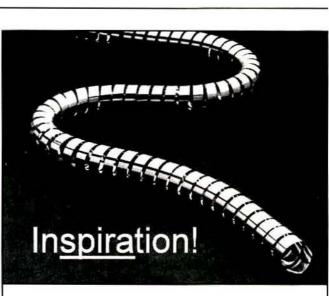

### Spira EMI Gaskets

The EMI gasket you see here is our Quick-Shield, which is ideal for meeting FCC requirements at a very low cost. We also have many other gaskets to solve other EMI and environmental sealing problems.

Call us today for your free color brochure!

12721 Saticoy Street S., N. Hollywood, CA 91605 Tel: 818/764-8222, Fax: 818/764-9880

Circle (40) on Fast Fact Card

Spira

# SUMMIT is a down to earth approach to reaching for the sky.

SUMMIT is an experienced contractor specializing in tower and civil construction work.

- Turnkey Tower Construction
- Civil Construction
- Antenna System Installation
- Specialty Fabrication
- Maintenance
- Trouble Shooting

### CALL 1-800-327-8902



Circle (42) on Fast Fact Card Mobile Radio Technology July 1995

48

| Motorola B<br>Bravo Exp<br>Page 1 of 1<br>Read paget | ress V<br>5 | er. R | 03.00.00          |              |    | Enter characters. PG Up/Dn for Menus |    |    |    |             |  |  |
|--|-------------|-------|-------------------|--------------|----|--------------------------------------|----|----|----|-------------|--|--|
| Inventory Control #                                  |             |       |                   |              |    | Serial #234EUC3WWX                   |    |    |    |             |  |  |
| Synthesized  | l Pager     |       | No                |              |    |                                      |    |    |    |             |  |  |
| Frequency  |             |       | 931.28758         | 1Hz          |    |                                      |    |    |    |             |  |  |
| Phone Number Screen                                  |             |       |                   |              |    |                                      |    |    |    |             |  |  |
| Coding For   | mat         |       | POCSAG 1200       |              |    |                                      |    |    |    |             |  |  |
|  |             |       | Code A<br>0408196 | Code<br>None | В  |                                      |    |    |    |             |  |  |
|  |             |       | 1234              | 1234         |    |                                      |    |    |    |             |  |  |
| Active   | Y.N         |       | YYYY              |              |    |                                      |    |    |    |             |  |  |
| Functions  | T.N.O       |       | NNNN              |              |    |                                      |    |    |    |             |  |  |
| Priority   | Y.N         |       | NNNN              | -            |    |                                      |    |    |    |             |  |  |
|  | F2<br>KEY   | F3    | 14                |              | F5 | F6<br>CLEAR TO                       | F7 | F8 | F9 | F10<br>EXIT |  |  |
|  | HELP        |       |                   |              |    | EMPTY                                |    |    |    | TO MAI      |  |  |

Figure 3. The first programming screen for the Bravo Express specifies the operating frequencynice, but not necessary for a crystal-controlled pager.

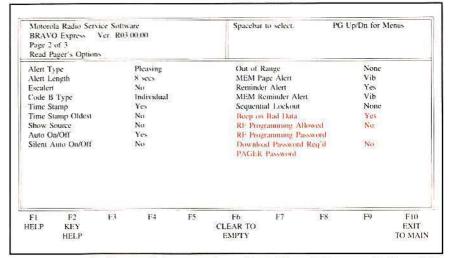


Figure 4. 'Beep on bad data: yes' helps to reveal reception problems. 'RF programming' is available on the Bravo Express; see text about 'RF downloading.'

| BRAVO Exp<br>Page 3 of 3                                 | io Service Sol<br>ress Ver. R<br>Pleasing Alert | 03.00.00                                  |   |                        | Spacebar to                  | select. PG T   | p/Dn for N                        | lenus   |
|--|---|---|---|------------------------|------------------------------|--|-----------------------------------|---|
| ALERT I :<br>ALERT 2 :<br>VOLUME<br>CODE A :<br>CODE B : | LOUD<br>Address 1                               | ALERT<br>ALERT<br>ALERT<br>ALERT<br>ALERT | 2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2 |                        | ALERT 2 and<br>addresses. AI | lows you to a<br>d then assign<br>.ERT 2 is the<br>'LOUD' or | the two ale<br>power-up<br>NORMAL | easing alert for<br>rts to the<br>alert. You may<br>alert level for |
|  | Address 3<br>Address 4                          | ALERT<br>ALERT                            | 222                                       |                        |                              |  |                                   |   |
| FI F2<br>HELP KET<br>HEL                                 | Y   | F4  | F   | S F6<br>CLEAR<br>EMPTY |                              | F8   | F9                                | F10<br>EXIT<br>TO MAIN  |

Figure 5. The third programming screen for the Bravo Express allows a selection of loud or normal alert levels.


# HIGH Q FILTERS

- Low loss
- Broad frequency range 30-950 MHz
- Single, double & triple cavities for spot or wider band attenuation
- Excellent power handling & temperature stability
- Field tunable

For more information, request our data sheets for HIGH Q FILTERS.



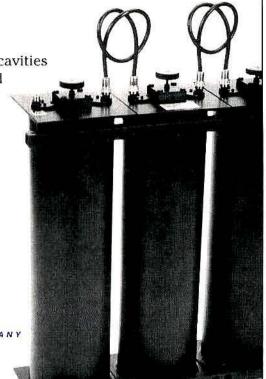MICROWAVE FILTER COMPANY 6743 KINNE STREET EAST SYRACUSE, NY 13057 800-448-1666 • 315-437-3953 FAX: 315-463-1467



Circle (44) on Fast Fact Card

# **DC-TO-AC INVERTERS**

1000 VOLT-AMPERES IN 3.5" VERTICAL RACK SPACE

MODEL 1654-48-120-60-U

- 120 VAC, SINGLE PHASE OUTPUT
- 24, 48 AND 130 VDC INPUTS
- 500 AND 1000 VA MODELS
- 19" OR 23" RACK MOUNTABLE
- OPTIONAL INTEGRAL TRANSFER SWITCH PERMITS OPERATION IN UPS/STANDBY MODES

### Wilmore Electronics CO., INC.

PO Box 1329, Hillsborough, NC 27278 • Telephone: (919) 732-9351 FAX: (919) 732-9359 Bravo uses an external resistor-capacitor (RC) data filter, whereas the Plus and Express use a two-port, selectable-bandpass active filter within the detector integrated circuit (IC). Attempts to use the Bravo and Plus/Express receiver boards interchangeably will result in frustration. They are not compatible.

#### **Express programming features**

The Express program has several options that may be confusing to the firsttime user. "RF downloading" is a feature that has found favor in the alphanumeric pager business because it allows the same transmitter that has been transmitting stock price information from Dow Jones to turn off any selected customer's capcode by sending the proper preamble and text. It controls service delivered to a late-paying user. Similarly, the RF-downloading feature may be used to select any of a number of datastreams (e.g., paging, stock prices or sports scores) to be decoded at the pager.

Current technology could easily provide paging companies with such ability. Such service is not supported in the Express, though, so any selections made in the "RF downloading" option are ignored by the pager. It is just as easy for the paging company to enable or disable an individual capcode at the switchboard.

Another feature of the program is the "beep on bad data." In areas where simulcast signals overlap, the possibility of phasing differences causing an imperfect match of the capcode exists. When the signal strength is relatively weak, the Bravo family of pagers often is willing to decode "bad" data. Received pages are solid when signal strength and phasing are favorable, but the letter "E" creeps into messages under unfavorable conditions—also when the receiver is out of alignment.

If the "beep on bad data" is left off (BBD=N on the Bravo), count on customers complaining of missed pages. I would rather have customers tell me they are getting "E's" in their messages than to have them miss them entirely. A few minutes on the alignment bench might be all that is required to restore proper operation.

#### Acknowledgement

I would like to thank the management and staff of JJ Sounds and Communications, South Houston, TX, for their help with this project. Tel.: 713-944-1813.

圈

Circle (45) on Fast Fact Card

August 1995



The journal of mobile communications technology

### Communications centers, p. 10

- Site management
- Servicing pagers
- Radio equipment removal
- APCO preview

in Promotion

# Servicing pagers: 450MHz receiver boards

Part 17—Here are some details about the inner workings of UHF Bravo Plus and Bravo Express receiver circuitry. Use an 'unknown' feature during extensive troubleshooting of the circuit boards.

#### By David Ludvigson

The lady came up to me quietly with a furtive look, "Can you fix this?" she whispered.

I looked at the pager in her hand. It was a Bravo Plus, or at least the circuit boards that make up the Bravo Plus. Neatly sandwiched between the front lens and the light diffuser were the remains of the liquid crystal display (LCD), its flex-strip curl-

Ludvigson is a technician in Houston.

ing lazily at the bottom of the case.

*Rule 1.* When disassembling a Bravo Plus to make any repairs, remove the diffuser lens by placing a jeweler's screwdriver between the screw retaining post and the edge of the diffuser lens, and gently "rock" the screwdriver to release the friction-fit part. Forcing the circuit boards out of the case without performing this step results in much unneeded cost and frustration!

Logic and receiver board removal then may be accomplished by the same technique used for the Bravo pagers. (See Figures 1 and 2 below.)

The NRE series of Motorola Bravo Plus

and Bravo Express receiver boards for 406MHz-512MHz includes:

| NRE6550B | 45MHz IF | 406MHz-423MHz |
|----------|----------|---------------|
| NRE6551B | 45MHz IF | 435MHz-450MHz |
| NRE6552B | 45MHz IF | 450MHz-465MHz |
| NRE6553B | 45MHz IF | 465MHz-480MHz |
| NRE6552A | 45MHz IF | 450MHz-465MHz |
| NRE6553A | 45MHz IF | 465MHz-480MHz |

Figure 3 on page 22 illustrates the parts and functions of the receiver boards. See the appropriate Motorola technical manual for a complete schematic.

Q451 and Q452 are configured as a cascode amplifier, capacitively coupled to

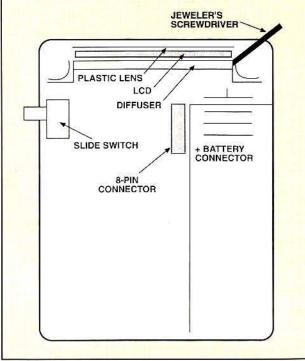


Figure 1. Step 1: Turn the pager off. Remove the battery clip at the bottom of the case, and remove the battery. Insert a jeweler's screwdriver at the edge of the diffuser lens to remove it.

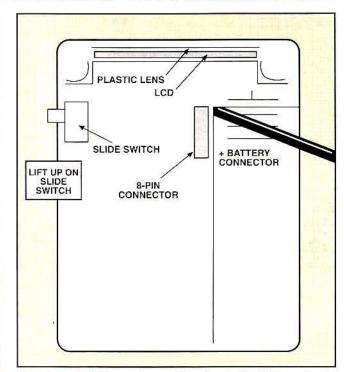


Figure 2. Step 2: With a small screwdriver placed at the "L" formed by the circuit board (to the left of the positive battery spring) and while lifting the lever of the side-mounted *on-vibrate-beep* switch, gently wedge the entire unit from the case.


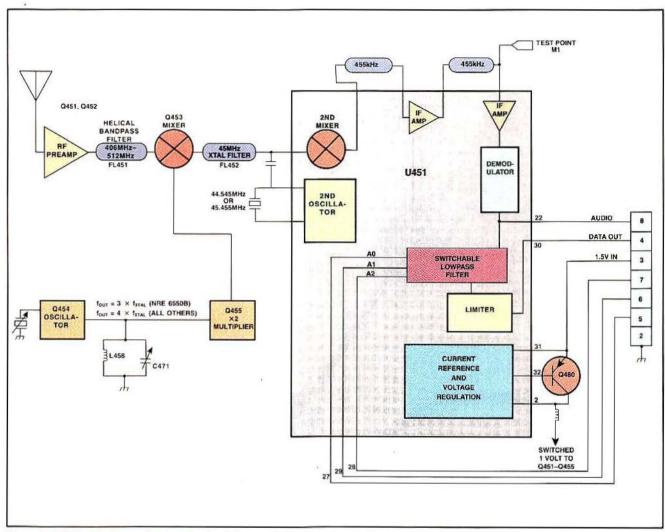


Figure 3. 406MHz-512MHz receiver boards. See text for multiplier operation details.

the loop antenna. Diode CR451 prevents damage by clamping any excessive signal levels to ground. The resulting amplified 406MHz-512MHz signal is injected through FL451, a helical filter generally broad enough to pass a 15MHz range without significant band-edge attenuation. The preamplified and filtered signal is then presented to the base of Q453, the first mixer.

At the same time, Q454 operates as a Colpitts crystal oscillator with a bit of L455 slug-tuning applied. This tuning allows the crystal oscillator to be centered at the required frequency to decode the paging signal properly. (See "Tales Crystal Filters Tell ..." in the October 1994 issue.) The Q454 output is actually either three or four times the crystal frequency. In the NRE6550B, the values chosen for Q454's collector resonate at

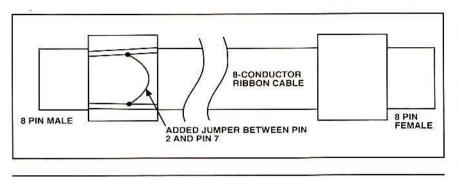



# Choose from Two Headset Systems



#### VOX System

#### NOISE-ATTENUATING HEADSETS WITH VOX

A built-in Voice-Activated (VOX) module allows clear, "hands-free" transmission in noisy work areas. A short radio adapter cord connects directly from a Series 7200 Headset to your portable two-way radio.

- Noise-canceling microphone. either boom-mounted or throat mic
- Headset noise reduction rating of 24 dB

### Push-to-Talk System

#### **NOISE-ATTENUATING HEADSETS** WITH PTT (Push-to-Talk) **ADAPTER CORDS**

The PTT Adapter attaches to belt or clothing and acts as an interface between Series 7000 Headsets and your portable two-way radio. Choose from eight headset models for your particular application.

- Noise-canceling microphone
- Headset noise reduction rating of 24 dB

Adapter cords available for all two-way radios. For more information and a Free Demonstration, call or write:



#### Figure 4. Modification to extender cable for Bravo Plus and Express pagers (not for Bravo). See text for details.

roughly three times the crystal frequency. All other NRE-series receivers are tuned to four times the crystal frequency.

Capacitively coupled, this three-or-four times crystal-frequency signal is applied to another filter (L458 and C471) that removes virtually all other frequencies besides the multiplied signal output. Q455 operates as a frequency doubler, yielding an overall output frequency of either six or eight times the crystal frequency. This signal is also applied to the base of mixer 0453.

Q453 (in the case of a NRE6552B) receives an oscillator frequency of eight times 50.6363MHz (405.09MHz) and an incoming range of frequencies that is determined by the bandwidth of the 450MHz-465MHz helical filter. Limited to a crystal frequency of 45.0MHz for the center of its response, signals around 405.09MHz + 45.000MHz = 450.09MHz are passed for further processing and decoding.

The crystal used for the second oscillator should be color coded brown for 45.455MHz and violet for 44.545MHz. The 45.455MHz version probably will require data inversion. (Respond YES to the programmer when the CUSTOMER RE-QUIRES DATA INVERSION prompt appears.) The 44.545MHz version probably will not require data inversion. In either case, tune the crystal frequency for the first strong peak on the IFFER as the slug is tuned clockwise into the core. (Again, see "Tales Crystal Filters Tell ..." in the October 1994 issue.)

Capacitive coupling is used to feed the second oscillator output into the second mixer within "jungle chip" U451, so called because of its complexity. At this point, the signal passing through FL452 is mixed with the second oscillator output to produce an output of 455kHz. This 455kHz signal is amplified through a pair of intermediate frequency (IF) amplifiers. and then demodulated by a quadrature detector. Audio output is brought out through the chip's pin 22 and also presented to the switchable lowpass filter. Line A2 (pin 28) is enabled by the battery-save strobe. Lines A0 and A1 (pins 27 and 29, respectively) control the bandpass characteristics of the signal that reaches the limiter. The signal is subsequently processed as output data.


There is an undocumented (and virtually unknown) feature of the Plus and the Express that may help you if you conduct

Circle (19) on Fast Fact Card

extensive troubleshooting on either circuit board. On the jumper-cable used to interconnect these boards, place a jumper between pins 2 (ground) and 7 (A2) as shown in Figure 4 on page 24. This jumper allows the receiver to operate "full-time" while the microprocessor continues to perform all of its "housekeeping" and "decoding" chores. An on-frequency POCSAG signal with a matching capcode and baud-rate will cause a "full-response" (alarm active for length of time determined when programmed). When troubleshooting, this utility should be of considerable value.
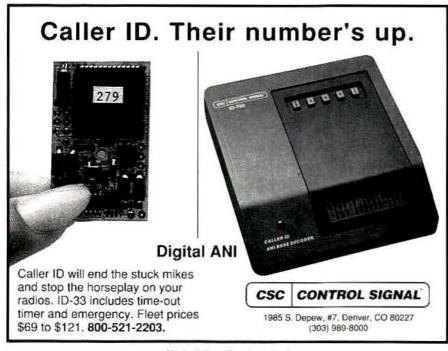
#### To this point ...

Many telephone calls have been received regarding some of the pagers that have been troublesome. One complaint is that there is a strong signal at test point M1 but no subsequent decoding. Test



Circle (21) on Fast Fact Card



point M1 is far removed from the actual demodulating stage (as shown in Figure 2). It is certainly possible to have a perfectly working "receiver" at 455kHz but nothing coming from the demodulator or audio stages. I use a dual-trace scope to look at what is available for both audio and data (pins 8 and 4 on the Plus and Express receiver boards' interconnect block). That "jungle-chip" does not stop at the IF! Keep a few test receiver and decoder boards around and try replacing suspected faulty boards with known good boards. If the signal at M1 looks good but decoding does not take place until the receiver board is replaced, then the demodulator or signal-processing section of the jungle-chip is falling down. Often, this failure may be traced to a loose chip capacitor or resistor.

Another problem is locating the operations frequency of some pager with its crystal-frequency marking positioned away from a viewing plane. The Ramsey Com 3 service monitor provides a programmable offset frequency, which I have set to 0.0250MHz for all pager frequencies. Merely putting the Ramsey into generate mode with a 1kHz tone allows me to sequentially move the frequency up or down in 0.0250MHz steps. This single feature of the Com 3 has saved countless hours of removing crystals and performing the math to calculate the operating frequency! On the Com 3, press CLR, enter .0250, press STO and OFFSET +. The same offset is useful on 450MHz. A tip of my hat to Ramsey!

There also has been mention of the "single-board Motorola pagers." These pagers basically are early versions of the two-board Bravo units and may or may not be worth the time to explain. To program them, select "BAB" on the programmer. To get them to work properly usually requires setting them for data inversion (DI=Y). The operating frequency is marked on the voltage-controlled oscillator (VCO) module on the rear side of the board. The chart provided in "Servicing Pagers: Frequencies, Coding Formats" (March 1994 issue) indicates the coding language and speed of the various decoder chips. I have not spent enough time to decide the various test points or what they signify in these "oldtimers.'


Motorola has introduced a conversion for the Bravo programmer that everyone will find valuable. This conversion consists of a new "ground" pin that physically connects to the logic board's negative battery tab and some new software to program the POCSAG "blob-chip." Newer versions of the decoder chip are no

Circle (22) on Fast Fact Card

longer covered with a ceramic "lid"; instead, they are covered with an epoxy-filled "blob." These chips *may or may not* be programmable using the unmodified programmer. Different voltage levels are used to program the codeplugs. Modifications are performed at all Motorola pager service centers.

One further note regarding the "missing page" problem. Everything in the Bravo family of pagers allows a choice for a function known as "beep on bad data" (BBD on the Bravo). Invariably, I set this function to YES because it defeats the need for a perfect checksum before displaying a message. This is enough to compensate for bad reception associated with signal overlap and weak signals. More on this next edition.

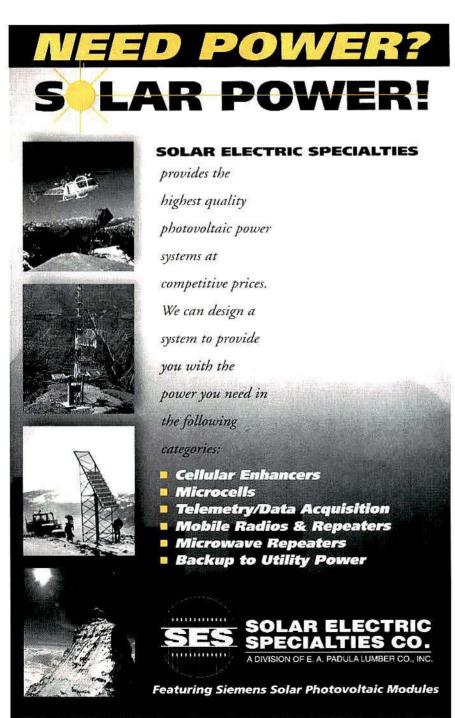When the pager is set this way, the message display degenerates to a string of Es when the receiver board drifts off fre-



P.O. Box 537, Willits, CA 95490 Phone: (707)459-9496 Fax: (707) 459-5132 Toll Free: (800) 344-2003 Circle (24) on Fast Fact Card quency or becomes nearly deaf to the transmitters. At the service bench, we either realign the oscillator and check the antenna tuning or replace the entire receiver board with a good one.

#### Acknowledgement

I would like to thank the management and staff of Toltec Communications Resources, Pasadena, TX, for their help with this project.

#### **Pager servicing series**

Part 1: "Build a Shielded Room," January 1994. (All pagers.)

Part 2: "Build an 'IFFER,'" February 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 3: "Frequencies, Coding Formats, March 1994. (Bravo.)

Part 4: "From Bench to Programmer," April 1994. (Bravo.)

Part 5: "The Receivers," May 1994. (Bravo.)

Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems in Paradise," July 1994. (Bravo.)

Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Part 9: "150MHz Receivers," September 1994. (Bravo.)

Part 10: "Tales Crystal Filters Tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and Some Aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)

Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)

Part 15: "And You Shall Receiver Knowledge...," June 1995. (Bravo Plus, Bravo Express.)


Part 16: "The Information Highway," July 1995. (Bravo Plus, Bravo Express.)

Part 17: "450MHz Receiver Boards," August 1995. (Bravo Plus, Bravo Express.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. Individual photocopies of articles printed since January 1983 can be ordered from the UMI Information Store, 800-248-0360.

硇

28

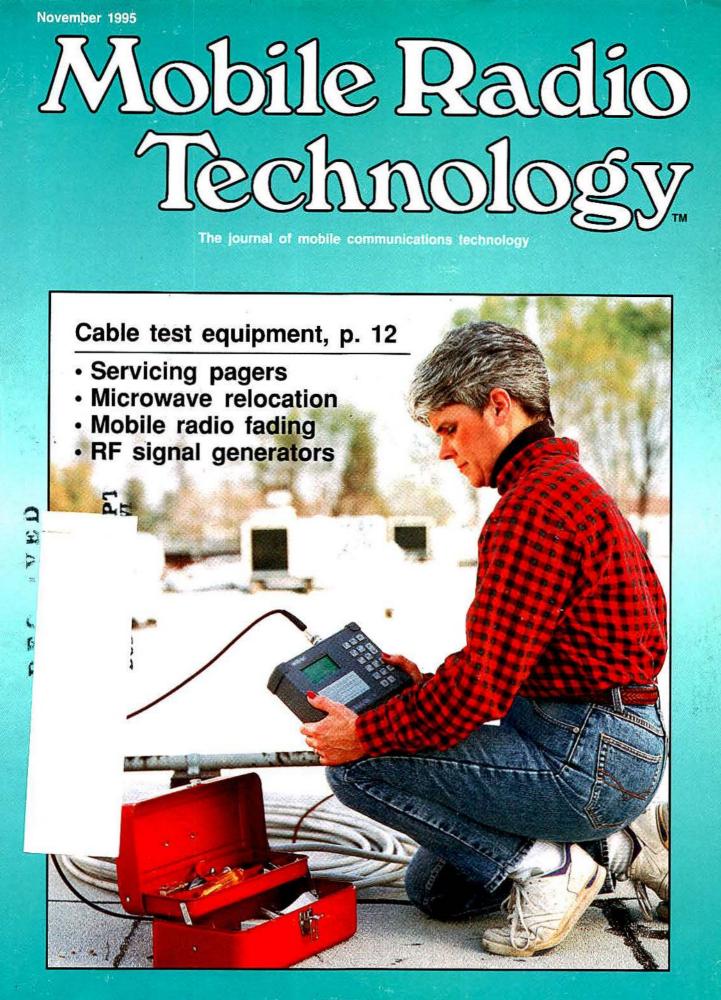

# Servicing pagers: Logic/decoder boards for Bravo Plus, Bravo Express

Part 18—Circuit descriptions unlock some of the mysteries about Bravo Plus and Bravo Express pagers. Miniaturization may defeat some repair attempts, but other faults can be remedied in a well-equipped service shop.

#### By David Ludvigson

The November 1994 article "Servicing Pagers: Microprocessor Board" introduced you to the Motorola Bravo pager's logic board. With that information as a background, this article covers the Bravo Plus version of the same board. Part number references can be found in the appropriate Motorola technical manuals.

#### The 'wake-up call'

As the Bravo Plus is first activated, a RESET is performed at pin 78 of the mi-

Ludvigson is a technician in Houston.

croprocessor (U025). This pin is held "low" for the time it takes to charge capacitor C5, and this "master RESET" causes the entire pager to perform the following operations:

(1) The power supply and voltage doubler circuitry is enabled. This action provides the 3V power to operate the entire microprocessor and logic functions.

(2) Once the 3V supply is operating smoothly and verified by proper operation at U023, the clock oscillator should be churning out a signal at 38.4kHz (pin 71, U025).

(3) With the 38.4kHz clock signal operating and the RESET invoked, the microprocessor address counter is reset to the lowest register. Each subsequent clock

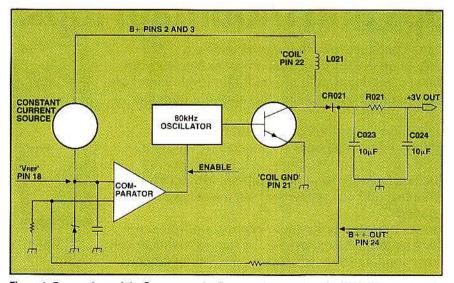


Figure 1. Few portions of the Bravo pager family are as important as the U023 3V power supply shown in this block-and-equivalent circuit diagram. This supply maintains the operating voltage for the microprocessor and logic circuitry. Without it, the pager would be nothing more than a radio receiver.


cycle (coming through an appropriate divider network) moves the operating system up, one notch at a time, through a copyrighted Motorola program. Although no portion of that program is divulged here, it is possible to observe several functions and to identify "what occurs when" to help with troubleshooting this remarkable board.

As the wake-up call proceeds, information stored in the codeplug (U024) is transferred from pin 2 of U024 to pin 2 of the microprocessor (U025), where the data are stored in various registers located in U025. This information includes everything that was programmed using the software, along with some mathematically derived information. More on this in a bit (or is it "byte"?).

Once the information transfers from the codeplug, the clock moves through each succeeding register, performing each software instruction located at each register. These instructions include testing the current position of various switches, testing battery status, testing 3V level status, resetting the "wake-up" for the liquid crystal display (LCD) to display a full-segment load of 12 digits, and then settling down to a time display in the window. The characteristic "four sets of two chirps" and the flash of DS021 round out the light-and-trumpet show, and the Bravo Plus is ready to begin its day.
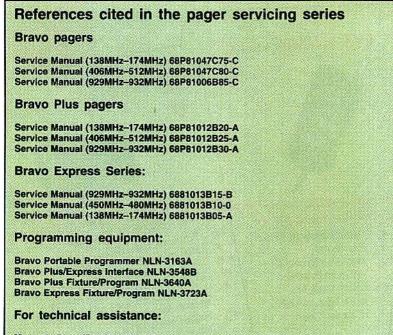
#### The 3V power supply

Few portions of the Bravo pager family are as important as the 3V power supply. (See Figure 1 to the left.) This supply maintains the operating voltage for the microprocessor and logic circuitry, and without it the pager would be nothing more than a radio receiver.



Motorola Parts ID, 800-422-4210 Motorola Technical Assistance, 800-548-9954 Motorola Repair Center/DFW Pager Repair 1701 Valley View Lane, Suite A Farmers Branch, TX 75234 214-241-1891 The "internals" of U023 contain a switchmode power supply. Essentially, a switchmode power supply is an energy transfer method. The flux energy stored in an inductor is added to energy already present on a dc power rail, using a technique called *step-up mode*.

In the case of the Bravo Plus, an oscillator operating at about 80kHz is gated to provide driving current to an output transistor. As configured, energy stored in the external inductor (L021) is momentarily placed in series-aiding mode with the source voltage of 1.5V. As the transistor is toggled, energy is alternately stored in L021 as the transistor saturates, and then placed in *series-aiding* mode with the source voltage as the transistor comes out of saturation. The toggled 80kHz square wave is rectified by CR021, filtered by a 10µF capacitor (C023), and decoupled by R021 and C024, providing a little more than 3V output.

The B++ output is deceptive—this is not the actual output of the supply, but a means of resistive tapping to provide a reference feedback voltage to be compared at the voltage reference ( $V_{REF}$ ), pin 18, U023. An internal comparator is constantly checked and toggled to cause the 80kHz oscillator



Circle (13) on Fast Fact Card

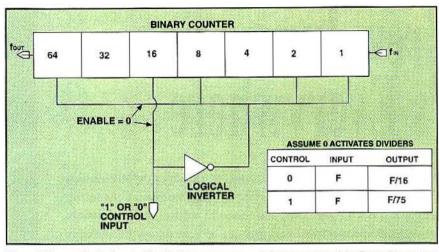


Figure 2. One method of control for the binary counter and divider stages of the Bravo Plus pager.

to provide adequate signal to keep the charge-discharge cycle across L021 operative and to maintain the required output voltage. Overall, this is a sophisticated supply, but it cannot handle much output current.

#### Meanwhile, back at the

microprocessor . . .

Remember the information loaded from

the codeplug contains both *instructional* and *mathematically derived* data. The instructional data contain responses programmed to such prompts as BEEP ON BAD DATA Y/N or SILENT MODE CHIRP Y/N. These instructional data represent bit patterns that are simple yes/no instructions.


The mathematically derived information is dependent on the capcode entered and (to some extent) by the baud (actually, bits per second [bps]) rate selected in the first screen of the programming session. As described in the November 1994 article, the capcode *mathematically* determines which *frame* will be used to seek the capcode.

In the case of the Bravo Plus and Bravo Express pagers, the baud (bps) rate also determines a division ratio that places the pager in a synchronous mode compatible with the selected POCSAG data rate.

The choice of 38.4kHz for the clock oscillator was *not* arbitrary. When divided by 75, the resulting frequency is 512Hz; when divided by 32, the resulting frequency is 1,200Hz; and when divided by 16, the resulting frequency is 2,400Hz. In any of these cases, a simple binary divider would suffice nicely to provide an accurate time base to match the baud rate of a POCSAG signal. (See Figure 2 above left.)

Those familiar with programming the Plus and the Express have long been familiar with the fact that some versions program to 512 baud or 2,400 baud, but not to both, and all of them program to 1,200 baud.

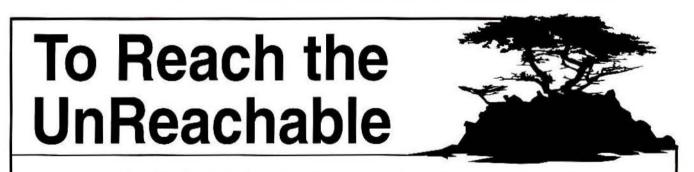This difference is because one version of the microprocessor has both a divide-



## Beyond wire, beyond cells, Zetron radio telephony controllers give you cost-effective, wireless telephone service in remote locations.

A normal touch-tone telephone is all that's needed to place and receive calls into the public telephone system. No special procedures are needed. Just lift the handset and receive dial tone!

#### Model 72 Extend-a-Line

A pair of Model 72s establishes a dedicated full-duplex link from the end of the phone line out to a remote location. Companding ensures premium audio quality.



#### Model 71 Remotaphone

Simply install a Remotaphone and touch-tone telephone in each remote spot. Your DTMF-signaling phone patch can support multiple Remotaphones, so

you can have low-cost telephone service anywhere. Works great with full-duplex or simplex radios!



Call today and ask for our brochure,

"Rural Radio Telephony Solutions from Zetron."

Zetron, Inc. 12034 134th Ct NE, PO Box 97004 Redmond WA 98073-9704 Phone: (206) 820-6363 Fax: (206) 820-7031

Circle (15) on Fast Fact Card

by-75 and a divide-by-32 binary counter, although another version contains the divide-by-32 and the divide-by-16 binary counter. In both cases, the division ratio may be set with either a 1 or a 0 controlling the clock's output frequency. (See Figure 2.)

Further housekeeping chores (e.g., 12/ 24-hour time displays and vibrator on-off functions) are directed to specific addresses within the processor's memory map to be performed at the appropriate times.

#### The 'I'm looking for it' mode

Once past the wake-up mode, the pager goes into an alternating on-off mode, turning the receiver board on briefly and then turning it off. The length of on-off timing is governed by the bps (baud) rate determined at the programmer and is directly controlled by the di-

## Beyond a Shadow of a Doubt, the Industry's Best Kept Secret

While most everyone in the industry knows Midland for its high quality 2-way radio equipment, some may not be aware that we have been designing and installing special wireless communication systems for over 20 years.

As the industry's needs have grown, so too has Midland's dedication to providing the wireless-based integrated conventional and trunked control systems so vital to meeting today's complex demands. Starting with a line of base station and repeater products that rank among the best in the industry, we're building systems to handle dispatch, resource control and operational requirements using advanced techniques including simulcast, voting and stackable system options.

> Midland Systems, with its wealth of experience and cutting edge technology, is dedicated to wireless solutions tailor-made to fit customers' needs. As a full service systems integrator, we can design and deliver turn-key systems, including engineering, propagation modeling and terrain analysis, spectrum management, equipment acquisition, project management, testing and maintenance.



Call or FAX for complete details. 1-800/MIDLAND Ext. 1690 FAX: 816/920-1144 In Canada: 905/420-4102 FAX: 905/420-5848

... We're in the Systems Business.

Supporting the APCO 25 Project

vision ratio just discussed.

The pager is looking for two basic signals, either the alternating "1010 ...," 576bit repetition signaling the beginning of a POCSAG transmission or the unique, 32bit "word" that contains the *frame sync code*. If the "1010 ..." sequence is found, the pager responds by lengthening the receiver's *on* time. If the *frame sync word* is found, the pager immediately resets the *frame counter* to zero and turns *on* at the *frame* appropriate to the capcode programmed to that pager.

Each *frame* (1 through 8) contains 64 bits organized as 32 bits for *capcode* and *parity*, and the following 32 bits contain the remaining information that will be displayed as a message, plus the same check sum.

The *capcode/parity* portion starts out with the first bit always being a zero. Bits 2 through 19 contain the capcode, and bits 20 and 21 identify the "source" of the pager call (a throwback to the day when pager calls were identified by the letters A through D to identify who was calling). It is the remaining bits' function (bits 22 through 32) to report parity tests performed on the message. These tests are used at the pager to verify accurate message reception.

If the values in these last 10 bits are not matched by the parity values received at the pager, the message is then turned over to a decision made at the programmer. BEEP ON BAD DATA = N prevents any response from the pager. BEEP ON BAD DATA = Y allows the message to be displayed with the letter E filling whatever portion of the message that did not match the calculated parity values.

It was mentioned earlier that the "1010 ...," 576-bit alternating *preamble* sequence of the POCSAG signal is monitored by the receiver. The speed at which this sequence is sent *must* be matched by the receiver to provide synchronous detection. Unless the receiver "sees" the alternating "1010 ..." preamble sequence, it remains in its "relaxed" on-off cycle, waiting for something to happen.

Similarly, if the *frame sync* happens to be sent at the same time the pager receiver is on, a proper decoding of the frame sync signal immediately resets the *frame counter* to zero and turns the pager receiver on again at the appropriate frame. Unmatched baud rates prevent the pager from responding to any portion of the frame sync or preamble signals.

#### The 'Storing it away!" mode

Upon receiving and properly acknowledging a page, the pager transfers



MODEL NC409

The

Model NC409 is a DTMF ANI/Alarm status encoder and companion product to the Model NC401 DTMF Decoder designed to automatically or manually generate any of the 16 DTMF characters. The NC409 features 15 memory locations of up to 30 digits each plus last number redial and multiple user-configurable functions. Programming is easily performed by means of a 12 or 16 button "X-Y" keypad with common ground or the Model NC500 Universal/P.C. programmer. The NC409 measures .85"W x 1.36"L x .165"H and comes complete with micro-miniature 14 pin header and 12° color coded cable assembly. For FREE detailed information ask for the NC409 user's manual.

For detailed information or product catalog call 1-800-874-8663 or Fax 916-477-8403



Circle (17) on Fast Fact Card

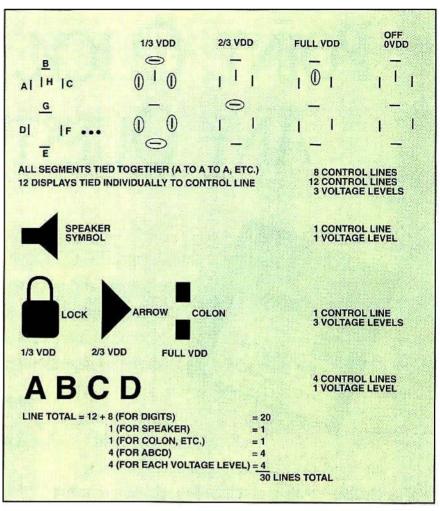


Figure 3. The liquid crystal display (LCD) consists of 12 eight-segment displays, eight specialfunction displays (arrow, speaker, lock, colon, A, B, C and D) and the "wake-up" display (all segments, all displays). These displays are controlled by 30 active connections between the output of the microprocessor and the display.

the 32-bit message to electronic memory, where it is stored in RAM (random access memory). The RAM has enough capacity to store 16 numbers plus the arrival time of the page. If it may be assumed that 32 bits are used for the message, and 32 bits are used for the time-clock, then a 64 bits would be used for each message-clock combination. With 16 message-clock combinations, 1,024 bits would be needed in RAM to contain all of the messages. When the memory is full, an overflow message is generated.

Using the lock/unlock feature, several messages may be "locked" into memory. This action means that the remaining "unlocked" memory is used to handle incoming messages, preventing overwrites, Associated with each locked message is a padlock icon, indicating the locked condition. Removing the locked condition involves displaying the locked number or

locked time display and pressing the black selector switch to remove the padlock symbol. RAM performs its own housekeeping by shifting memory contents up to the newly opened space and opening the bottom of RAM memory to allow a new message to occupy the newly opened 64-bit area.

New messages arrive at the Bravo Plus in an unlocked condition but may be maintained in RAM (depending upon how the pager is programmed), in which case the Bravo Plus may be turned off with no loss of messages. It is not until the clear all message is enacted (by pushing the gray push-button) that all unlocked messages are cleared from RAM. All locked messages must be unlocked before they become erasable.

#### Translating and displaying

The display consists of 12 eight-segment displays, eight special-function displays


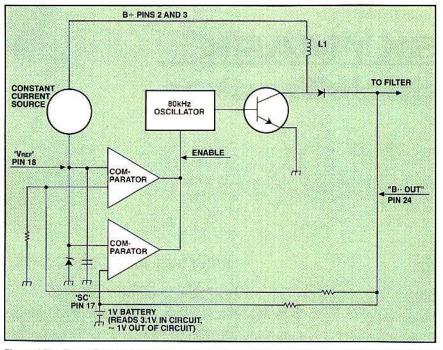


Figure 4.The Bravo Express U2 power supply chip uses an onboard battery to maintain the VCC voltage to the real-time clock when the power has been shut down, as shown in this block-and-equivalent circuit diagram. This single feature allows an internal timer to compare *master on* and *master off* times (set by the user) and to transfer control to or from the AAA-size battery as a source of main power.

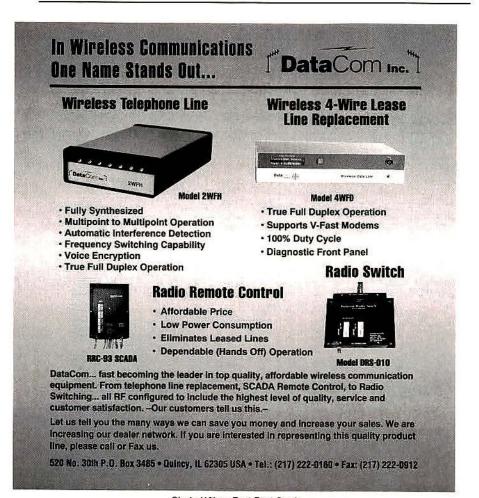

(arrow, speaker, lock, colon, A, B, C and D), and the "wake-up" display (all segments, all displays). These displays are controlled by 30 active connections between the output of the microprocessor and the display.

There are four "backplane" voltage levels and control lines. Individual voltage steps of 0, 1/3, 2/3 and full VDD are applied to these four lines, which activate separate LCD planes within the crystal display. *Zero* equals *off.* 

There are 12 eight-segment displays, Assuming that a typical multiplex arrangement is used, these 12 displays would be controlled by 8 + 12 = 20 lines. These lines are used in conjunction with the four backplane voltages to provide numeric data. (See Figure 3 on page 24.)

The *speaker* display uses a single control line and a voltage level to display the symbol to the screen.

Lock, arrow and colon share a single control line and use the available three levels of display planes to darken the appropriate symbol. Otherwise, the set of displays remains inactive (VDD = 0).

Letters A, B, C and D are controlled by four control lines and a single display plane/voltage level.

The line total equals the following:

12 + 8 (for digits) = 20 1 (for speaker) = 1 1 (for colon, etc.) = 1 4 (for A, B, C and D) = 4 4 (for voltage levels) = 4  $\overline{30}$ 

At best, the schematics are ambiguous ... These are multiplexed displays, which means the average service shop is not going to be able to see (let alone fully diagnose) potential problems with the output from the microprocessor chip. If the display shows "stray" portions of some other voltage level's segments, replacing the contact strip and display often cures the problem. (The conductive ribbon might be touching an adjacent contact next to its own.) LCD replacement requires the proper set of tools and a bit of patience, but being able to do it is often worth the investment.

#### Notes on the Bravo Express

Refer to the appropriate Motorola schematics.

The previous information largely applies to the Bravo Express logic boards with the following exceptions:

First, the power supply chip uses an onboard battery (see pin SC of U2) to maintain the VCC voltage to the real-time


Circle (19) on Fast Fact Card

clock when the power has been shut down. (See Figure 4 on page 26.) This single feature allows an internal timer to compare *master on* and *master off* times (set by the user) and to transfer control to or from the AAA-size battery as a source of main power. Compare the pinouts of U025 in the Bravo Plus with the pinouts of U1 in the Bravo Express. U025 and U1 are the same chip, just loaded with different software. U023 equals U2, and U024 equals U3 but the same programming software does not work on both pagers.

Second, the *Port A* register is configured differently, but this difference is largely just a matter of switch placement and the addition of *mode* and *select* switches to step the user through various features available in the Express.

Third, geographical territory on the logic board is limited. Only someone with a pair
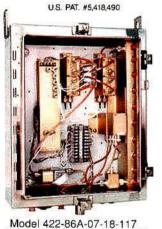
### 422-Series Auto-Backup<sup>TM</sup> Tower-Mounted Preamplifier Systems For the 806-960 MHz Frequency Range




- Auto-Backup system (US and other patents pending) monitors primary preamplifier and switches to backup preamplifier in case of primary failure.
- Secondary preamplifier is normally off-line and isolated from events that would destroy <u>both</u> amplifiers in competitive parallel-connected, "redundant" systems.
- High-selectivity, six- to ten-section combline preselectors for trunking, AMPS and GSM bands in 5, 10, 12.5, 15, 18 and 25 MHz bandwidths.
- Multiple power supplies with automatic battery backup for maximum system reliability.
- Ground-level control panel provides positive diagnostic and power backup capabilities via a separate DC cable.

Auto-Backup Tower-Mounted

Preamplifier System

- High-performance bipolar preamplifiers feature low noise figure and high output intercept point.
- High-performance receiver multicoupler output amplifiers have a third-order output intercept point of +43 dBm to assure a large dynamic range.

**Auto-Backup...** The no-compromise receiving system for today's world.

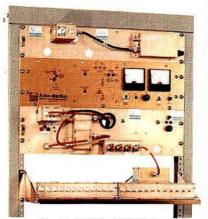

Model 42-86A-42-24-117 24-Channel Receiver Multicoupler with 422-Series Auto-Backup Control Panel and RF Test Panel



MULTICOUPLERS - SIGNAL BOOSTERS DUPLEXERS - CAVITY FILTERS - RF SYSTEM PRODUCTS 8625 Industrial Parkway - Angola, New York 14006 Telehone (716) 549-4700 - Fax (716) 549-4772

TX RX SYSTEMS INC.

of eagle eyes and nerves of steel should attempt repairs to this board!

#### Acknowledgement

I would like to thank the management and staff of Toltec Communications Resources, Pasadena, TX, for their help with this project. Tel.: 713-947-7660.

#### Pager servicing series

Part 1: "Build a Shielded Room," January 1994. (All pagers.)

Part 2: "Build an 'IFFER," February 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 3: "Frequencies, Coding Formats," March 1994. (Bravo.)

Part 4: "From Bench to Programmer," April 1994. (Bravo.)

Part 5: "The Receivers," May 1994. (Bravo.)

Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems in Paradise," July 1994. (Bravo.)

Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Part 9: "150MHz Receivers," September 1994. (Bravo.)

Part 10: "Tales Crystal Filters Tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and Some Aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)

Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)

Part 15: "And You Shall Receiver Knowledge ...," June 1995. (Bravo Plus, Bravo Express.)

Part 16: "The Information Highway," July 1995. (Bravo Plus, Bravo Express.)

Part 17: "450MHz Receiver Boards," August 1995. (Bravo Plus, Bravo Express.)

Part 18: "Logic/Decoder Boards for Bravo Plus, Bravo Express," November 1995. (Bravo Plus, Bravo Express.)

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. Individual photocopies of articles printed since January 1983 can be ordered from UMI Information Store, 800-248-0360.

Editor's note: The final installment in this article series will appear in the January 1996 issue. David Ludvigson has made an arrangement with the publisher such that, when the series is complete, he will offer a compilation of all the articles for purchase. Ludvigson also is preparing a videotape with pager servicing information based on his articles. January 1996

# sile Radio echnology The journal of mobile communications technology

Servicing pagers, p. 10

- Dry air systems
  Snow plow installations
  Product/services showcase

An INTERTEC® Publ

# Servicing pagers: The 'tinfoil tomb'

Part 19—Use aluminum foil to build a do-it-yourself shielded room and overcome oxidation and breakage problems associated with rooms made of copper circuit-board material. Proper earth grounding plays a key role.



Photo 1. This is the northeast corner of an  $\vartheta' \times \vartheta' \times 7'$  room with a fluorescent light fixture near the center of the ceiling. The walls and ceiling are gypsum-board; the floor is 8-inch concrete.

#### By David Ludvigson

"Servicing Pagers: Build a Shielded Room," the first article in this series (January 1994), described a do-it-yourself shielded room made of copper-clad, circuit-board material. I like to call it the "copper coffin," because receivers "die" when they are brought into the room.

Although the original design works well, it is difficult to build. Moreover, extended use has revealed the need for several modifications, and sometimes individual "tiles" of circuit-board material must be replaced for the room to retain effective shielding. Corrosion and the inevitable cracked circuit board require a "minesweeping" exercise with a transistor radio to locate RF leaks.

Ludvigson is a technician in Houston.



Photo 2. Applying the shielding began by hanging 8-foot lengths of 15-inch aluminum foil directly on the wall. Overlapping pieces are stapled directly to the wall with office paper staples.



Photo 3. A hole is drilled through the concrete floor at the northeast junction, and a 4-foot-long,  $5_{\rm fs}$ inch-diameter copper ground rod is driven into the underlying soil for an earth ground connection.

Photo 4. The No. 4 ground wire is bonded mechanically and electrically to the foil at the juncture of both walls and the floor. Foilbacked tape is applied to the entire length of each section's seam.

placed on an 8-inch concrete floor.

Construction began by hanging 8-foot lengths of 15-inch aluminum foil directly on the wall. Overlapping pieces were stapled with office paper staples directly to the wall. (See Photo 2 above.)

At the northeast junction of walls and floor, a single hole was drilled through the concrete and a 4-foot-long, <sup>5</sup>/<sub>8</sub>-inchdiameter copper ground rod was driven into the underlying soil. Without a connection to this ground, the surrounding foil has virtually no effect on receiver sensitivity to AM or FM broadcast stations. If the room is not fully and completely earth grounded, it will not work.

By the way, just because an electrician says a connection to a ground rod is good does not necessarily mean that it is. Photo 3 above shows oxidation around the clamp. Despite an electrician's opinion, the connection was not grounded. The clamp had to be removed, the rod cleaned and the

I directly to the wall with is driven into the unc for an earth ground c The copper coffin's costs were largely absorbed in the acquisition of several pieces of test equipment, but 70 tiles at \$6

absorbed in the acquisition of several pieces of test equipment, but 70 tiles at \$6 per tile (not including the intensive labor) added up to an expensive project. There had to be another way.

Some tests conducted at home used a 4foot cube covered with aluminum foil sold for home use. The cube was connected to an earth ground, and a transistor radio placed within it could not receive a 1kW AM broadcast station three miles away.


The combination of a remodeling project at JJ Sounds and the maintenance problems with the copper coffin led us to try aluminum foil for RF shielding.

Photo I above left shows the northeast corner of a room measuring about  $8' \times 9'$ with an overall height of about seven feet. A single fluorescent fixture mounts in the center of the ceiling. The walls and ceiling are constructed of standard two-by-fours with gypsum-board walls and ceiling clamp reset to make a truly effective ground. Perhaps the path of the copper rod abraded the oxidation on its way into the earth.

At this point, bringing a transistor radio near a grounded section of foil revealed some attenuation of broadcast band signals, but overlapping joints were leaking RF badly. Passing the broadcast band receiver next to a joint while applying enough pressure to seal the junction caused further signal reduction.

"Ground" is one thing to a radio communications technician. To an electrician, "ground" is *neutral*, and neutral may or may not have anything to do with an earth ground.

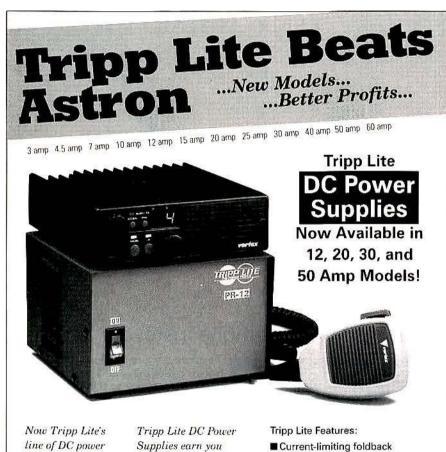With respect to the "tinfoil tomb," the electrical service's earth ground is nearly 70 feet from the junction box used for power distribution to the shielded room. This earth ground consists of a ½-inch rod



\$1.14 MORE

on average than

Astron models

PROFIT PER AMP

Compare Tripp Lite

quality, service and

will agree - the clear

choice is Tripp Lite!

support to Astron

and we think you

Now Tripp Lite's line of DC power supplies cover the full range of amperages, including the popular **12 and 20** amp radios. For dealers, Tripp Lite provides outstanding customer service before and after the sale. Best of all,



500 N. Orleans, Chicago IL 60610 Tel: 312/755-8741 Fax: 312/644-6505 Faxback: 312/755-5420 E-mail: info %tripplite@mcimail.com Web: http://tripplite.com

- Current-limiting foldback for complete over-current protection
- Crowbar overvoltage protection
- Solid state, integrated circuitry
- High quality filtering for very low ripple/low noise
- Fully regulated output maintains 95% of no-load value
- Unbeatable product support, service and reliability
- Rackmount models available

Ready for an alternative to Astron? Call and ask for Dept. PR 2 to sample a Tripp Lite DC Power Supply Today! driven into the earth and clamped to the conduit that extends to the junction box. Several mechanical junctions of the conduit were physically separated from each other, and a few showed a dc shortcircuit when an ohmmeter was connected

#### Pager servicing series

Part 1: "Build a Shielded Room," January 1994. (All pagers.) Part 2: "Build an 'IFFER,'" February

Part 2: "Build an 'IFFER,'" February 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 3: "Frequencies, Coding Formats," March 1994. (Bravo.)

Part 4: "From Bench to Programmer," April 1994. (Bravo.)

Part 5: "The Receivers," May 1994. (Bravo.)

Part 6: "Elegant Simplicity," June 1994. (Bravo.)

Part 7: "Problems in Paradise," July 1994. (Bravo.)

Part 8: "406MHz-512MHz Receivers," August 1994. (Bravo.)

Part 9: "150MHz Receivers," September 1994. (Bravo.)

Part 10: "Tales Crystal Filters Tell ...," October 1994. (Bravo, Bravo Plus, Bravo Express.)

Part 11: "Microprocessor Board," November 1994. (Bravo.)

Part 12: "Headaches (and Some Aspirin)," January 1995. (Bravo.)

Part 13: "Mixed Signals," February 1995. (Bravo.)

Part 14: "Essential Differences," April 1995. (Bravo Plus, Bravo Express.)

Part 15: "And You Shall Receiver Knowledge ...," June 1995. (Bravo Plus, Bravo Express.)

Part 16: "The Information Highway," July 1995. (Bravo Plus, Bravo Express.)

Part 17: "450MHz Receiver Boards," August 1995. (Bravo Plus, Bravo Express.)

Part 18: "Logic/decoder Boards for Bravo Plus, Bravo Express," November 1995. (Bravo Plus, Bravo Express.)

Part 19: "The 'tinfoil tomb,'" January 1996 (All pagers.)

#### **End of Series**

Back issues printed within the past two years can be ordered for \$5 each, postpaid. Call customer service at 800-441-0294. Issues printed more than two years ago and individual article photocopies are unavailable from the publisher. Individual photocopies of articles printed since January 1983 can be ordered from UMI Information Store, 800-248-0360.

Editor's Note: David Ludvigson has made an arrangement with the publisher to offer a compilation of all the articles for purchase. He also is preparing a videotape with pager servicing information based on his articles. You can reach the author at Toltec Communications Resources, Pasadena, TX; tel. 713-947-7660 or 713-946-5521.

| om included: |
|--------------|
|              |
|              |
|              |
|              |
|              |
|              |
|              |
| <u>\$400</u> |
|              |
|              |

on either side of the mechanical junction. To improve the grounding, another <sup>5</sup>/<sub>8</sub>inch copper rod was driven into the earth a few inches from the "grounded" conduit. An 8-foot length of No. 4 gauge stranded copper wire was run to the junction box, and *neutral*, whatever its electrical potential might have been, was grounded.

Electrical service to the "tinfoil tomb" consists of two independent branches, each on a separate 20A breaker. Four double outlets were used with sets 1 and 3 on one branch and sets 2 and 4 on the other.

Aluminum conduit and junctions were

abraded to maintain "interruption-proof" dc integrity at each end before being joined mechanically. It is not enough merely to pass a green-coated wire through the conduit back to the earth ground, but that had better be done, too.

On each side of the ac line, in the outlet boxes, a  $0.1\mu$ F, 600V bypass capacitor effectively reroutes to ground any RF coming down the power lines. Without these bypass capacitors, the transistor radio would "come alive" when passed near the outlets. These same capacitors render wireless intercoms nearly worthless as a means of room-to-room communications.

Photo 4 on page 10 shows the placement of a foil wrap around the No. 4 ground wire. This wire is grounded mechanically and electrically to the foil at the juncture of both walls and the floor.

Foil-backed tape is applied to the entire length of each section's seam. The seams could be taped with virtually any type of tape, but foil-backed tape maintains the visual monotony! Taping each seam prevents RF leakage through each junction.

#### The floor

Photo 5 on page 16 shows how a double-

## **DSPatch**—THE WORLD'S MOST ADVANCED DIGITAL SWITCH FOR VOICE COMMUNICATIONS



Ttilities, airlines, railroads, public-safety, military and other government agencies worldwide have come to rely on Avtec for advanced, high-capacity console solutions for integrated radio/telephone systems. DSPatch is a color touchscreen console system that employs Digital Signal Processors (DSP's) at every line and workstation. Its distributed

architecture ensures instant responses, even in large systems. DSPatch may be configured to support from 32 to 1,024 external lines or operator workstations.

#### FEATURES INCLUDE:

- User configurable screens
- Conventional or trunked radio
- ANI with call queue
- Multi-format paging
- Simultaneous conferences
- Many more

DSPatch32, a 32-port system, is available for smaller applications.

Call, fax or write for additional information or a budgetary proposal.



4335 Augusta Highway Gilbert, SC 29054 USA Phone: (803) 892-2181 FAX: (803) 892-3715



Photo 5. A double-layer of foll on the floor is taped and bonded to the wall foil. Crosspieces will support the floor deck.



Photo 6. Foil-backed tape covers the bottom of the 2"×2" floor frame of interlocking crosspieces to maintain bonding even if the underlying foil becomes abraded.

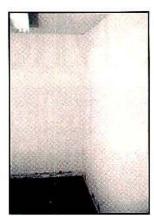


Photo 7. The southeast corner before shielding. The fluorescent light fixture requires bypassing and bonding to the foil.

Photo 8. The southeast corner after shielding. The foil, floor support lattice and electrical service boxes are put in place.

layer of foil is laid, taped and bonded to the protruding wall foil shown in Photo 2. Liberal use of foil-backed tape virtually hermetically seals the flooring to the walls.

John Espinoza's custom woodworking provided an interlocking  $2" \times 2"$  frame and filler crosspieces to support the ¾-inch plywood floor. Foil-backed tape covers the bottom of this frame to maintain bonding should the underlying foil be abraded. (See Photo 6 above.)


Photos 7 and 8 above right are *before* and *after* views of the southeast corner during construction.

Applying spray-on adhesive, Irving Johnson and John Espinoza covered the exposed ceiling (Photos 9 and 10 on page 18) and then placed the foil. (See Photos 11 and 12 on page 18.) Again, these overlapping junctions were stapled and taped to prevent RF leakage.

The dangling fluorescent light fixture was bypassed with capacitors (using the method described earlier) and bonded to the ceiling foil. A receiver picks up some residual hum near the fixture, but


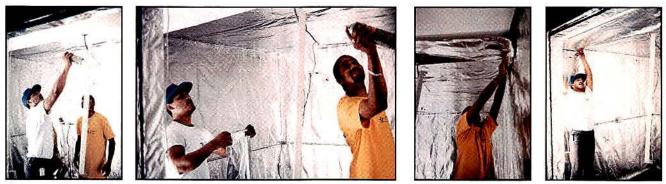
### **CADEX** CADEX ELECTRONICS INC. CALL: 1-800-565-5228 FAX: (604) 451-7991



Photos 9-12. John Espinoza (on the left in the first two photos) and Irving Johnson cover the exposed ceiling with spray adhesive and then place the foil. The overlapping junctions are stapled and taped to prevent RF leakage.

RF signals are virtually eliminated.

Unlike the copper coffin, the door to the "tinfoil" tomb was simple to construct. Photo 13 on page 20 shows that a single layer of aluminum foil was simply stapled directly to the door, folded around the door thickness, and then taped to secure the gaps. The door jamb was treated similarly, becoming in essence an external laminate to the existing woodwork.

Flooring inside the "tinfoil tomb" is about two inches above the concrete floor at the entrance, so foil from the floor was form-fitted around a two-by-four used as a threshold. This configuration provides metal-to-metal contact between the threshold and the door when the door is closed. The elevated floor was covered with carpeting.

Next, a table was constructed along the north wall. This, too, was covered with aluminum foil and bonded to the walls. Over the tabletop, a layer of gray carpeting provides a bit of insulation from the foil. There is not much value in building a table that "shorts out" the circuitry being worked on.

Photos 14 and 15 on page 20 show the equipment setup. From left to right are a Panavise's mount used to secure various boards for servicing, a Ramsey COM 3 service monitor and a KNS Enterprises Cushman multifunction POCSAG/Golay generator.

The large black unit with the blue screen is a Tenma 72-920 40MHz dual-trace oscilloscope. Atop this unit is the modified AM radio described in the February 1994

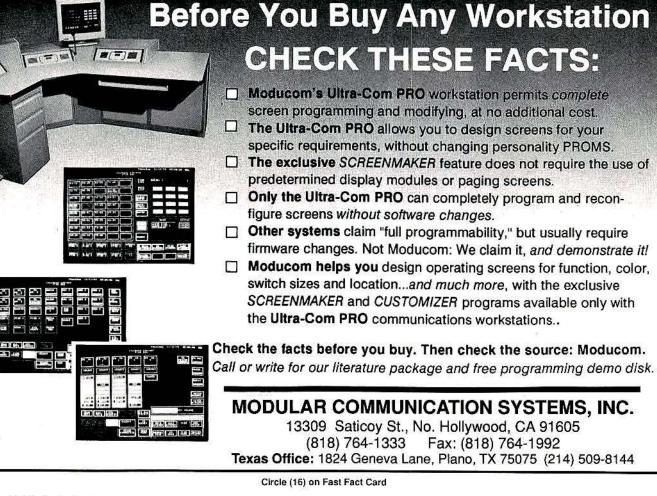




Photo 13. Aluminum foil is stapled directly to the door, folded around it, and then taped to secure the gaps. The door jamb is treated similarly.



Photo 14. The table for equipment used to service pagers has been built in the northeast corner of the shielded room, close to the earth ground connection.

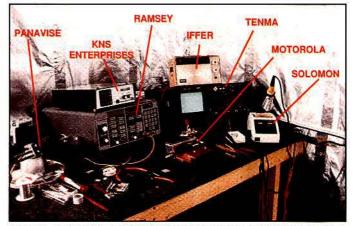


Photo 15. Equipment used for pager servicing includes a PanaVise mount, a Ramsey COM 3 service monitor, a KNS Enterprises Cushman multifunction POCSAG/Golay generator and a Tenma 72-920 40MHz dual-trace oscilloscope. Additional equipment includes an 'IFFER,' a Solomon Brothers SL-10 soldering station and a Motorola RTL 1005 radiation test fixture.

article "Servicing Pagers: Build an 'IFFER.'" A Solomon Brothers SL-10 soldering station (available from Micro Alarm Systems, 800-736-2999) provides temperature-controlled soldering convenience. For \$42.50, it is a surprising value, and it includes a grounding post (guess where that is connected?) and multiple replacement tips.

At front and center is the Motorola RTL-1005 radiation test fixture, surrounded by hand tools and repair aids. In the white box next to the soldering station is a jeweler's loupe, a 10-power monocle that

HIGH Q FILTERS NOTCH AND BANDPASS Low loss Broad frequency range 30-950 MHz Single, double & triple cavities for spot or wider band attenuation Excellent power handling & temperature stability Field tunable For more information, request our data sheets for HIGH Q FILTERS. MICROWAVE FILTER COMPANY 6743 KINNE STREET EAST SYRACUSE, NY 13057 800-448-1666 • 315-437-3953 FAX: 315-463-1467

attaches to the eyeglass bow.

Project expenses are detailed in the box on page 14.

#### How does it work?

Preliminary testing shows little difference between the copper-circuit-boardand the aluminum-foil-shielded rooms. Both require excellent grounding, and both provide about 50dB of attenuation to 930MHz signals. With the aluminum version, copper oxidation is a thing of the past, and any RF leaks can be fixed with a patch of aluminum foil and aluminum tape.

With both rooms, RF has to be piped in by coax connectors to bring in enough signal for a pager to receive on-the-air signals. Received signal strength on a pager is roughly equivalent to that generated by the Ramsey Com 3 when the attenuator is at full minimum (X1 scale with variable attenuator set at minimum). The room *is* effective.

#### Acknowledgement

My thanks to Raymond Duran, Irving Johnson, John Espinoza and Leo Rodriguez at JJ Sounds and Communications. South Houston, TX, for their help with this project. Additional thanks go to the management and staff of Toltec Communications Resources, Pasadena, TX, for their help with this project. Tel. 713-947-7660. My thanks as well to readers who have called with thought-provoking questions and kind words about this article series.

啣

Circle (18) on Fast Fact Card